



Digital design

Ch 4. Combinational logic



4-1 Combinational circuits

- Outputs are determined from the **present** inputs
- Consist of input/output variables and logic gates

 


Fig. 4-1 Block Diagram of Combinational Circuit

4-2 Analysis procedure

- To determine the function of circuit
- Analysis procedure
 - Make sure the circuit is **combinational** or **sequential**
 - Obtain the output Boolean functions or the truth table

Obtain procedure

- Boolean function
 - Label all gate outputs
 - Make output functions at each level
 - Substitute final outputs to input variables
- Truth table
 - Put the input variables to binary numbers
 - Determine the output value at each gate
 - Obtain truth table

Obtain procedure

Table 4-1

Truth Table for the Logic Diagram of Fig. 4-2

A	B	C	F_2	F_2	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

 


Fig. 4-2 Logic Diagram for Analysis Example

4-3 Design procedure

1. Determine the required number of input and output from specification
2. Assign a letter symbol to each input/output
3. Derive the truth table
4. Obtain the simplified Boolean functions
5. Draw the logic diagram and verify design correctness

Code conversion example

- BCD to excess-3 code converter
 - Excess-3 code : decimal digit+3

Code conversion example

Table 1-5
Four Different Binary Codes for the Decimal Digits

Decimal digit	BCD 8421	2421	Excess-3	8 4-2-1
0	0000	0000	0011	0 0 0 0
1	0001	0001	0100	0 1 1 1
2	0010	0010	0101	0 1 1 0
3	0011	0011	0110	0 1 0 1
4	0100	0100	0111	0 1 0 0
5	0101	1011	1000	1 0 1 1
6	0110	1100	1001	1 0 1 0
7	0111	1101	1010	1 0 0 1
8	1000	1110	1011	1 0 0 0
9	1001	1111	1100	1 1 1 1
Unused bit combinations	1010	0101	0000	0 0 0 1
	1011	0110	0001	0 0 1 0
	1100	0111	0010	0 0 1 1
	1101	1000	1101	1 1 0 0
	1110	1001	1110	1 1 0 1
	1111	1010	1111	1 1 1 0

Code conversion example

- BCD to excess-3 code converter
 - Excess-3 code : decimal digit+3
- Design procedure
 - 1) Determine inputs/outputs
 - Inputs : A,B,C,D (0000~1001)
 - Outputs : W,X,Y,Z (0011~1100)

Code converter example

2)Derive truth table

Table 4-2
Truth Table for Code-Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Code converter example

3) Obtain simplified Boolean functions

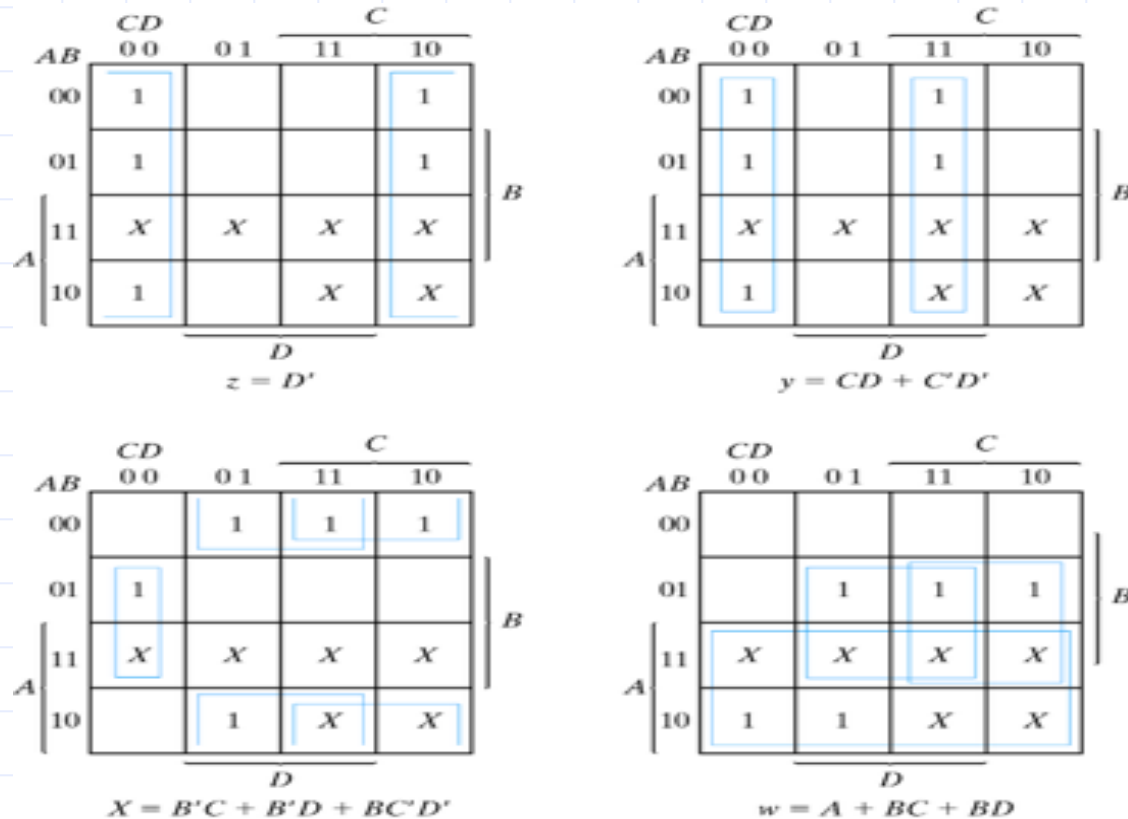


Fig. 4-3 Maps for BCD to Excess-3 Code Converter

Code converter example

4) Draw the logic diagram

$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$\begin{aligned} x &= B'C + B'D + BC'D' = B'(C + D) + BC'D' \\ &= B'(C + D) + B(C + D)' \end{aligned}$$

$$w = A + BC + BD = A + B(C + D)$$

 


Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter

4-4 Binary adder-subtractor

- Binary adder
 - Half adder : performs the addition of 2-bits($x+y$)
 - Full adder : performs the addition of 3-bits($x+y+z$)
 - Two half adder can be employed to a full adder
- Realization of Binary adder-subtractor
 - Half adder
 - Full adder
 - Cascade of n -full adder
 - Providing a complementing circuit

Half Adder

- Sum of 2 binary inputs
- Input : X(augend), Y(addend)
Output : S(sum), C(carry)


Table 4-1
Truth Table for the Logic Diagram of Fig. 4-2

A	B	C	F ₂	F ₂	T ₁	T ₂	T ₃	F ₁
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1


$$S = xy' + x'y$$

$$C = xy$$

Half adder

 
 
$$\begin{aligned} \text{(a) } S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$\begin{aligned} \text{(b) } S &= x \oplus y \\ C &= xy \end{aligned}$$


Fig. 4-5 Implementation of Half-Adder

Full adder


- Sum of 3 binary inputs
- Input : X,Y(2 significant bits),Z(1 carry bit)
- Output : S(sum),C(carry)

Table 4-4
Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$C = xy + xz + yz$$

$$= xy + xy'z + x'yz$$

Fig. 4-6 Maps for Full Adder

Full adder

 


Fig. 4-7 Implementation of Full Adder in Sum of Products

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

지연시간:

$x \Rightarrow s$: 2ns
 $x \Rightarrow c$: 5ns
 $y \Rightarrow s$: 2ns
 $y \Rightarrow c$: 4ns
 $z \Rightarrow s$: 1ns
 $z \Rightarrow c$: 4ns

Binary adder

- Sum of two n-bit binary numbers

- 4-bit adder

A=1011, B=0011

Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

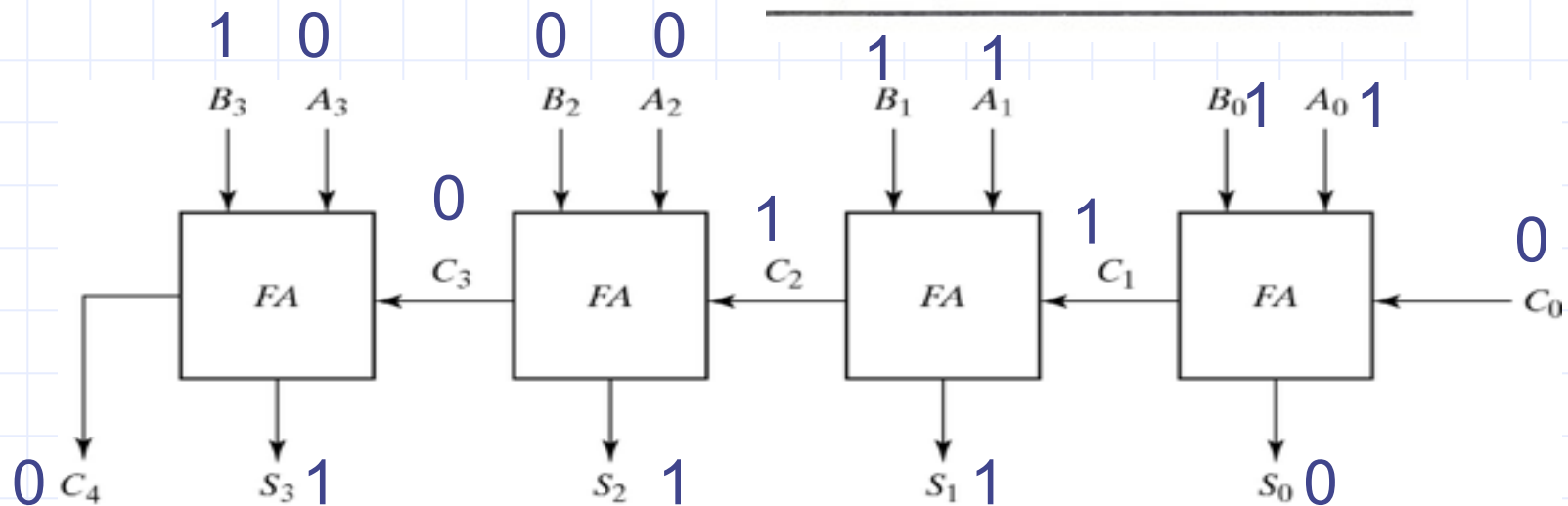


Fig. 4-9 4-Bit Adder

Carry propagation

- Rising of delay time(carry delay)
- One solution is carry lookahead
- All carry is a function of P_i, G_i and C_0

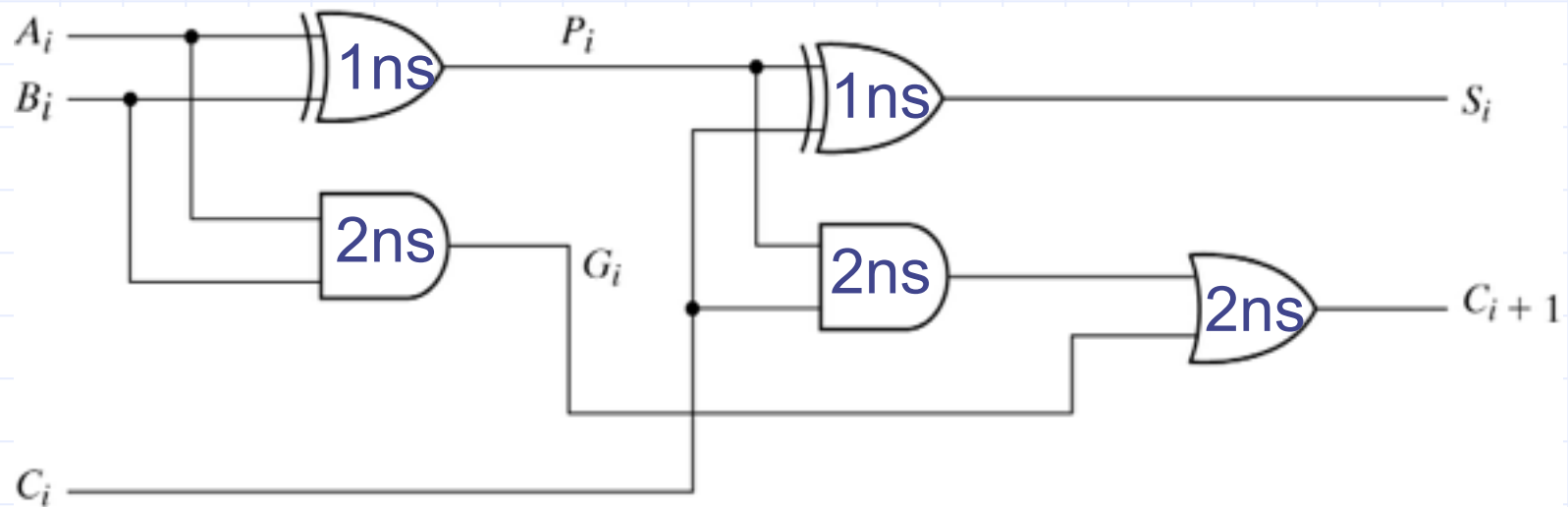


Fig. 4-10 Full Adder with P and G Shown

Carry propagation

- Carry lookahead generator

C_0 = input carry

$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1(G_0 + P_0C_0) = G_1 + P_1G_0 + P_1P_0C_0$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

Carry propagation

- 4-bit adder with carry lookahead

 


Fig. 4-12 4-Bit Adder with Carry Lookahead

Binary subtractor

- $A - B = A + (2\text{'s complement of } B)$
- When $M=0$ (act as adder) $M=1$ (subtractor)


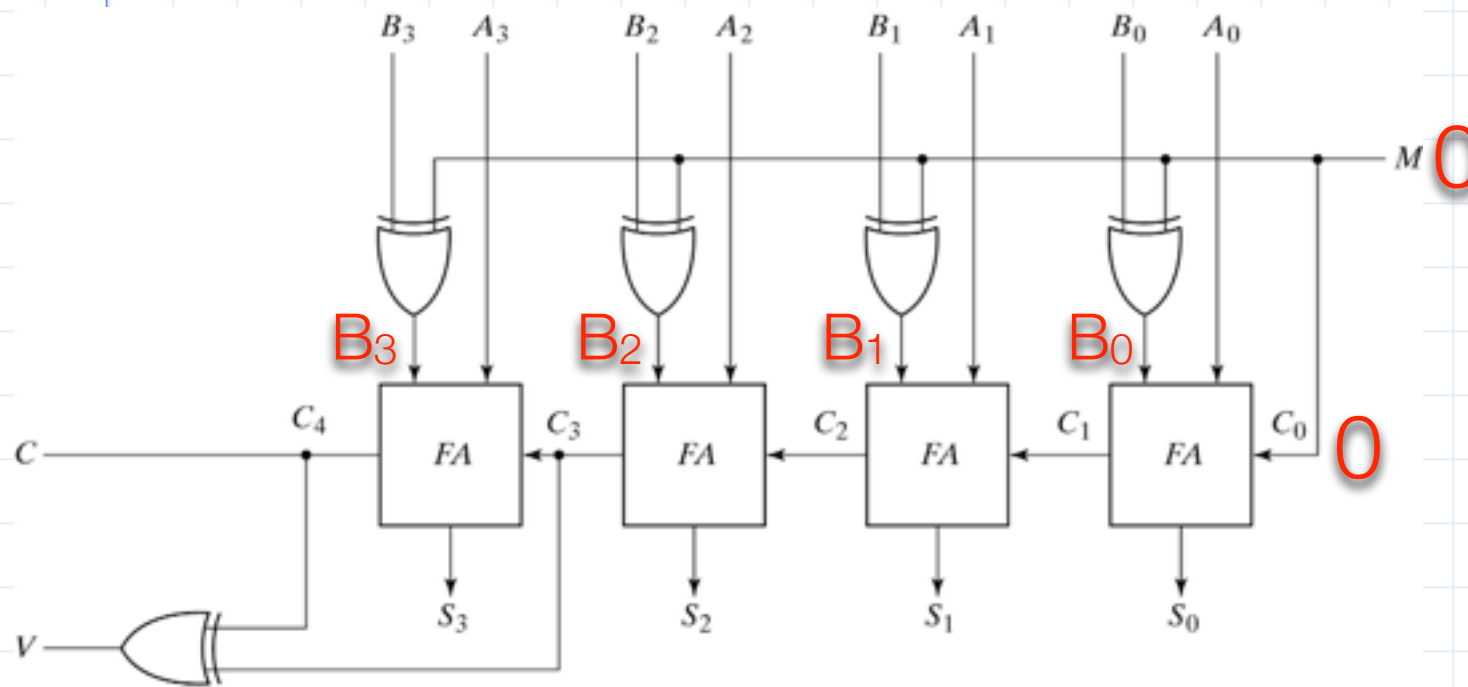


Fig. 4-13 4-Bit Adder Subtractor

$$x \oplus 0 = x, \quad x \oplus 1 = x'$$

Binary subtractor

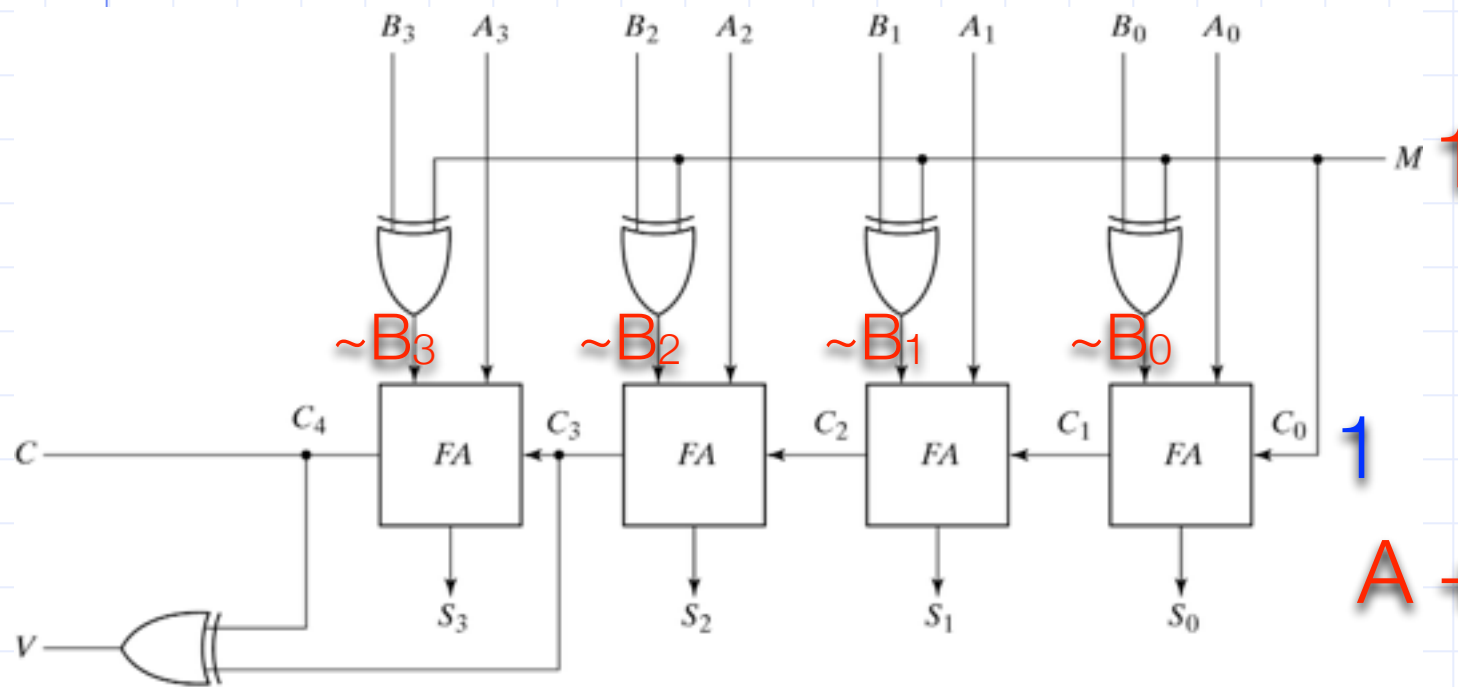- $A - B = A + (2\text{'s complement of } B)$
- When $M=0$ (act as adder) $M=1$ (subtractor)



$$A + (\sim B) + 1$$

Fig. 4-13 4-Bit Adder Subtractor

$$x \oplus 0 = x, x \oplus 1 = x'$$

Overflow

- Sum of n digit number occupies n+1 digit
- Occurs when two numbers are same sign
(examples of overflow)

carries:	0	1	
+70	0	1000110	
+80	0	1010000	
—	—	—	
+150	1	0010110	

(양수)+(양수) => (음수)

carries:	1	0	
-70	1	0111010	
-80	1	0110000	
—	—	—	
-150	0	1101010	

(음수)+(음수) => (양수)

4-5 Decimal adder

- Calculate binary and represent decimal in binary coded form
- Decimal adder for the BCD code

BCD Adder

- BCD digit output of 2-BCD digit sum
- Carry arise if output 1010~1111

$$C = K + Z_8 Z_4 + Z_8 Z_2$$

1100 1010
1101 1011
1110
1111

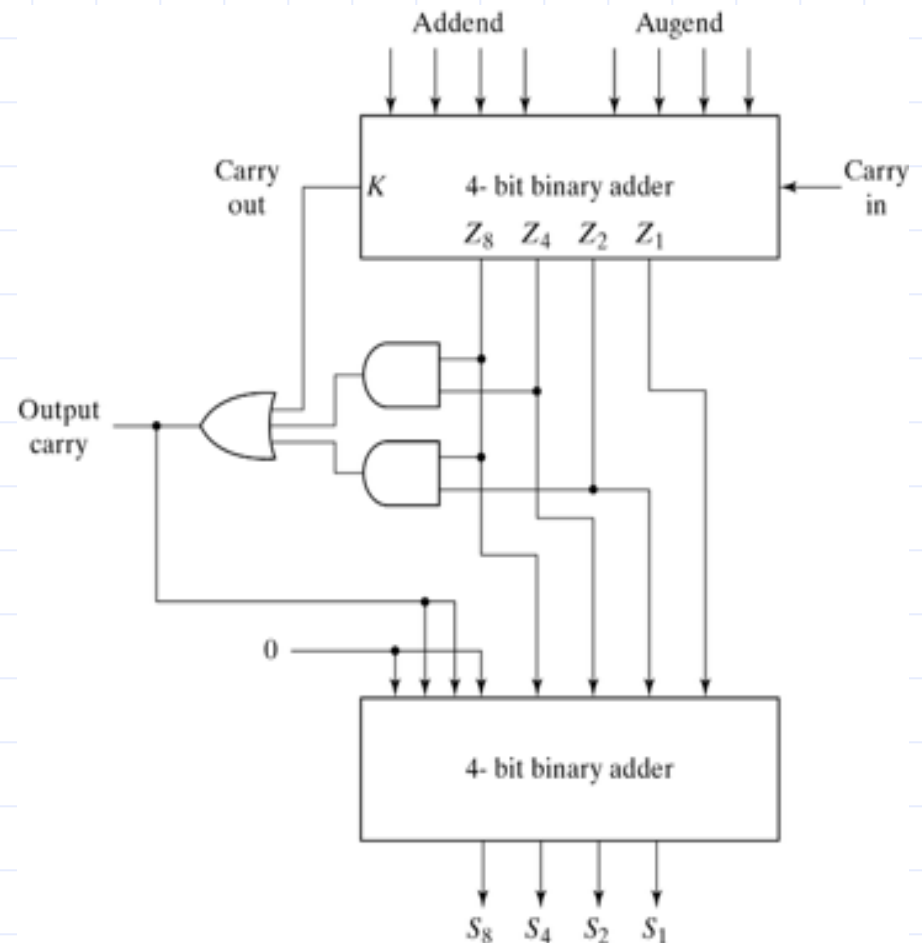


Fig. 4-14 Block Diagram of a BCD Adder

4-6 Binary multiplier

- 2bit x 2bit = 4bit(max)

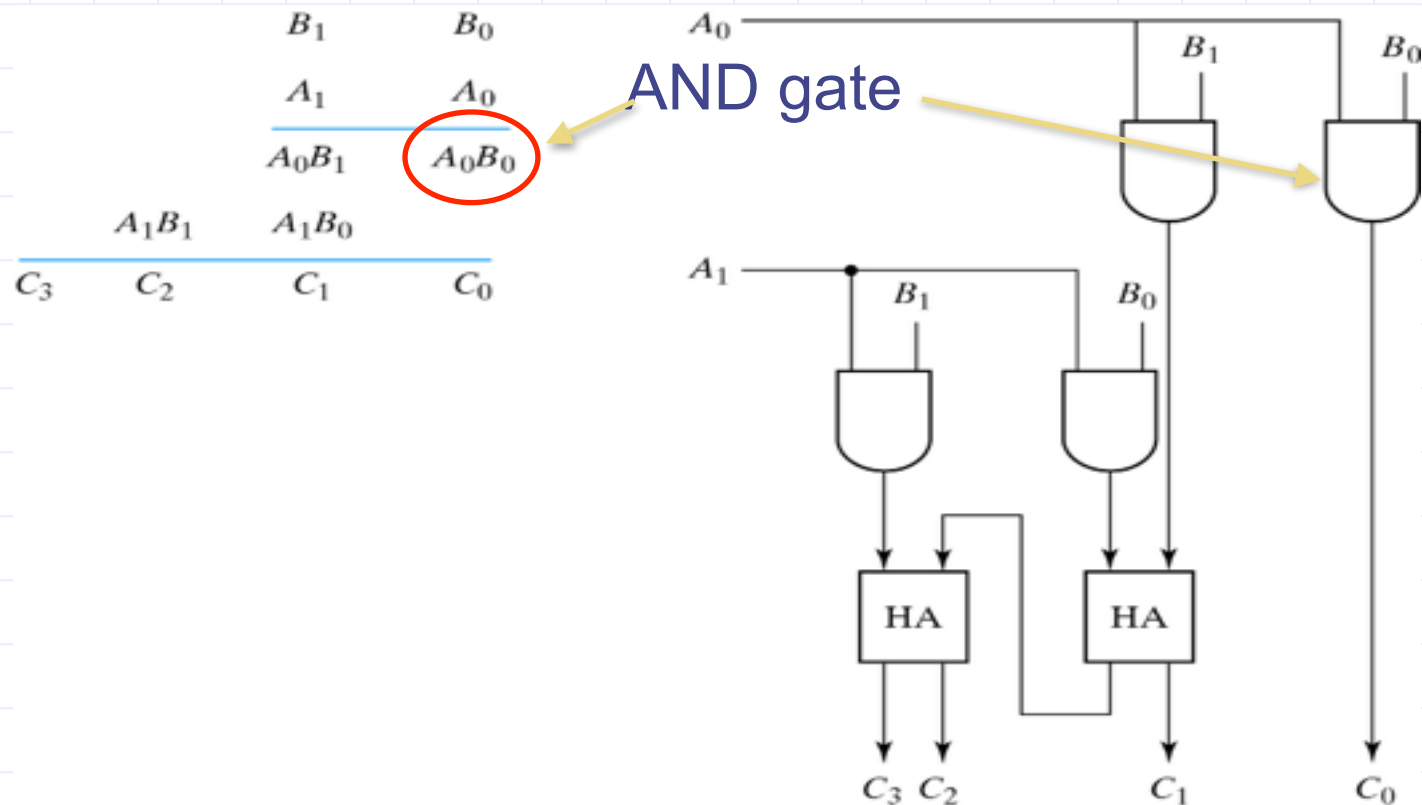


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

Binary multiplier

- (K-bit) x (J-bit)
 - (K x J) AND gates,
 - (J-1) K-bit adder needed

$$\begin{array}{r}
 \begin{array}{cccc}
 B_3 & B_2 & B_1 & B_0 \\
 \times & A_2 & A_1 & A_0 \\
 \hline
 A_0B_3 & A_0B_2 & A_0B_1 & A_0B_0 \\
 A_1B_3 & A_1B_2 & A_1B_1 & A_1B_0 \\
 A_2B_3 & A_2B_2 & A_2B_1 & A_2B_0
 \end{array}
 \end{array}$$

 


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

4-7 Magnitude comparator

- $X_i = 1$ only if the pair of bits in i are equal
- $(A=B) = x_3 x_2 x_1 x_0$
- $(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$
- $(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$
- $x_i = A_i' B_i + A_i B_i'$

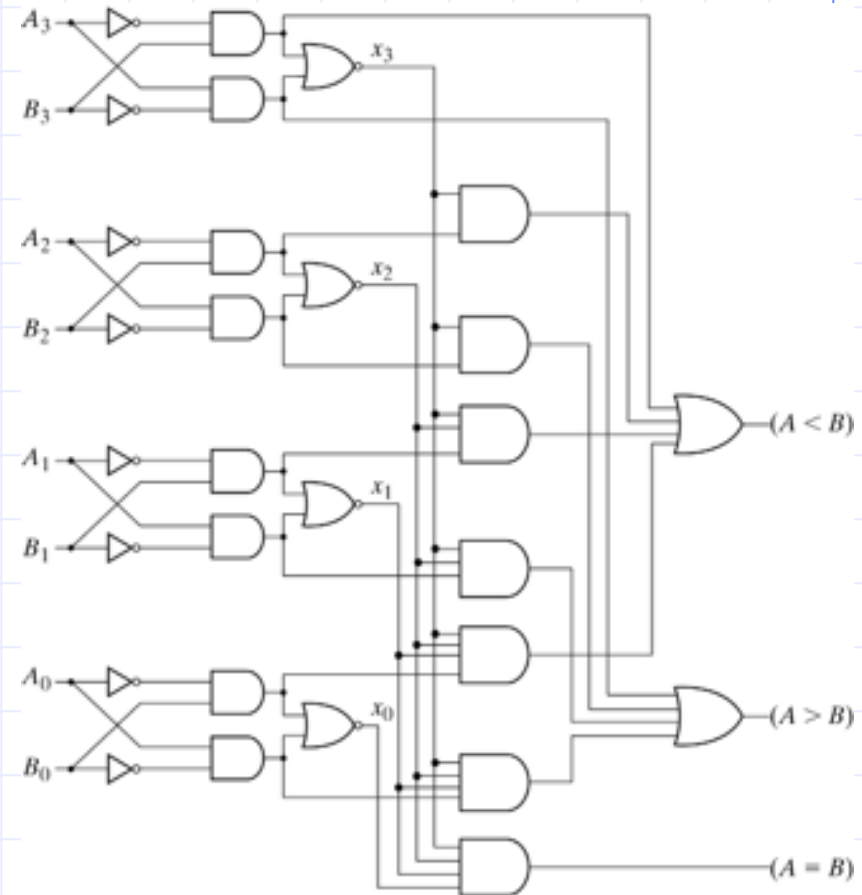


Fig. 4-17 4-Bit Magnitude Comparator

4-8 Decoders

- Generate the 2^n (or less) minterms of n input variables
 - Eg)3 to 8 line decoder

Table 4-6
Truth Table of a 3-to-8-Line Decoder

Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


 


Fig. 4-18 3-to-8-Line Decoder

Decoders

 - 2 to 4 line decoder with Enable input
 - Control circuit operation by E



(a) Logic diagram

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

Decoders

- Decoders with enable inputs can be a larger decoder circuit

Eg) 4x16 decoder by two 3x8 decoders

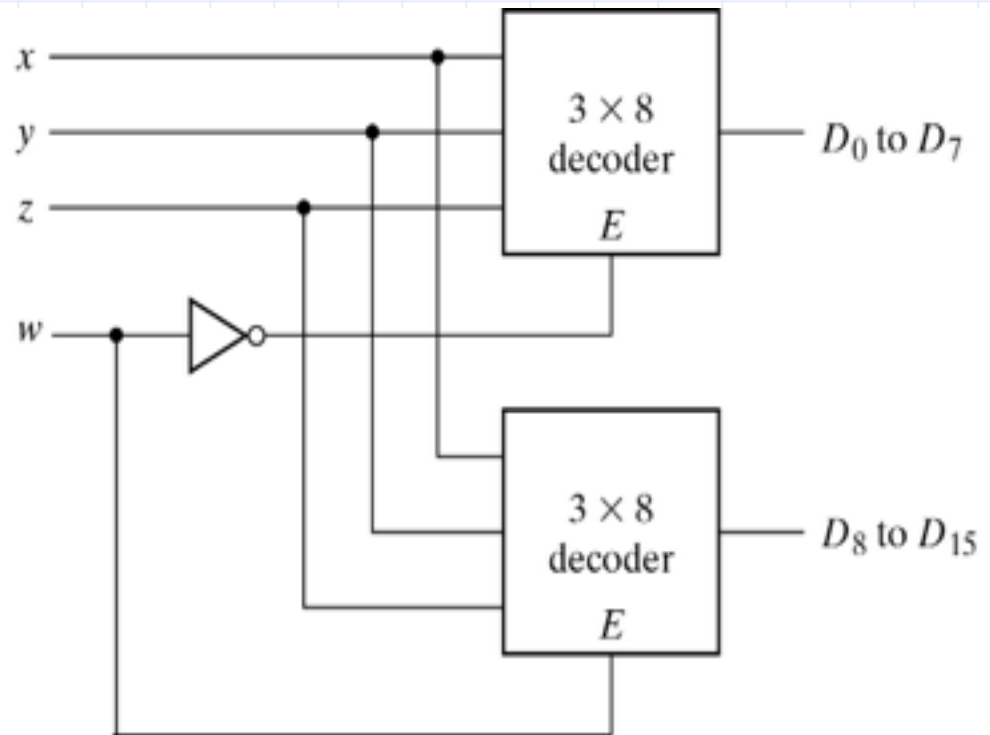


Fig. 4-20 4×16 Decoder Constructed with Two 3×8 Decoders

Decoders

- Combinational logic implementation
 - Any combinational circuit can be implemented with line decoder and OR gates
 - Eg)full adder

Table 4-4
Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

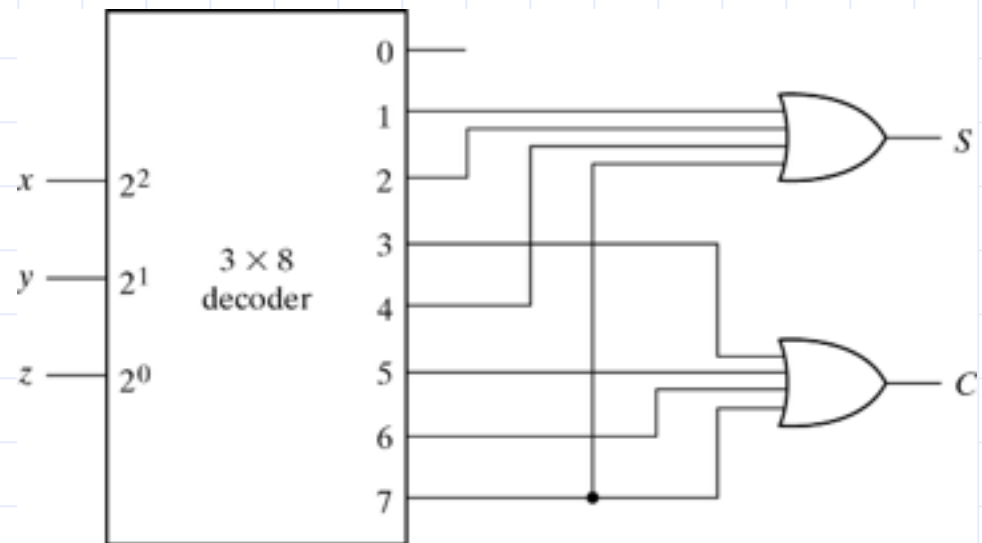


Fig. 4-21 Implementation of a Full Adder with a Decoder

4-9 Encoders

- Inverse operation of a decoder
- Generate n outputs of 2^n input values
 - Eg) octal to binary encoder

Table 4-7
Truth Table of Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Priority encoder

- Problem happens two or more inputs equal to 1 at the same time
- Give a priority function to circuit

Table 4-8
Truth Table of a Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

(x100 means 0100, 1100)

 


Fig. 4-22 Maps for a Priority Encoder

4-10 Multiplexers


- Select a binary information from many input lines
- Selection is controlled by a set of selection lines
- 2^n input lines have n selection lines

Multiplexers

- 4 to 1 line multiplexer

s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

 

(a) Logic diagram

Multiplexers

- Quadruple 2 to 1 line multiplexer

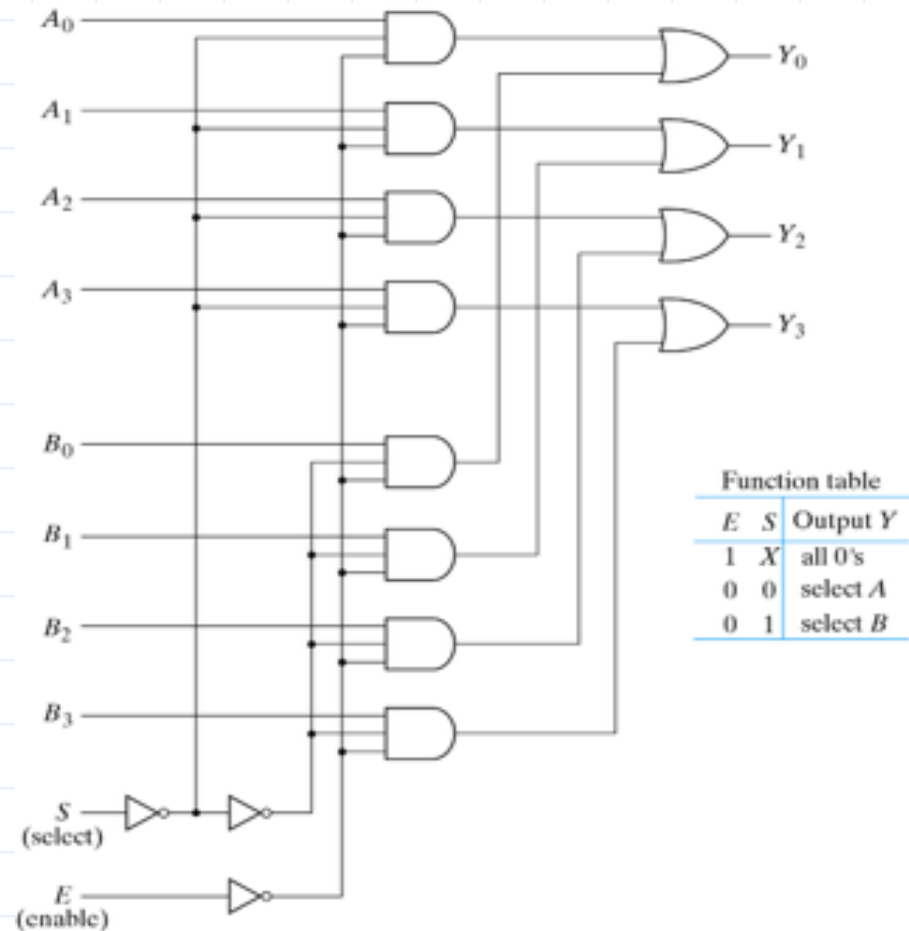



Fig. 4-26 Quadruple 2-to-1-Line Multiplexer

Multiplexers

- Boolean function implementation
 - Minterms of function are generated in a MUX
 - n input variables, $n-1$ selection input

x	y	z	F	
0	0	0	0	
0	0	1	1	$F = z$
0	1	0	1	
0	1	1	0	$F = z'$
1	0	0	0	
1	0	1	0	$F = 0$
1	1	0	1	
1	1	1	1	$F = 1$

(a) Truth table

 

(b) Multiplexer implementation

$$F = xy + yz' + x'y'z$$

Multiplexers

- Three-state gates
 - Logic 1, 0 and high-impedance
 - High-impedance behaves like an open circuit


 



Fig. 4-29 Graphic Symbol for a Three-State Buffer

Multiplexers

- Multiplexers with three-state gates

 

(a) 2-to-1- line mux

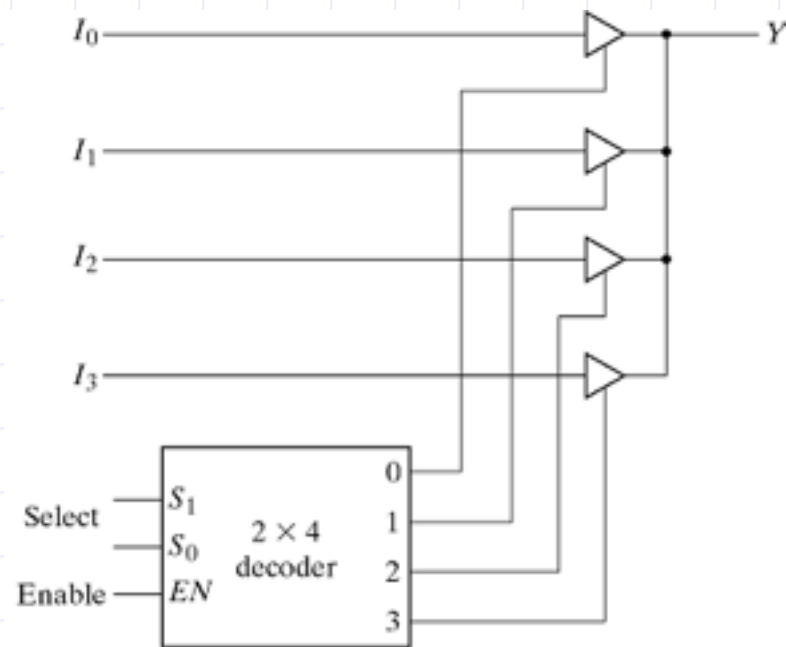

(b) 4 - to - 1 line mux

Fig. 4-30 Multiplexers with Three-State Gates


Verilog HDL

HDL(Hardware Description Language)

- HDL: 하드웨어의 설계에 사용되는 언어
- Verilog HDL은 하드웨어를 모듈 단위로 설계하며, 다양한 방법으로 하드웨어를 기술
- 현재 대부분의 디지털 하드웨어는 HDL을 사용하여 설계됨

HDL(Hardware Description Language)

 - VHDL, Verilog HDL
- Module Representation



```
//HDL
module smpl_circuit(A,B,C,x,y);
  input A,B,C;
  output x,y;
  wire e;
  and g1(e,A,B);
  not g2(y, C);
  or g3(x,e,y);
endmodule
```

HDL(Hardware Description Language)

■ Gate Delays - `timescale 1ns/100ps

```
//Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input A,B,C;
    output x,y;
    wire e;
    and #(30) g1(e,A,B);
    or #(20) g3(x,e,y);
    not #(10) g2(y,C);
endmodule
```

```
//Stimulus for simple circuit
module stimcrct;
    reg A,B,C;
    wire x,y;
    circuit_with_delay cwd(A,B,C,x,y);
    initial
        begin
            A = 1'b0; B = 1'b0; C = 1'b0;
            #100
            A = 1'b1; B = 1'b1; C = 1'b1;
            #100 $finish;
        end
    endmodule
```

HDL(Hardware Description Language)

■ Boolean Expressions

- AND, OR, NOT는 &, |, ~로 표시

assign x = (A & B) | ~C); // (A and B) or (not C)

```
//Circuit specified with Boolean equations
module circuit_bln (x,y,A,B,C,D);
    input A,B,C,D;
    output x,y;
    assign x = A | (B & C) | (~B & C);
    assign y = (~B & C) | (B & ~C & ~D);
endmodule
```

Instantiation

```
module halfadder (S,C,x,y);  
  input x,y;  
  output S,C;  
  //Instantiate primitive gates  
  xor (S,x,y);  
  and (C,x,y);  
endmodule
```

```
module fulladder (S,C,x,y,z);  
  input x,y,z;  
  output S,C;  
  wire S1,D1,D2;  
  //Instantiate the halfadder  
  halfadder HA1 (S1,D1,x,y),  
             HA2 (S,D2,S1,z);  
  or g1 (C,D2,D1);  
endmodule
```

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

Instantiation in 4-bit adder

```
module _4bit_adder (S,C4,A,B,C0);  
    input [3:0] A,B;  
    input C0;  
    output [3:0] S;  
    output C4;  
    wire C1,C2,C3; //Intermediate carries  
    //Instantiate the fulladder  
    fulladder FA0 (S[0],C1,A[0],B[0],C0),  
                FA1 (S[1],C2,A[1],B[1],C1),  
                FA2 (S[2],C3,A[2],B[2],C2),  
                FA3 (S[3],C4,A[3],B[3],C3);  
endmodule
```

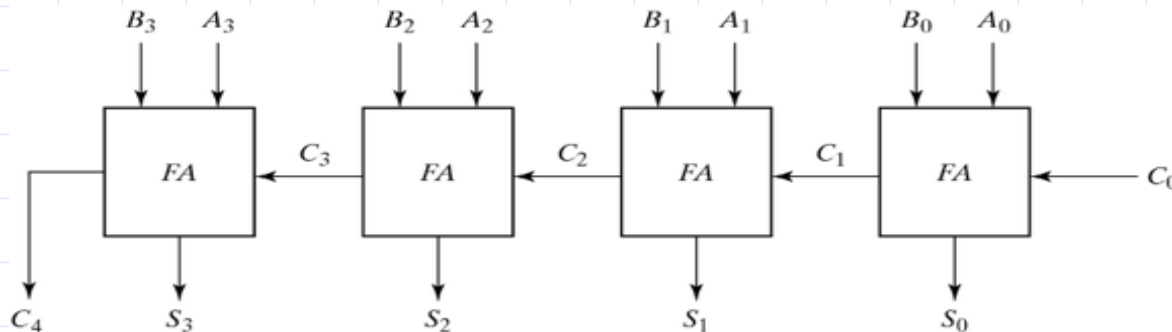



Fig. 4-9 4-Bit Adder

4-11 HDL for combinational circuit

- Modeling techniques:
 - Gate level modeling
 - ◆ Instantiation of gates and user defined modules
 - Dataflow modeling
 - ◆ Using continuous assignment statements-assign
 - Behavioral modeling
 - ◆ Using procedural assignment statements-always

Gate-level modeling

 - Circuit is specified by its **gates** and their **interconnection**(연결)



HDL Example 4-1

```
//Gate-level description of a 2-to-4-line decoder
//Figure 4-19
module decoder_gl (A,B,E,D);
  input A,B,E;
  output [0:3]D;
  wire Anot,Bnot,Enot;
  not
    n1 (Anot,A),
    n2 (Bnot,B),
    n3 (Enot,E);
  nand
    n4 (D[0],Anot,Bnot,Enot),
    n5 (D[1],Anot,B,Enot),
    n6 (D[2],A,Bnot,Enot),
    n7 (D[3],A,B,E);
endmodule
```

Dataflow modeling

- Assign a value to a net by using operands and operators

eg) $J=01, K=10$ can be
 $\{J, K\}=0110$


$\text{out} = x ? A : B$ means
 $\text{out} = A$, if x is true
 $= B$, if x is false

Table 4-10
Verilog HDL Operators

Symbol	Operation
+	binary addition
-	binary subtraction
&	bit-wise AND
	bit-wise OR
^	bit-wise XOR
~	bit-wise NOT
==	equality
>	greater than
<	less than
{ }	concatenation
?:	conditional

Assignment

- 2-to-4 line decoder

 

HDL Example 4-3

//Dataflow description of a 2-to-4-line decoder
//See Fig. 4-19

```
module decoder_df (A,B,E,D);  
    input A,B,E;  
    output [0:3] D;  
    assign D[0] = ~(~A & ~B & ~E),  
           D[1] = ~(~A & B & ~E),  
           D[2] = ~(A & ~B & ~E),  
           D[3] = ~(A & B & ~E);  
endmodule
```

4-bit adder

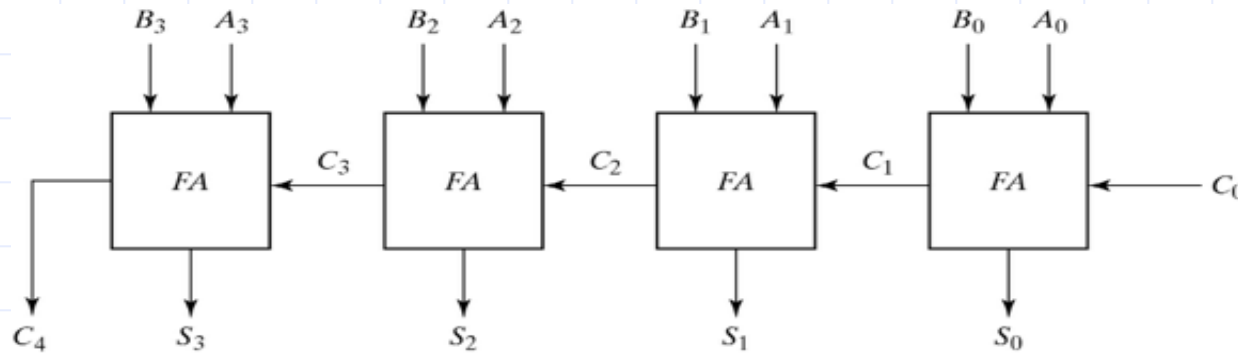


Fig. 4-9 4-Bit Adder

HDL Example 4-4

```
//Dataflow description of 4-bit adder
module binary_adder (A,B,Cin,SUM,Cout);
    input [3:0] A,B;
    input Cin;
    output [3:0] SUM;
    output Cout;
    assign {Cout,SUM} = A + B + Cin;
endmodule
```

Behavioral modeling

- Use procedural assignment statement, **always**
- Target output must be the reg data type

Eg) 4 to 1 line mux

```
module mux4x1_bh (i0,i1,i2,i3,select,y);  
    input i0,i1,i2,i3;  
    input [1:0] select;  
    output y;  
    reg y;  
    always @ (i0 or i1 or i2 or i3 or select)  
        case (select)  
            2'b00: y = i0;  
            2'b01: y = i1;  
            2'b10: y = i2;  
            2'b11: y = i3;  
        endcase  
endmodule
```

Writing a simple test bench

- Test bench : Applying stimulus to test HDL and observe its response
- **reg - inputs , wire - outputs**


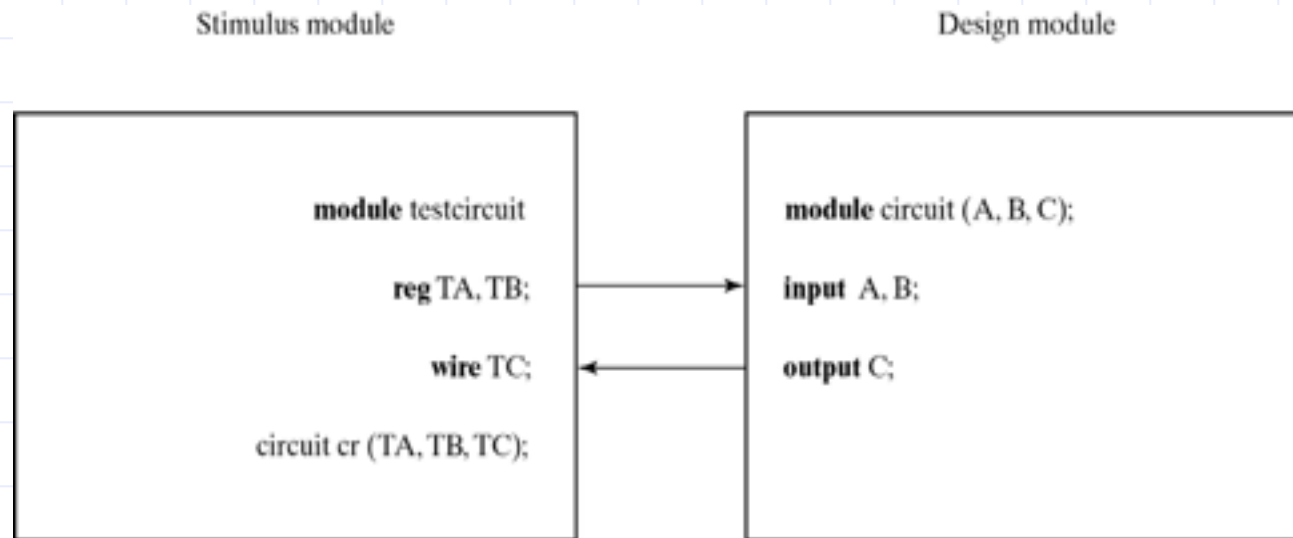


Fig. 4-33 Stimulus and Design Modules Interaction

System tasks

- System tasks : keywords that can display various outputs (begin with \$)
- \$display , \$write , \$monitor , \$time , \$finish
- Format of system tasks
 - Task name(format specification,argument list);
 - Eg) \$monitor(%d %b %b, C,A,B);

Example of testbench

 

```
//Stimulus for mux2x1_df.
module testmux;
    reg TA,TB,TS; //inputs for mux
    wire Y;       //output from mux
    mux2x1_df mx (TA,TB,TS,Y); // instantiate mux
    initial
        begin
            TS = 1; TA = 0; TB = 1;
            #10 TA = 1; TB = 0;
            #10 TS = 0;
            #10 TA = 0; TB = 1;
        end
    initial
        $monitor("select = %b A = %b B = %b OUT = %b time = %0d",
            TS, TA, TB, Y, $time);
endmodule
//Dataflow description of 2-to-1-line multiplexer
//from Example 4-6
module mux2x1_df (A,B,select,OUT);
    input A,B,select;
    output OUT;
    assign OUT = select ? A : B;
endmodule
```