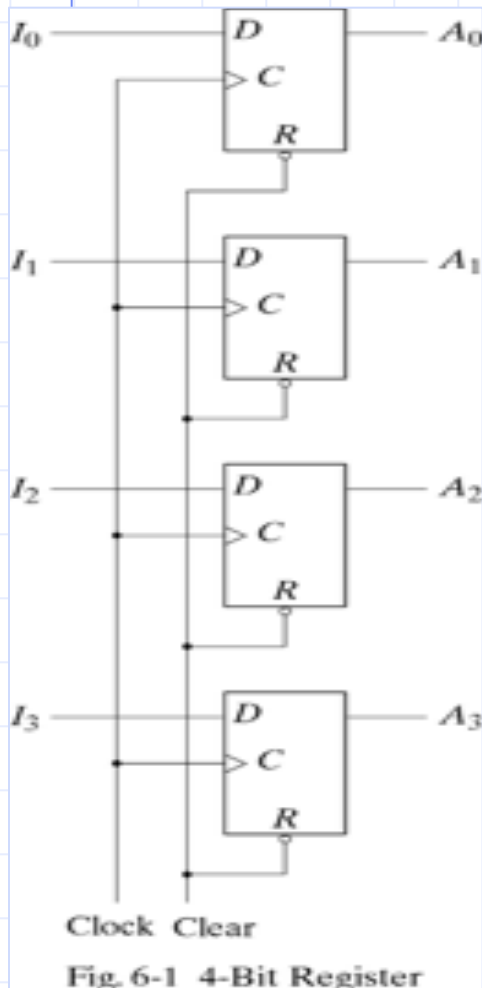


6 Registers and Counters

6-1 REGISTERS

⊕ **Register**- a group of binary cells suitable for holding binary information.



- ❑ Clock=0 -> 1 : input information transferred
- ❑ Clock=0 : unchanged
- ❑ Clear=0 : clearing the register to all 0's prior to its clocked operation.

Register with Parallel Load

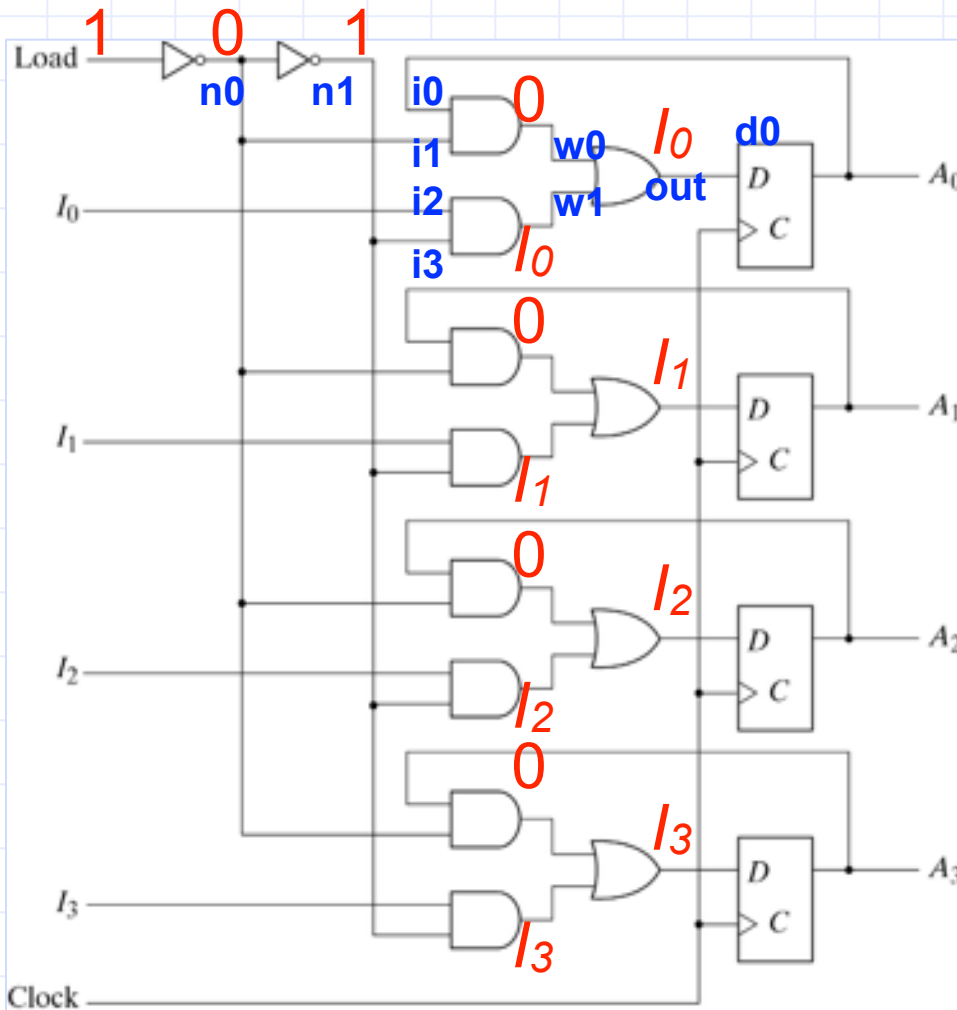


Fig. 6-2 4-Bit Register with Parallel Load

- ❑ Clock=0->1 : input information
-> loading
- ❑ Clock=0 or 0->1 or 1: the content of the register -> unchanged
- ❑ Load input=1 : the I inputs are transferred into the register

Register with Parallel Load


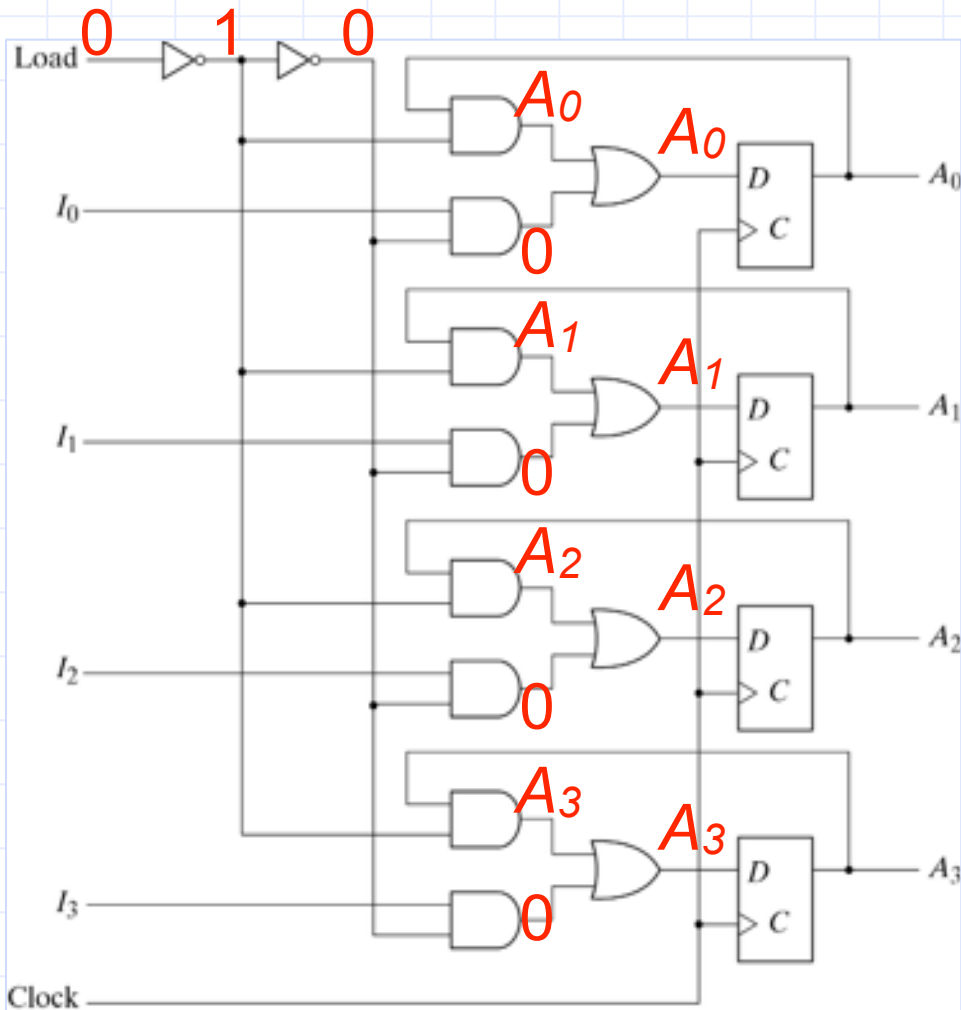


Fig. 6-2 4-Bit Register with Parallel Load

❑ Load input=0 ; maintain the content of the register

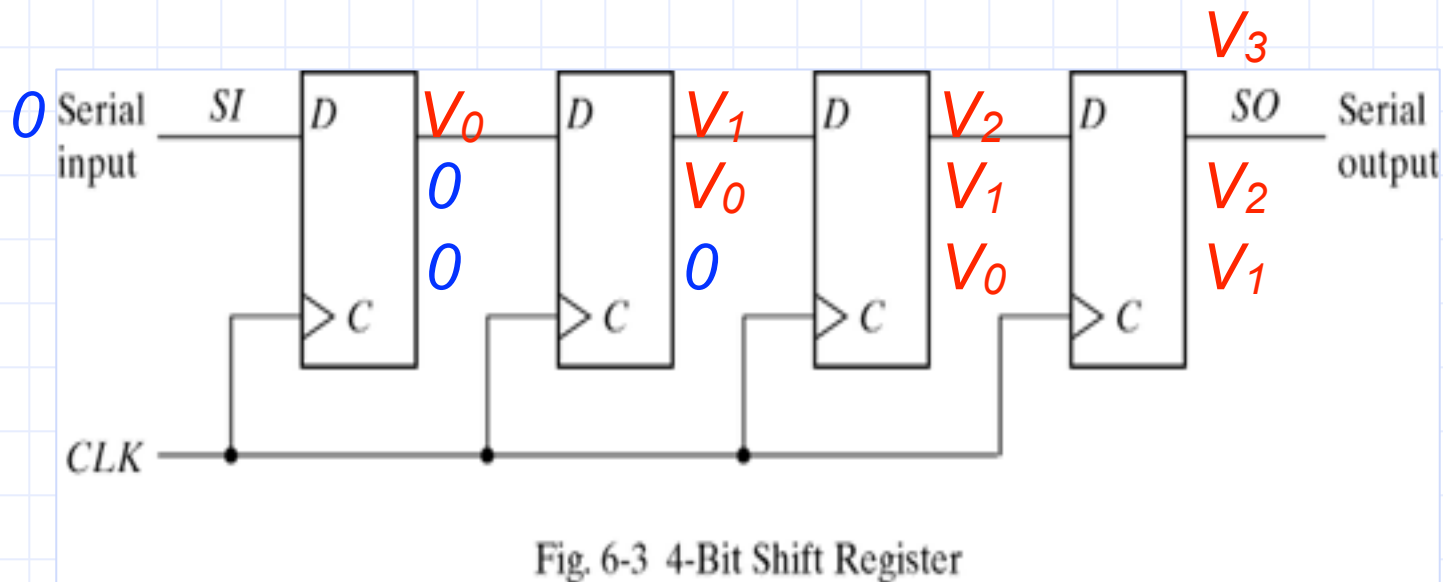6-2 SHIFT REGISTERS


Shift register-capable of shifting its binary information in one or both directions




The simplest shift register

Serial Transfer

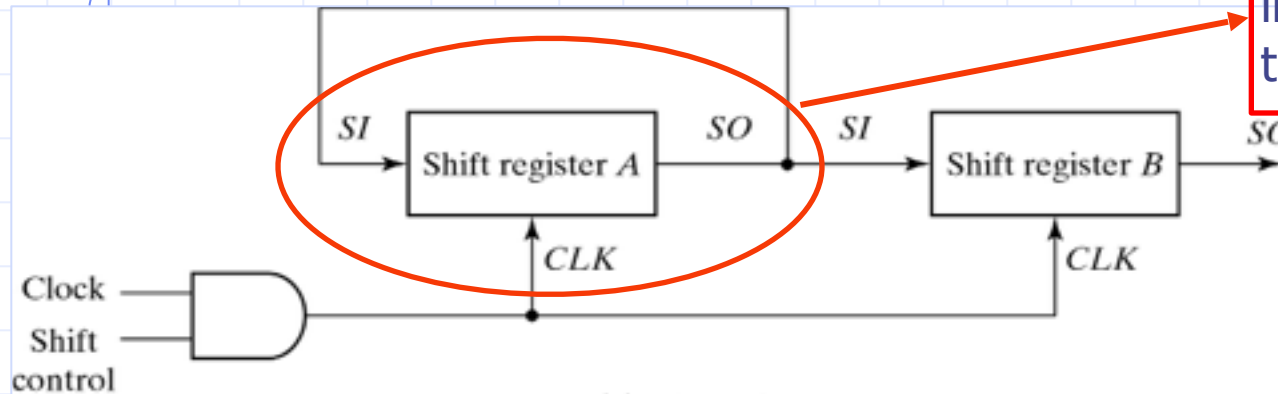To prevent the loss of information stored in the source register



(a) Block diagram

 


(b) Timing diagram

Fig. 6-4 Serial Transfer from Register A to register B


Serial-Transfer Example

Timing pulse	Shift register A	Shift register B	Serial output of B
Initial value	1 0 1 1	0 0 1 0	0
After T ₁	1 1 0 1	1 0 0 1	1
After T ₂	1 1 1 0	1 1 0 0	0
After T ₃	0 1 1 1	0 1 1 0	0
After T ₄	1 0 1 1	1 0 1 1	1


Serial Transfer

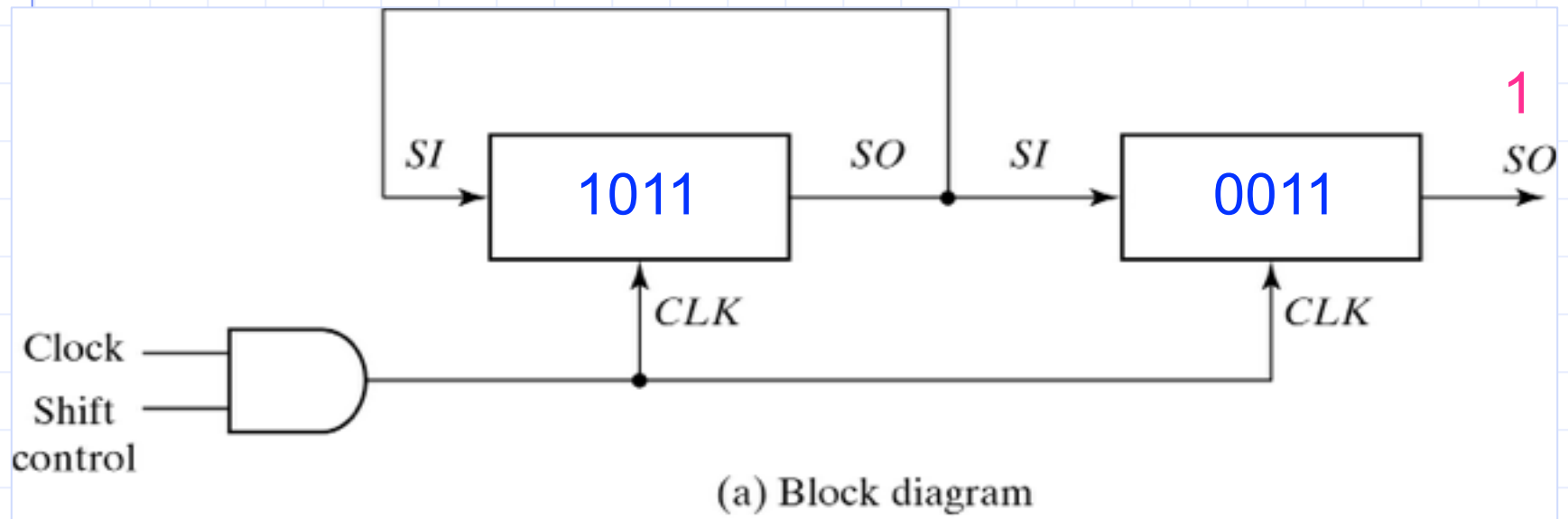


Serial Transfer

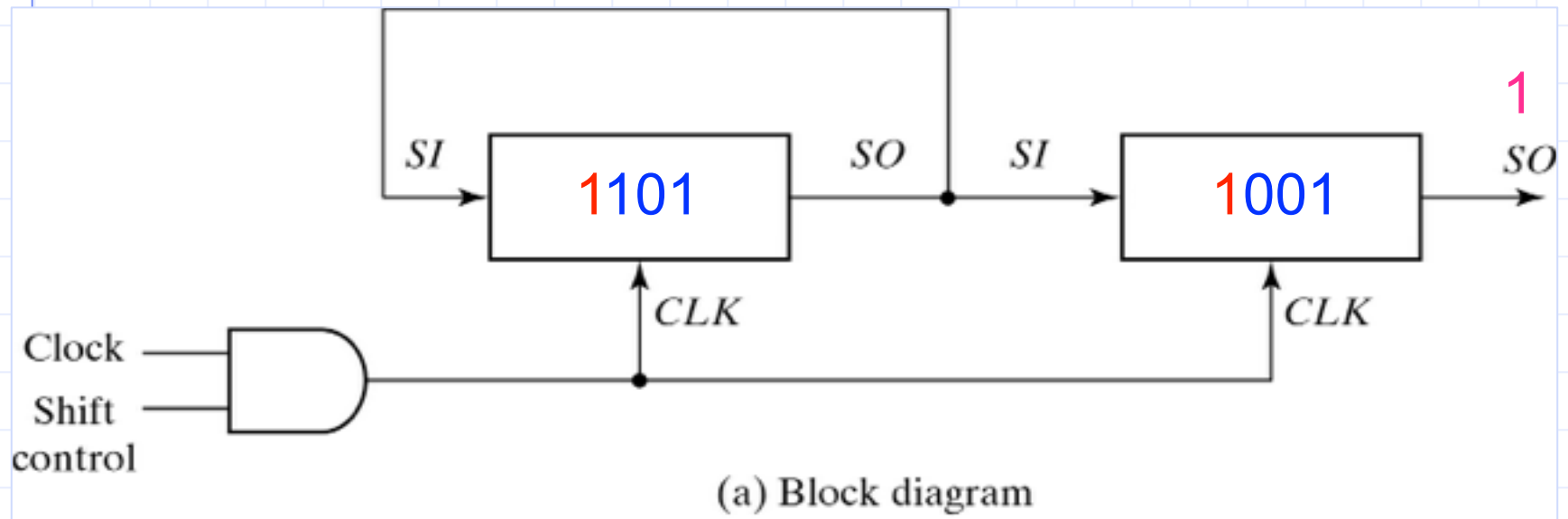


Serial Transfer

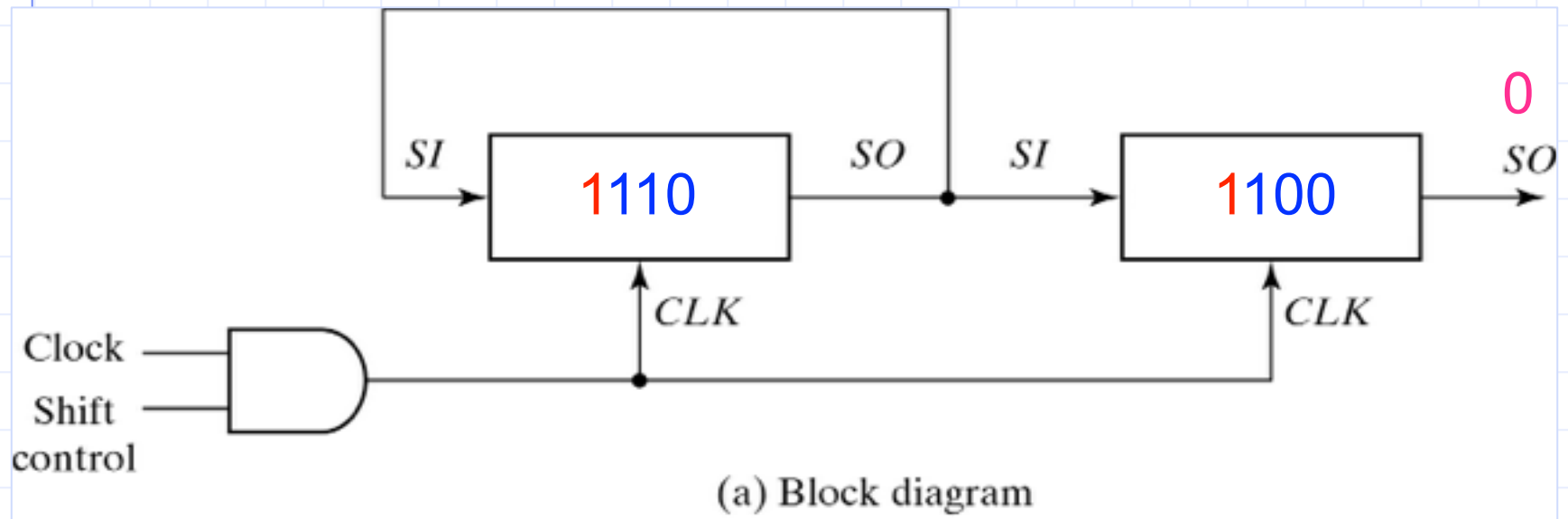

Serial Transfer

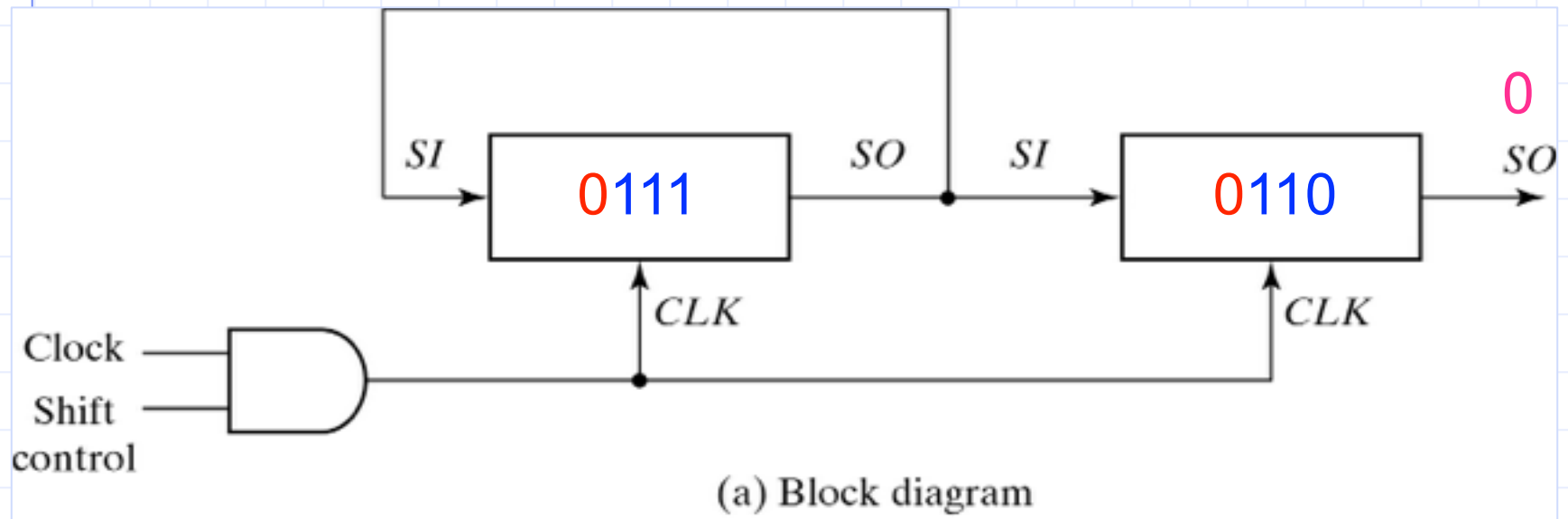

Serial Transfer

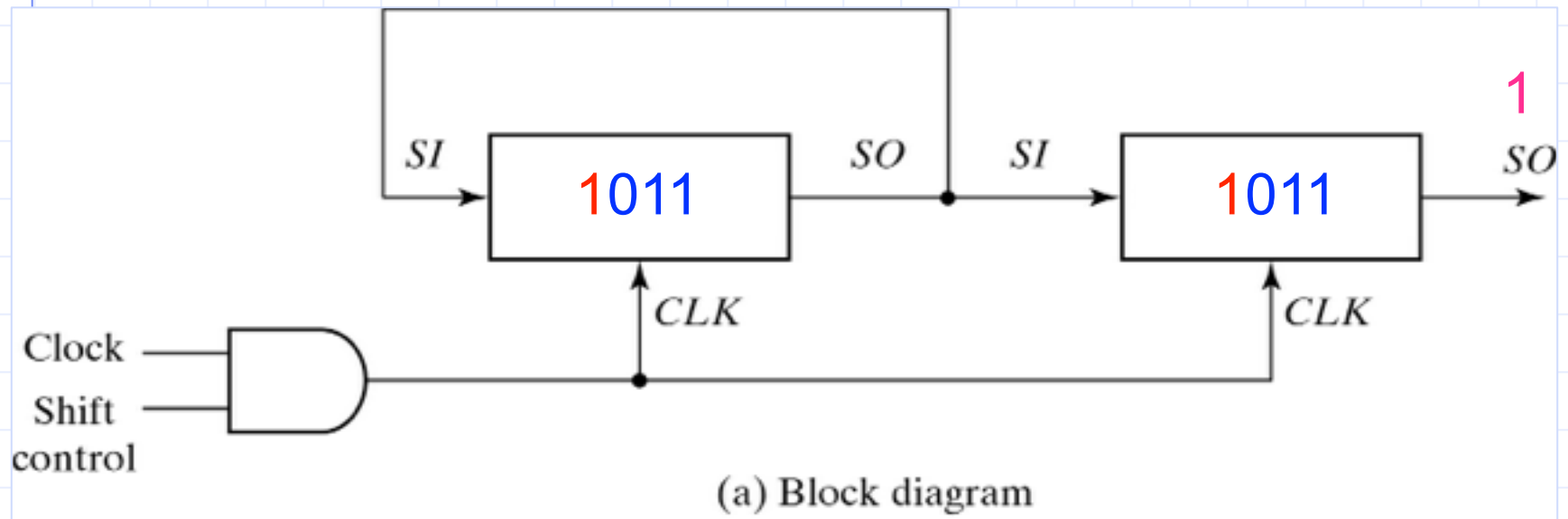

Serial Addition

 


Fig. 6-5 Serial Adder

Operation

- ❑ calculate **A+B**
- ❑ The **SO** of **A** and **B** provide a pair of significant bits for the **FA**
- ❑ Output **Q** gives the input carry at **z**
- ❑ The shift-right control enables both registers and the carry flip-flop.
- ❑ The sum bit from **S** enters the leftmost flip-flop of **A**

Serial Addition

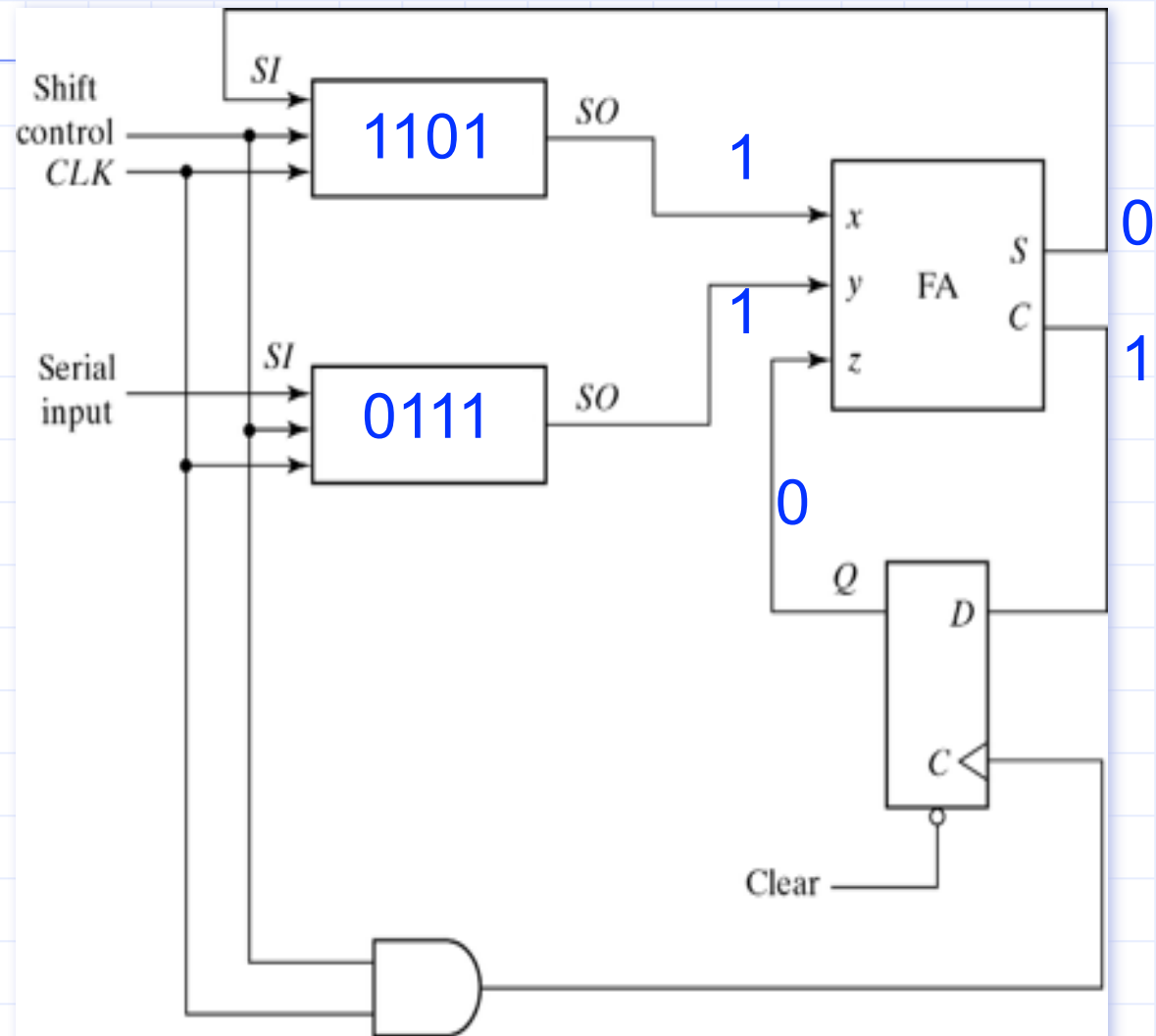


Fig. 6-5 Serial Adder

Serial Addition

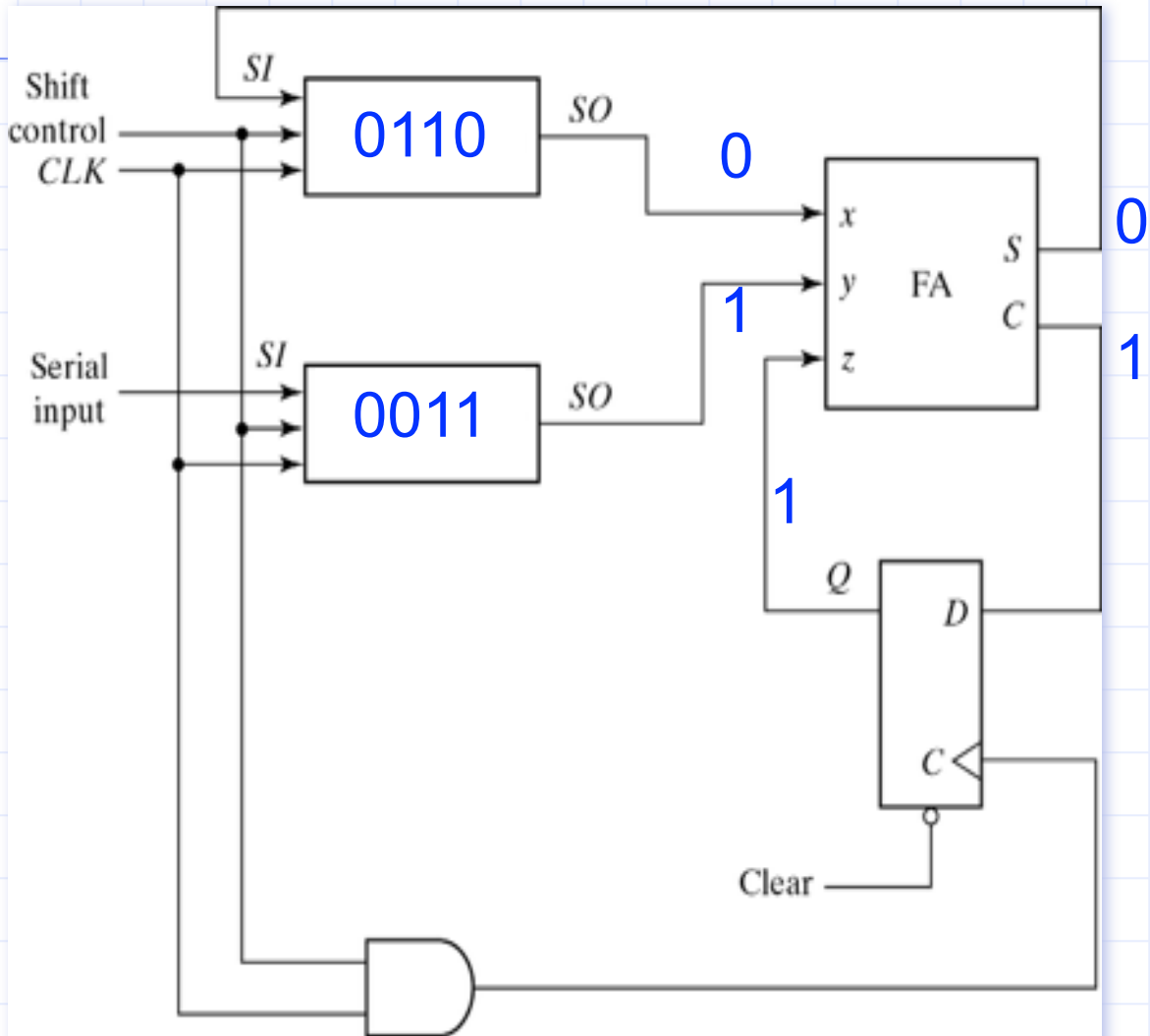


Fig. 6-5 Serial Adder

Serial Addition

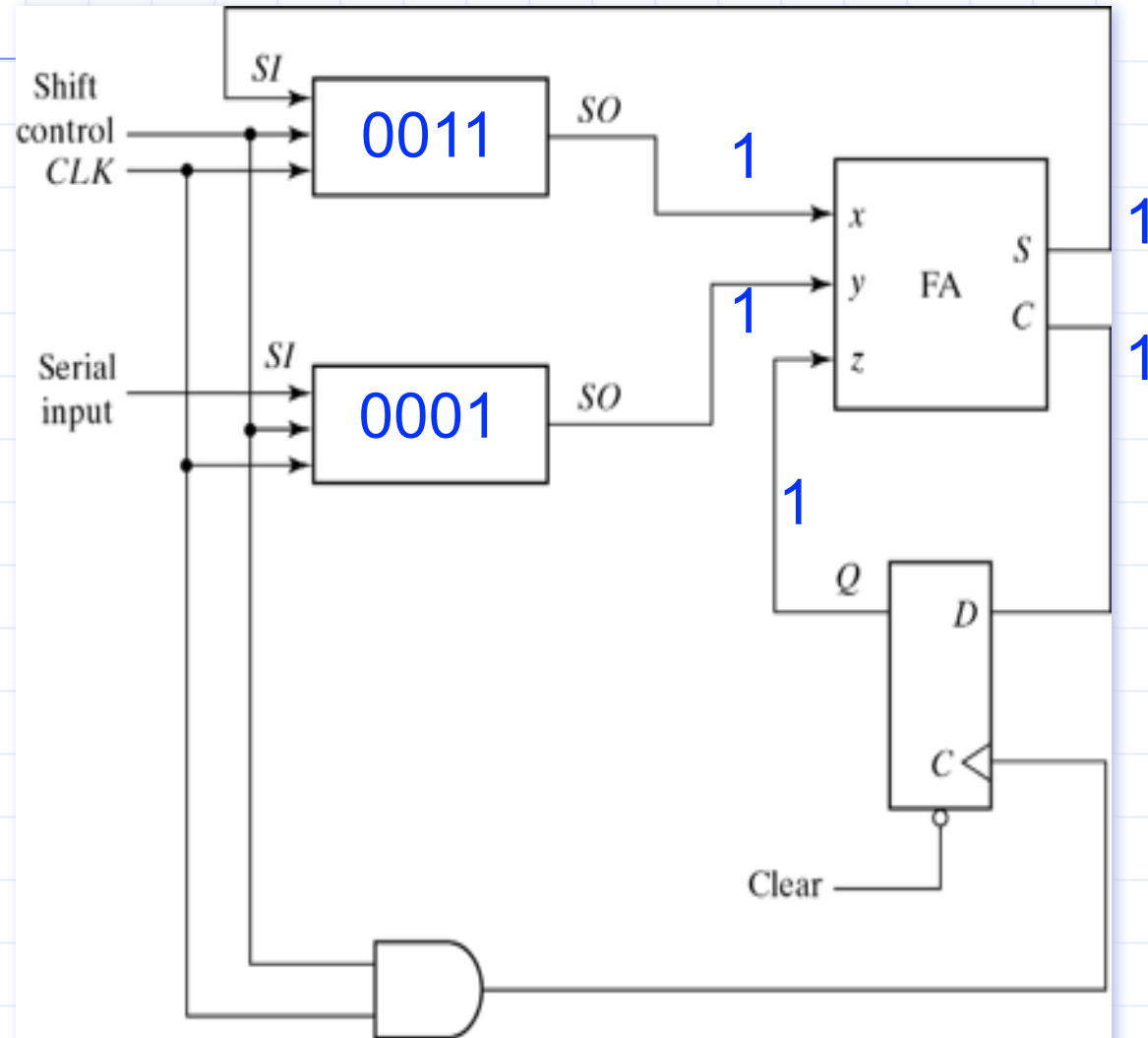


Fig. 6-5 Serial Adder

Serial Addition

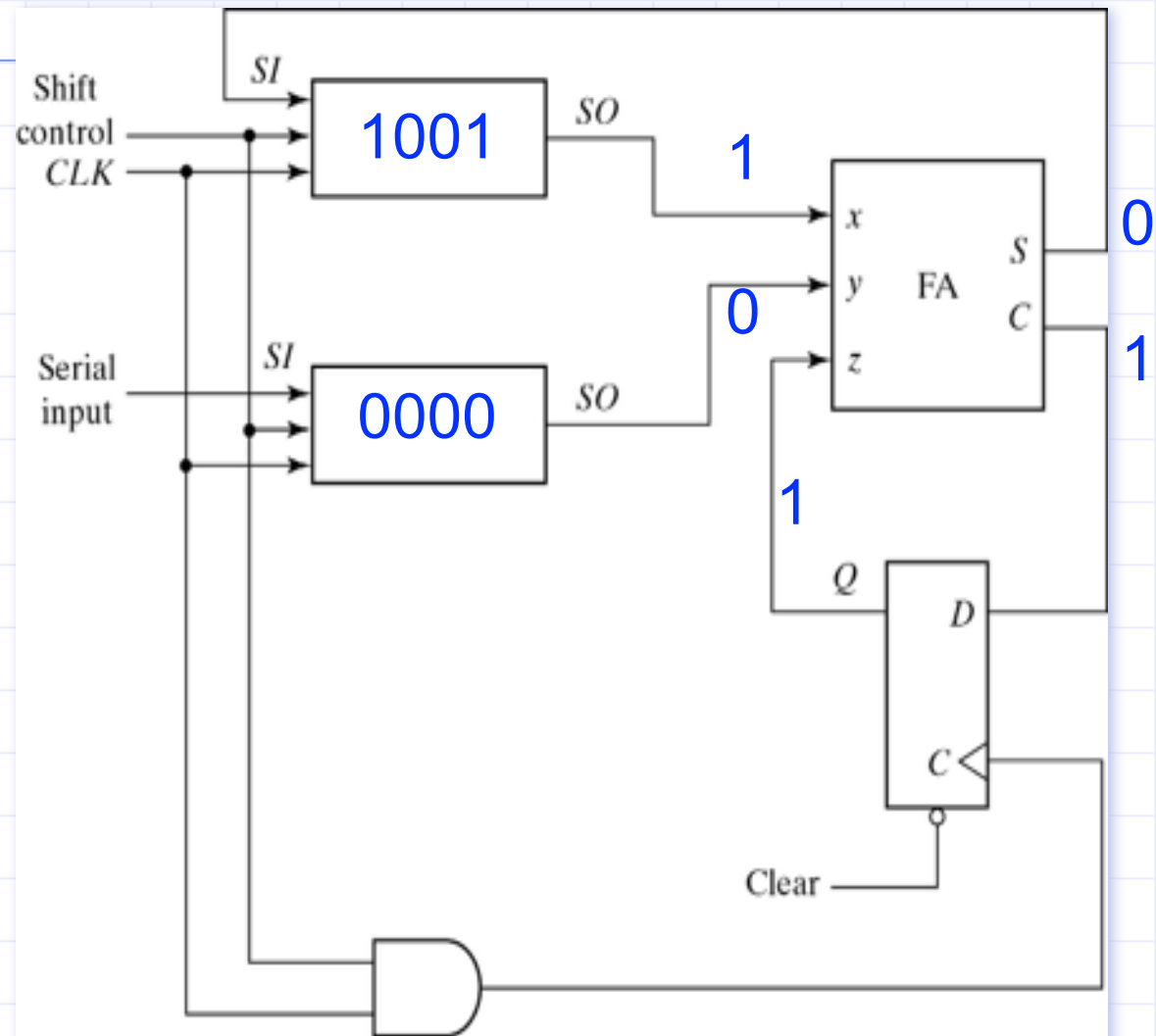


Fig. 6-5 Serial Adder

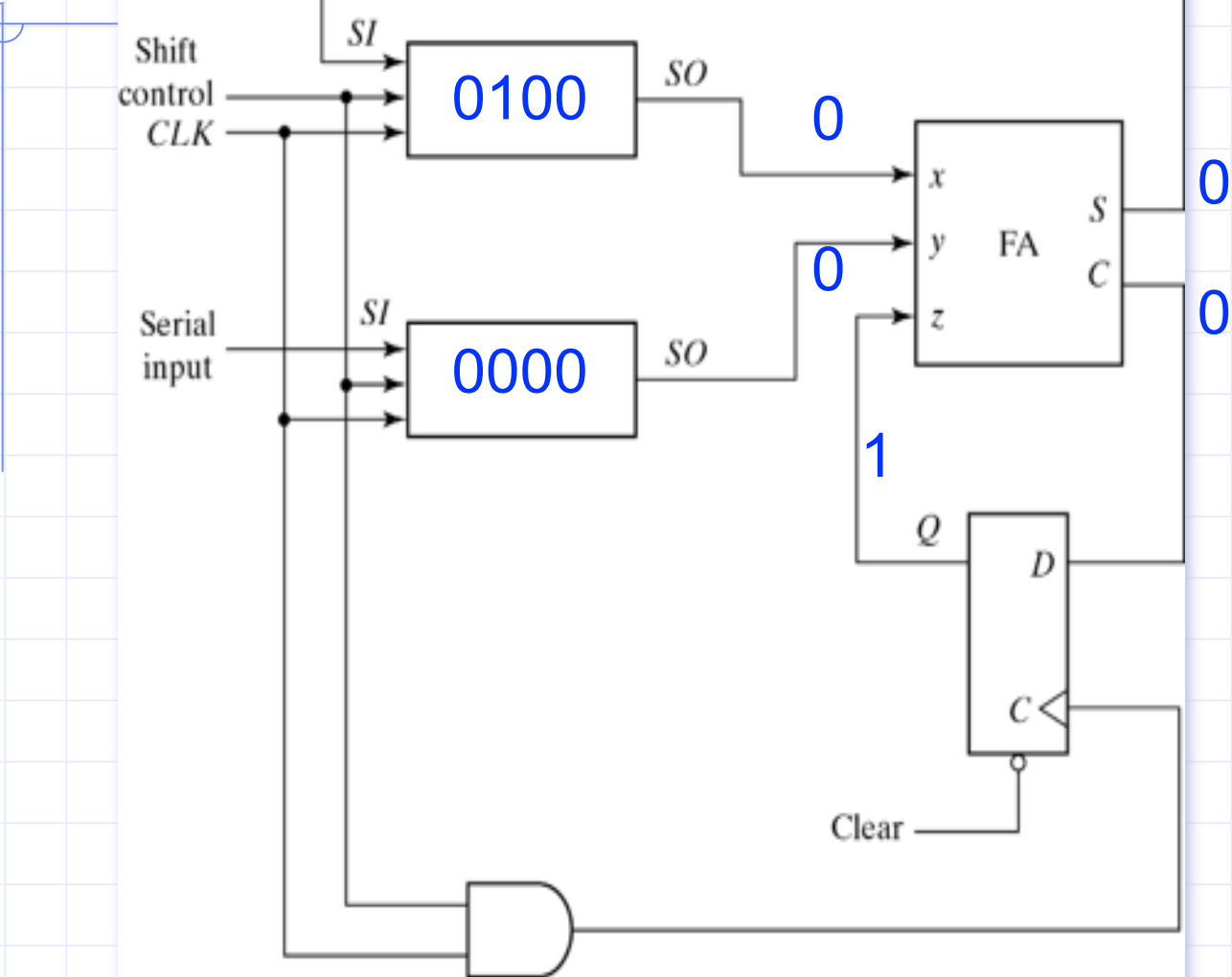


Fig. 6-5 Serial Adder

State Table for Serial Adder

Table 6-2
State Table for Serial Adder

Present State Q	Inputs $x \quad y$		Next State Q	Output S	Flip-Flop Inputs	
					J_Q	K_Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

By k-map

Second form of Serial Adder


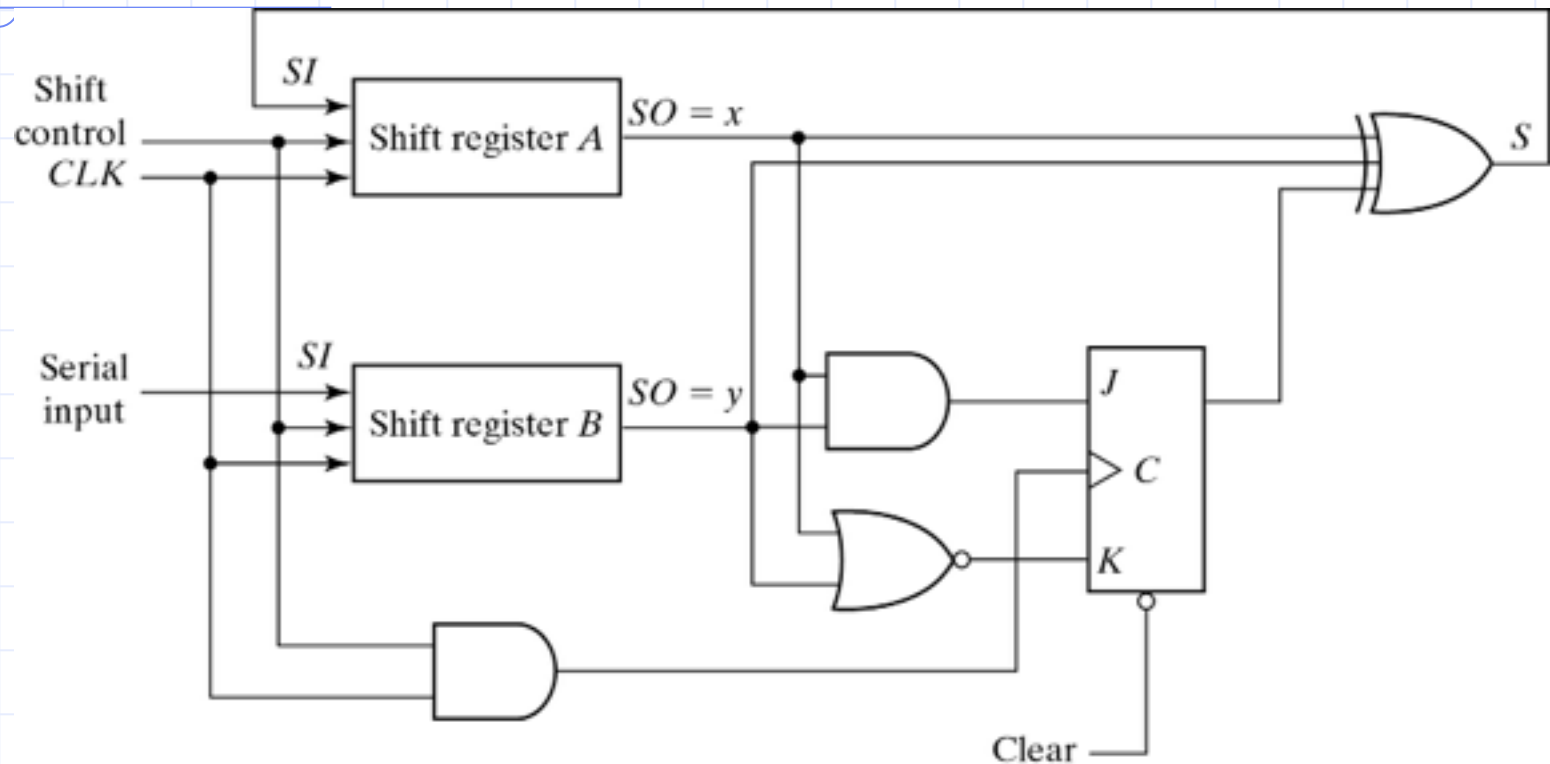


Fig. 6-6 Second form of Serial Adder


Universal Shift Register

 

□ $S_1, S_0 \rightarrow 0, 0$; No change

Fig. 6-7 4-Bit Universal Shift Register


Universal Shift Register

 

□ $S_1, S_0 \rightarrow 0, 1$; Shift right

Fig. 6-7 4-Bit Universal Shift Register


Universal Shift Register

 

□ $S_1, S_0 \rightarrow 1, 0$; Shift left

Fig. 6-7 4-Bit Universal Shift Register

Universal Shift Register

 

□ $S_1, S_0 \rightarrow 1, 1$; Parallel load

Fig. 6-7 4-Bit Universal Shift Register




(a) With T flip-flops


0000

Count: 1 \rightarrow 0,
A₀: 1 \rightarrow 0, A₁: 1 \rightarrow 0,
A₂: 1 \rightarrow 0, A₃: 1 \rightarrow 0

6-3 RIPPLE COUNTERS

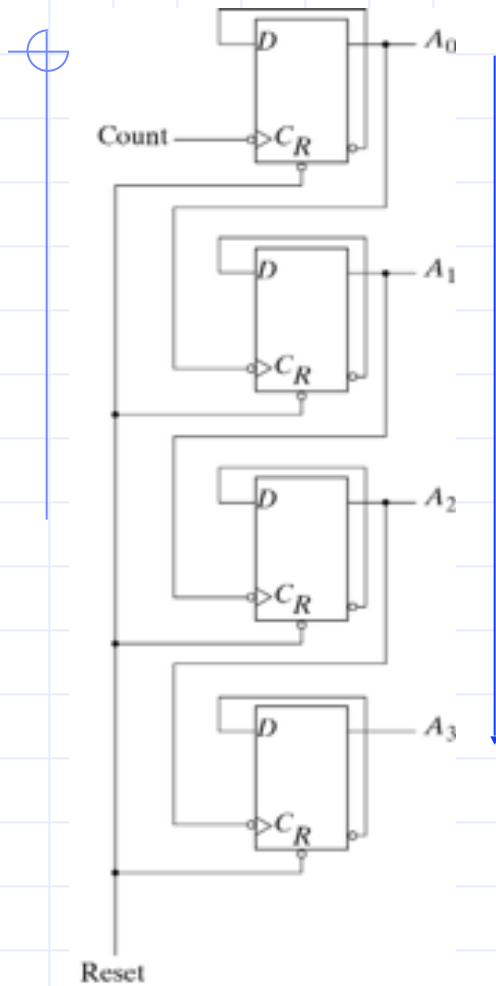

(b) With D flip-flops

 

Count sequence for a binary Counter

Count sequence A₃ A₂ A₁ A₀		Conditions for Complementing
0 0 0 0	Complement A ₀	
0 0 0 1	Complement A ₀	A ₀ will go from 1 to 0
0 0 1 0	Complement A ₀	and complement A ₁
0 0 1 1	Complement A ₀	A ₀ will go from 1 to 0
		and complement A ₁ ;
0 1 0 0	Complement A ₀	A ₁ will go from 1 to 0
0 1 0 1	Complement A ₀	and complement A ₂
0 1 1 0	Complement A ₀	A ₀ will go from 1 to 0
0 1 1 1	Complement A ₀	and complement A ₁
.....		
1 0 0 0	and so on...	

BCD Ripple Counter

Count: 1 -> 0

 


Fig. 6-9 State Diagram of a Decimal BCD-Counter


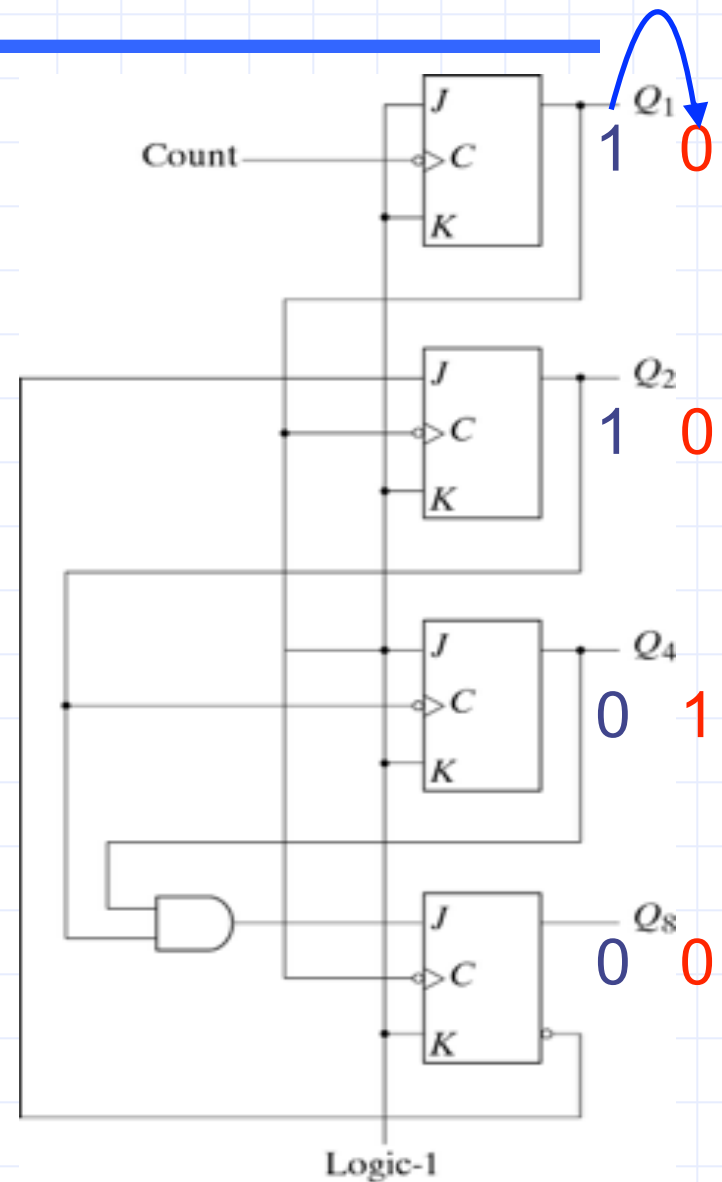


Fig. 6-10 BCD Ripple Counter

Count: 1 -> 0

 

BCD Ripple Counter

operation

1. Q_1 is complemented on the negative edge of every count pulse.
2. Q_2 is complemented if $Q_8=0$ and Q_1 goes from 1 to 0. Q_2 is cleared if $Q_8=1$ and Q_1 goes from 1 to 0.
3. Q_4 is complemented when Q_2 goes from 1 to 0.
4. Q_8 is complemented when $Q_4Q_2=11$ and Q_1 goes from 1 to 0. Q_8 is cleared if either Q_4 or Q_2 is 0 and Q_1 goes from 1 to 0

Three-Decade Decimal BCD Counter

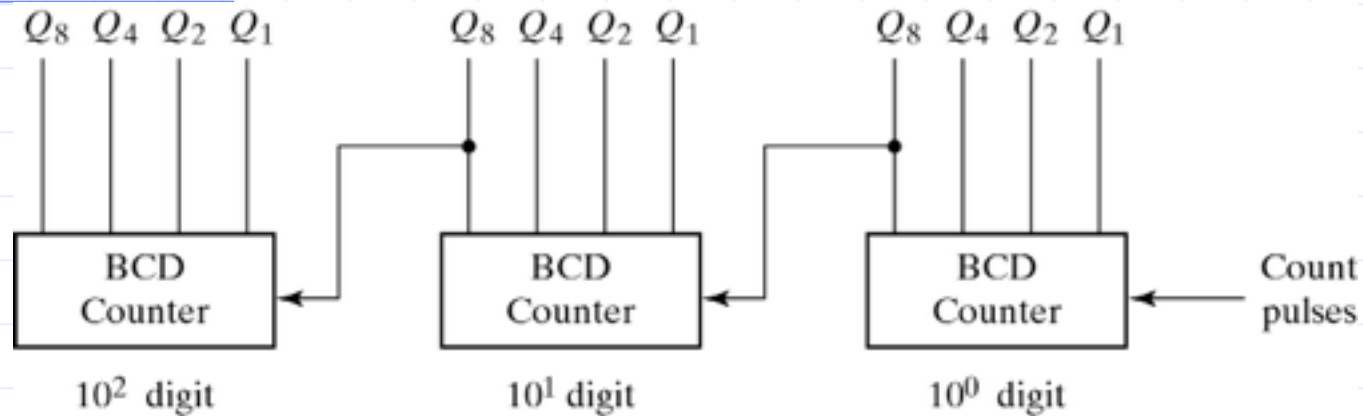


Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter

❑ To count from **0** to **999**, We need a three-decade counter.

6-4 SYNCHRONOUS COUNTERS


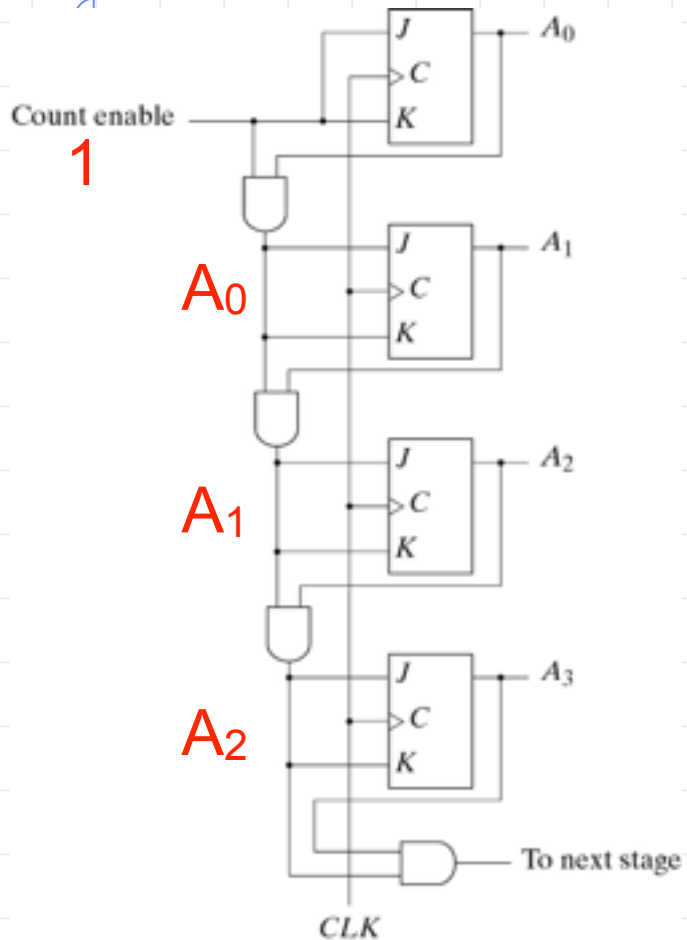


Fig. 6-12 4-Bit Synchronous Binary Counter

- ❑ The first stage A_0 has its **J** and **K** equal to **1** if the counter is enabled .
- ❑ The other **J** and **K** inputs are equal to **1** if all previous low-order bits are equal to **1** and the count is enabled.
- ❑ $A_0 = 1$ 이면, 클럭의 상승에지가 발생할 때 마다, A_1 의 값은 반전된다.

Up-Down Binary Counter

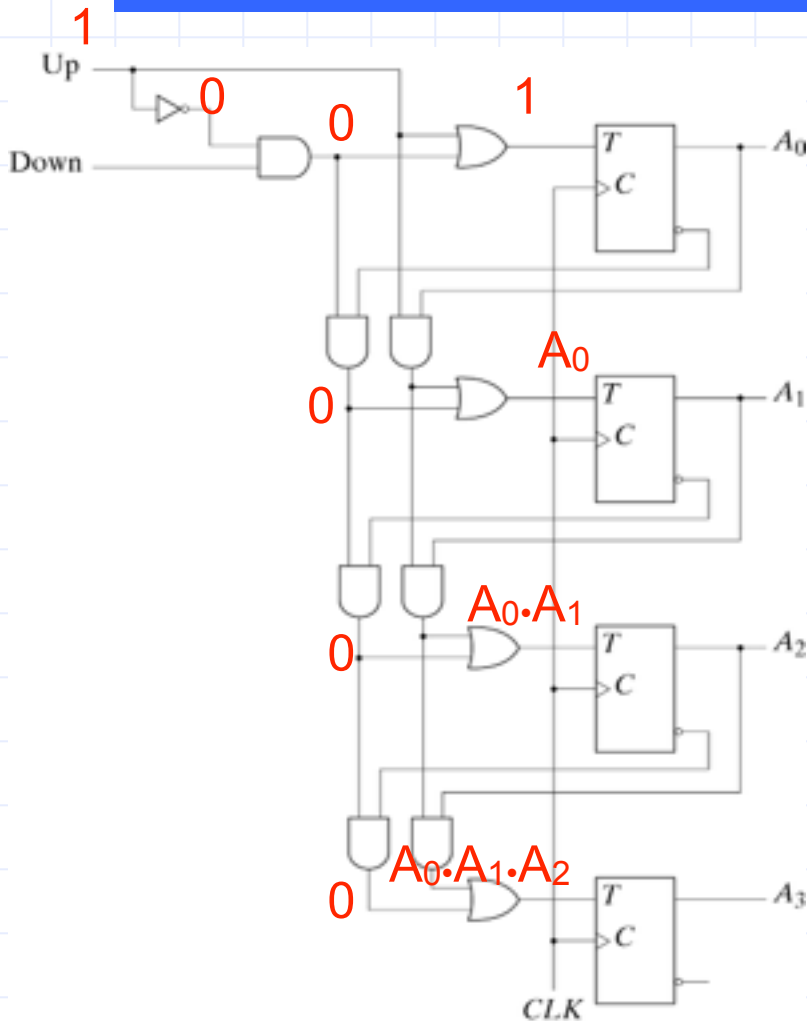


□ **Up** input control=**1** ;count up (the **T** inputs receive their signals from the values of the previous normal outputs of the flip-flops.)

0000
0001
0010
0011
0100

CLK: 0->1
CLK: 0->1
CLK: 0->1
CLK: 0->1
CLK: 0->1

Fig. 6-13 4-Bit Up-Down Binary Counter

0

 

CLK: 0->1


CLK: 0->1

CLK: 0->1

CLK: 0->1

34


Up-Down Binary Counter

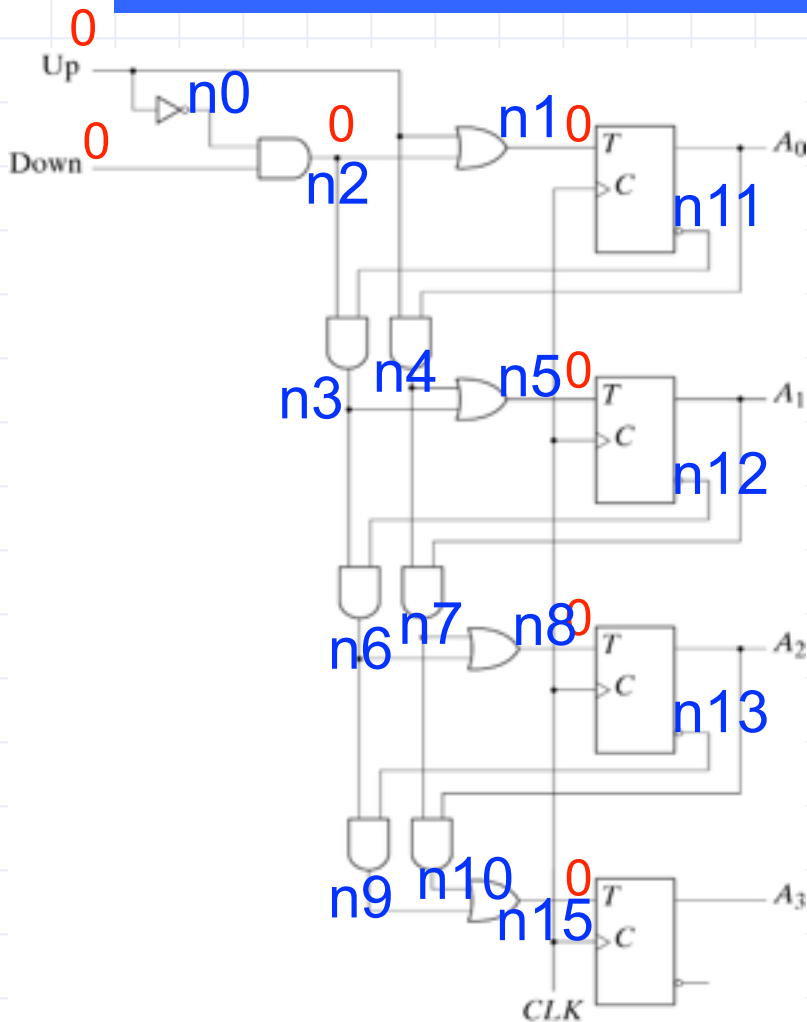

□ **Up=down=0** ; unchanged state

Fig. 6-13 4-Bit Up-Down Binary Counter

Up-Down Binary Counter

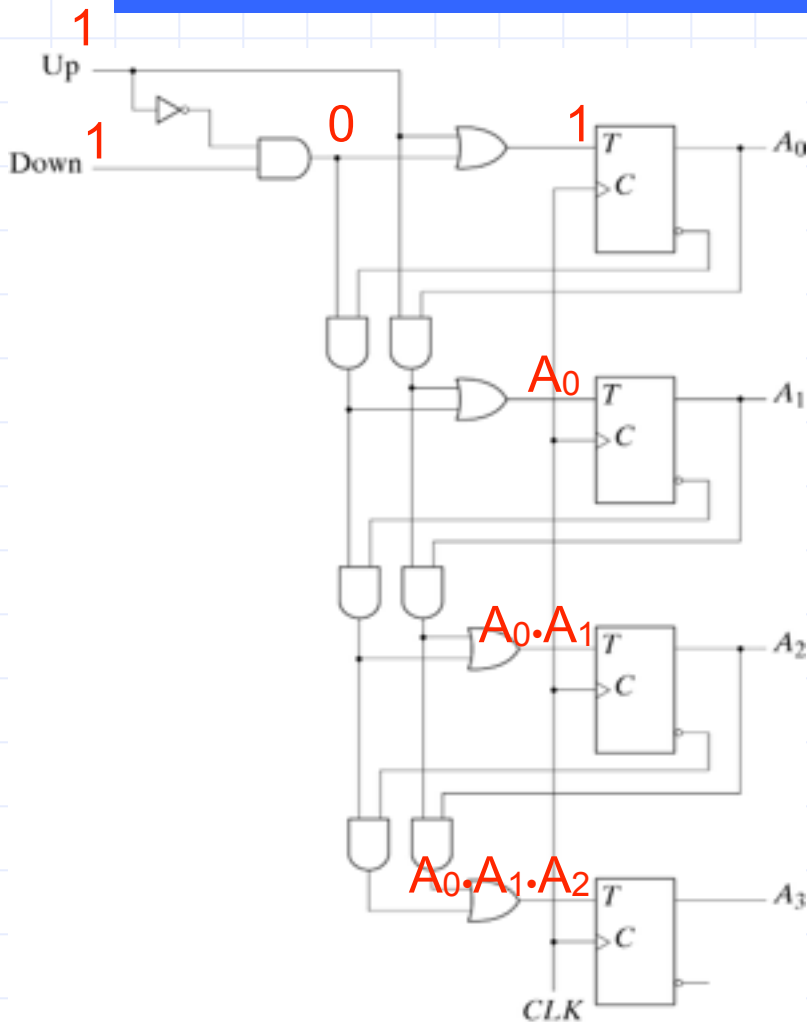

□ **Up=down=1** ;count up

Fig. 6-13 4-Bit Up-Down Binary Counter

BCD Counter

Table 6-5
State Table for BCD Counter

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

$$T_{Q1} = 1$$


$$T_{Q2} = Q'_8 Q_1$$

$$T_{Q4} = Q_2 Q_1$$

$$T_{Q8} = Q_8 Q_1 + Q_4 Q_2 Q_1$$

$$y = Q_8 Q_1$$

Binary Counter with Parallel Load

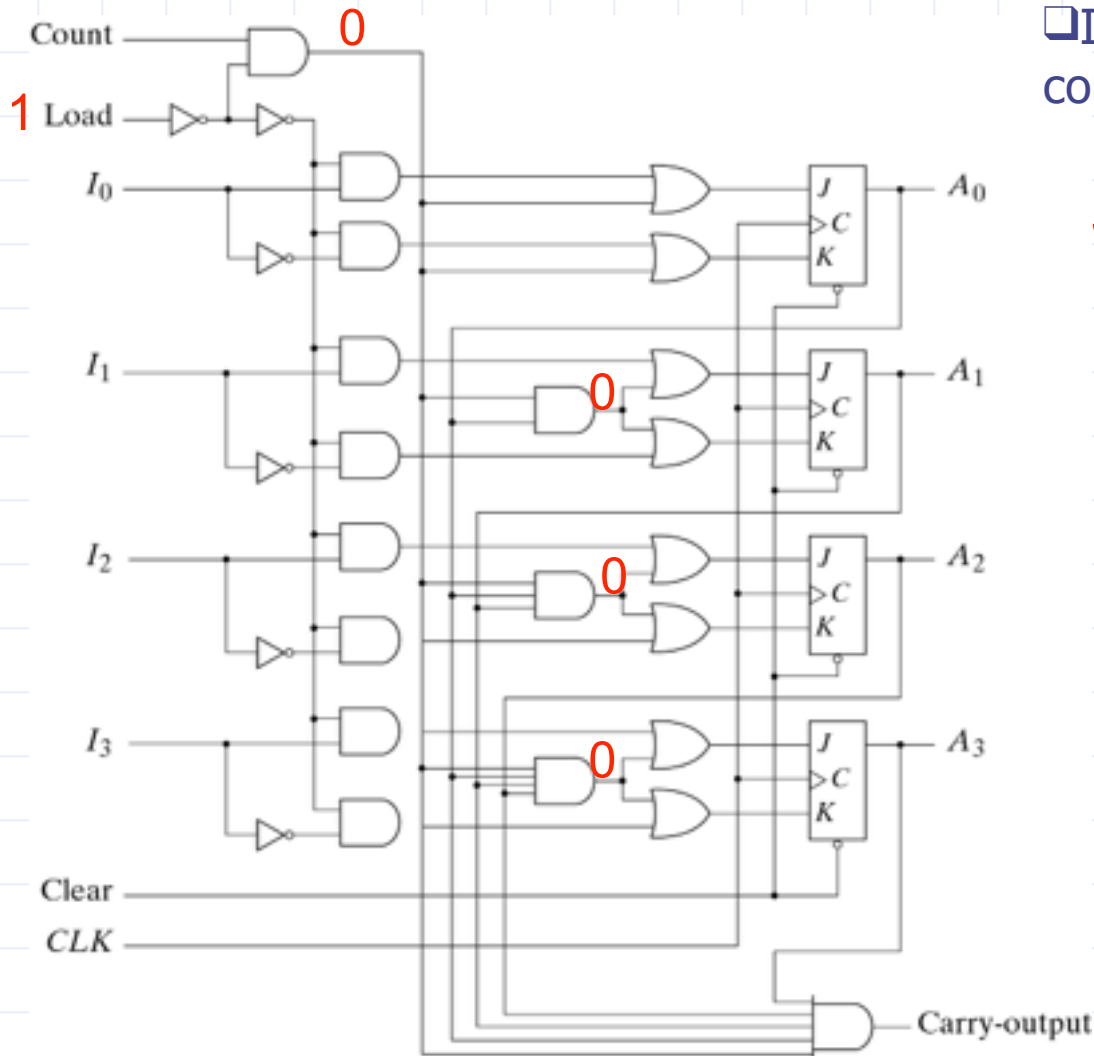

□ Input **load** control=1 ; disables the count sequence ,data transfer

$$J_i = I_i$$

$$K_i = \sim I_i$$

$$A_i = I_i$$

Fig. 6-14 4-Bit Binary Counter with Parallel Load

Binary Counter with Parallel Load

 


Fig. 6-14 4-Bit Binary Counter with Parallel Load

□ **Load** = 0 and **count** = 1 ; count

$$J_0 = 1$$

$$K_0 = 1$$

$$J_1 = A_0$$

$$K_1 = A_0$$

$$J_2 = A_0 \cdot A_1$$


$$K_2 = A_0 \cdot A_1$$

$$J_3 = A_0 \cdot A_1 \cdot A_2$$

$$K_3 = A_0 \cdot A_1 \cdot A_2$$



Binary Counter with Parallel Load

 


□ **Load=0** and **count=0** ; unchanged

$$J_i = 0$$

$$K_i = 0$$

Fig. 6-14 4-Bit Binary Counter with Parallel Load

Binary Counter with Parallel Load

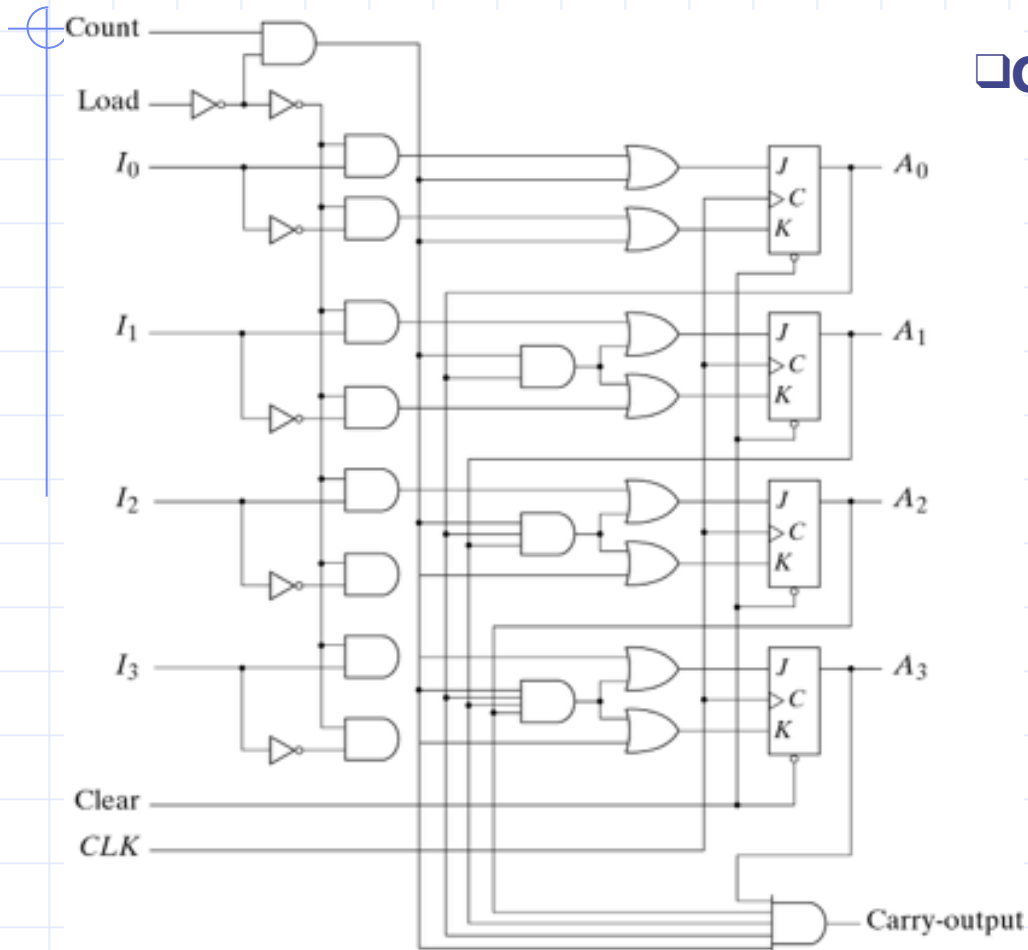

□ **Carry out=1**(all flip-flop=1)

Fig. 6-14 4-Bit Binary Counter with Parallel Load

BCD COUNTER using Binary Counter with Parallel Load

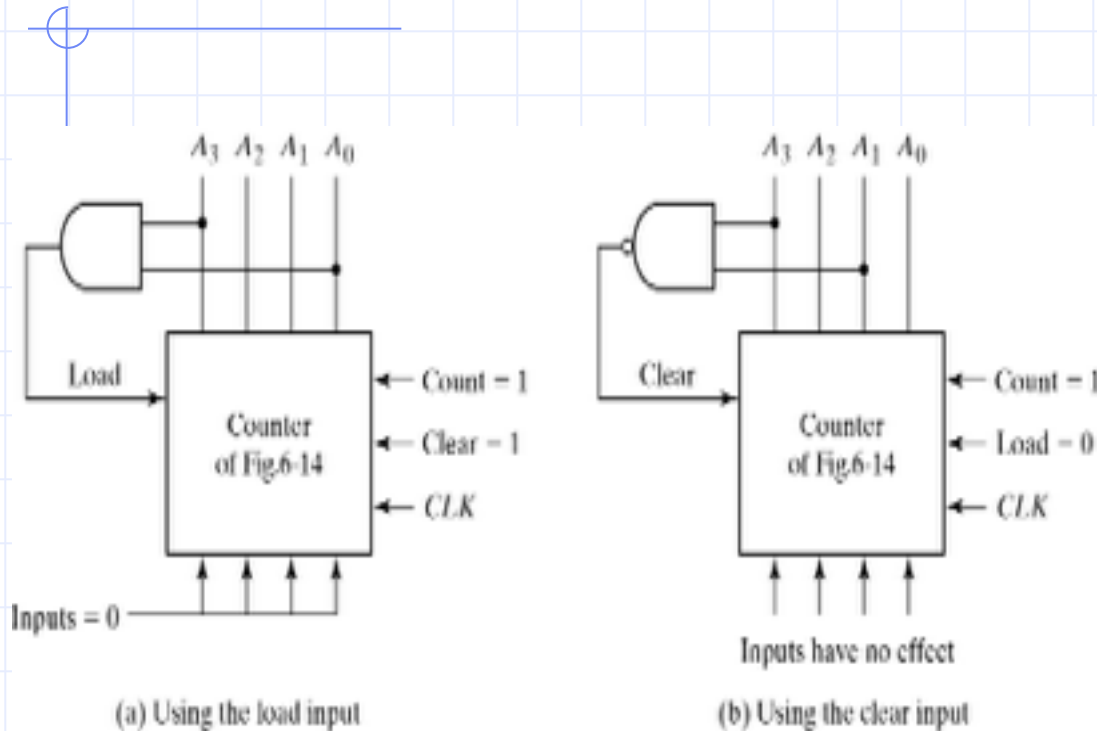



Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load

❑ The **AND** gate detects the occurrence of state **1001(9)** in the output. In this state, the load input is enabled and all-**0**'s input is loaded into register.

❑ The **NAND** gate detects the count of **1010(10)**, as soon as this count occurs the register is **cleared**.

❑ A momentary **spike** occurs in output A_2 as the count goes from **1001** to **1010** and immediately to **0000**

6-5 OTHER COUNTERS

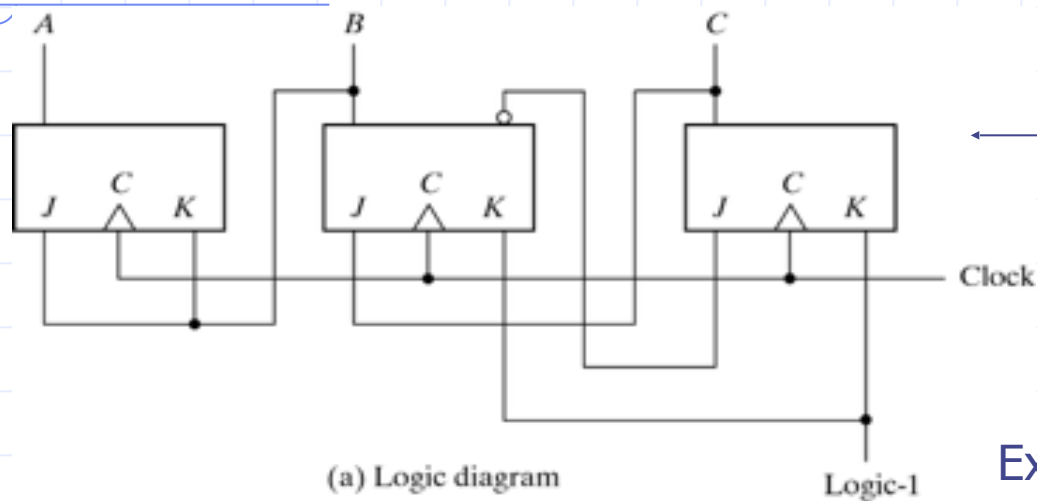

$$\begin{aligned} J_A &= B & K_A &= B \\ J_B &= C & K_B &= 1 \\ J_C &= B' & K_C &= 1 \end{aligned}$$

Except **011, 111**

 


Fig. 6-16 Counter with Unused States

Table 6-7
State Table for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

Ring Counter


 
 


Fig. 6-17 Generation of Timing Signals

- ❑ A circular shift register with only one flip-flop being set at any **particular time**. ; all others are cleared.
- ❑ **The single bit** is shifted from one flip-flop to the other.

Johnson Counter

 

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$


(b) Count sequence and required decoding

Fig. 6-18 Construction of a Johnson Counter

□ A circular shift register with **the complement output of the last flip-flop** connected to the input of the first flip-flop.

D Flip-Flop
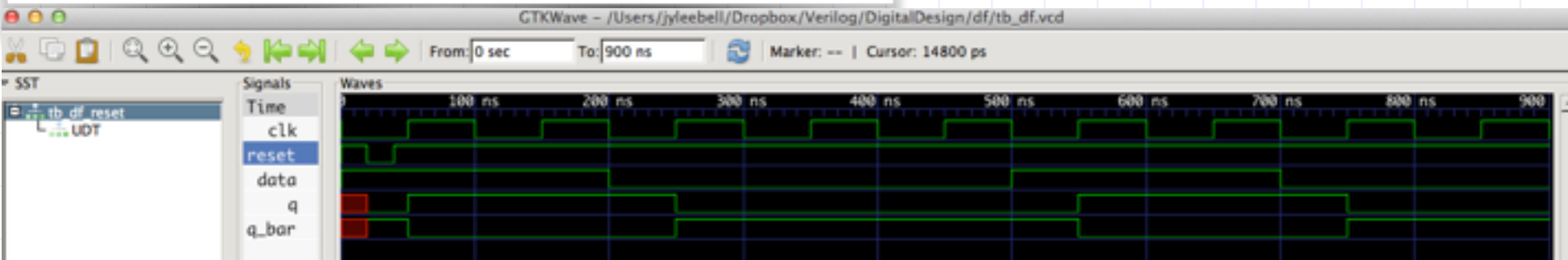
```
module df_reset (q, q_bar, data, reset, clk);  
    output q, q_bar;  
    input data, reset;  
    input clk;  
  
    reg q;  
  
    assign q_bar = ~q;  
  
    always @(posedge clk or negedge reset) begin  
        if (reset == 0) q <= 0;  
        else q <= data;  
    end  
endmodule
```



6-1 REGISTERS

 


Fig. 6-1 4-Bit Register

```

module reg4_behav (A_b, I, Clear, Clock);
    output [3:0] A_b;
    input [3:0] I;
    input Clear, Clock;

    reg [3:0] A_b;

    always @(posedge Clock or negedge Clear) begin
        if (Clear == 0) A_b <= 4'b0000;
        else A_b <= I;
    end
endmodule

module reg4_str (A_s, I, Clear, Clock);
    output [3:0] A_s;
    input [3:0] I;
    input Clear, Clock;

    df_reset FF0 (.q(A_s[0]), .data(I[0]), .reset(Clear), .clk(Clock));
    df_reset FF1 (.q(A_s[1]), .data(I[1]), .reset(Clear), .clk(Clock));
    df_reset FF2 (.q(A_s[2]), .data(I[2]), .reset(Clear), .clk(Clock));
    df_reset FF3 (.q(A_s[3]), .data(I[3]), .reset(Clear), .clk(Clock));
endmodule
    
```

6-1 REGISTERS

```
module tb_reg4;
  reg clk, reset;
  reg [3:0] I;


  wire [3:0] A_b, A_s;

  reg4_behav UDT0 (.A_b(A_b), .I(I), .Clear(reset), .Clock(clk));
  reg4_str UDT1 (.A_s(A_s), .I(I), .Clear(reset), .Clock(clk));

  initial begin
    clk = 0;
    I = 0;
    reset = 1;
    #20 reset = 0;
    #20 reset = 1;
  end

  always #50 clk = ~clk;

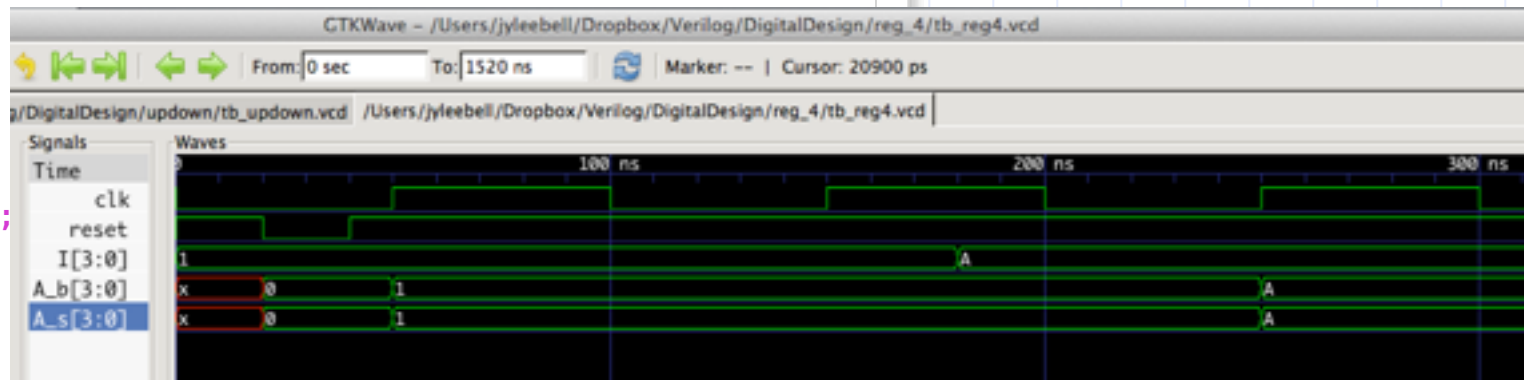  initial begin
    I = 1;
    #180 I = 10;
    #180 I = 11;
    #200 I = 8;
    #20 reset = 0;
    #200 reset = 1;
    #180 I = 2;
    #180 I = 3;
    #200 I = 4;
    #180 $finish;
  end
endmodule
```



Register with Parallel Load

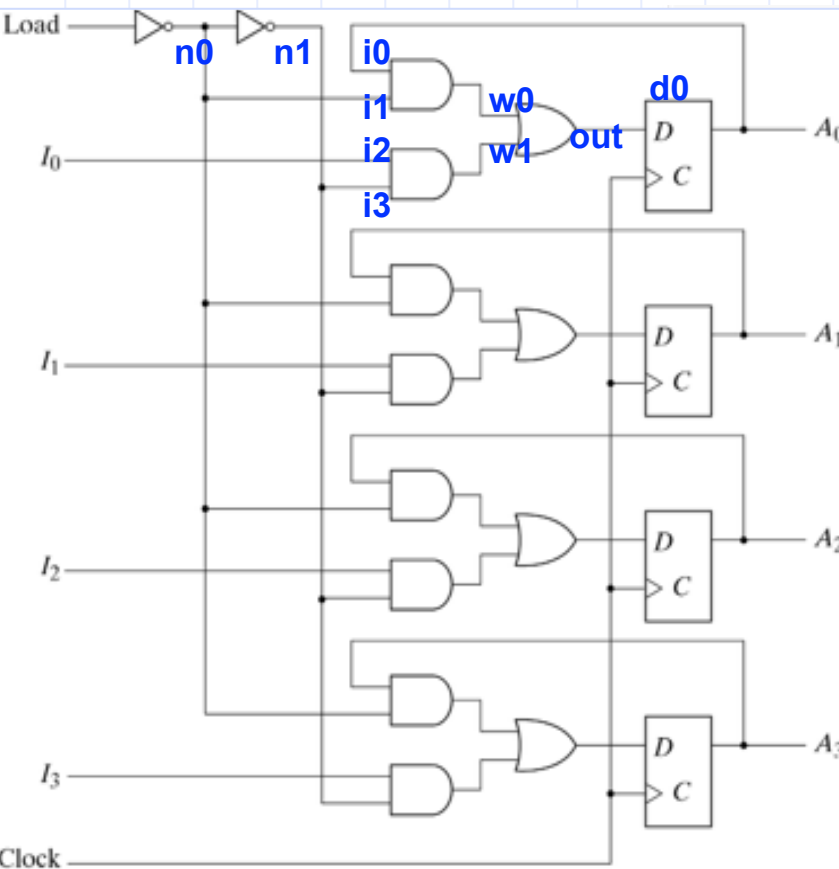


Fig. 6-2 4-Bit Register with Parallel Load

```
module and_or (i0, i1, i2, i3, out);
input i0, i1, i2, i3;
output out;

wire w0, w1;

and AND0 (w0, i0, i1);
and AND1 (w1, i2, i3);
or OR0 (out, w0, w1);
endmodule

module reg4_pl_str (A_s, I, Load, Clock);
output [3:0] A_s;
input [3:0] I;
input Clock, Load;

wire d0, d1, d2, d3;
wire n0, n1;

not U0 (n0, Load);
not U1 (n1, n0);
and_or U2 (A_s[0], n0, I[0], n1, d0);
and_or U3 (A_s[1], n0, I[1], n1, d1);
and_or U4 (A_s[2], n0, I[2], n1, d2);
and_or U5 (A_s[3], n0, I[3], n1, d3);
```

```
df_reset FF0 (.q(A_s[0]), .data(d0), .reset(1'b1), .clk(Clock));
df_reset FF1 (.q(A_s[1]), .data(d1), .reset(1'b1), .clk(Clock));
df_reset FF2 (.q(A_s[2]), .data(d2), .reset(1'b1), .clk(Clock));
df_reset FF3 (.q(A_s[3]), .data(d3), .reset(1'b1), .clk(Clock));
endmodule
```

Register with Parallel Load

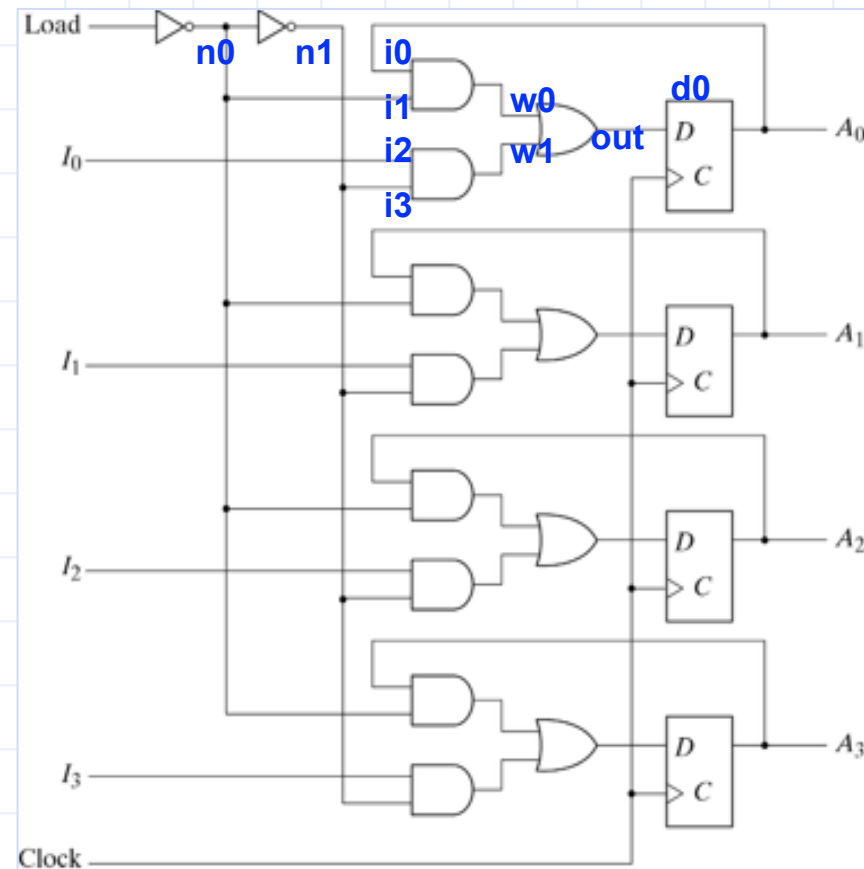


Fig. 6-2 4-Bit Register with Parallel Load

```
module reg4_pl_behav (A_b, I, Load, Clock);  
    output [3:0] A_b;  
    input [3:0] I;  
    input Load, Clock;  
  
    reg [3:0] A_b;  
  
    always @(posedge Clock) begin  
        if (Load == 1) begin  
            A_b <= I;  
        end  
        else begin  
            A_b <= A_b;  
        end  
    end  
endmodule
```

Register with Parallel Load

```
module tb_reg4_pl;
  reg clk, load;
  reg [3:0] I;



  wire [3:0] A_b, A_s;

  reg4_pl_behav UDT0 (.A_b(A_b), .I(I), .Load(load), .Clock(clk));
  reg4_pl_str UDT1 (.A_s(A_s), .I(I), .Load(load), .Clock(clk));

  initial begin
    clk = 0;
    I = 0;
    load = 0;
    #6 load = 1;
  end

  always #50 clk = ~clk;

 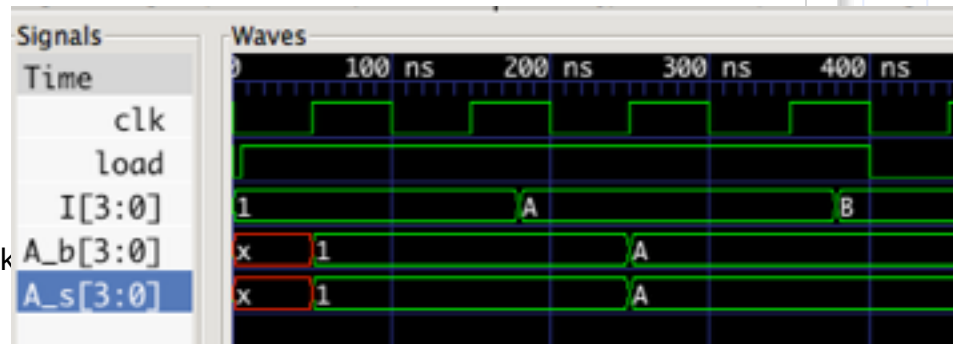  initial begin
    I = 1;
    #180 I = 10;
    #20 load = 1;
    #180 I = 11;
    #20 load = 0;
    #200 I = 8;
    #20 load = 0;
    #200 load = 1;
    #180 I = 2;
    #180 I = 3;
    #200 I = 4;
    #180 $finish;
  end
end
endmodule
```



6-2 SHIFT REGISTERS

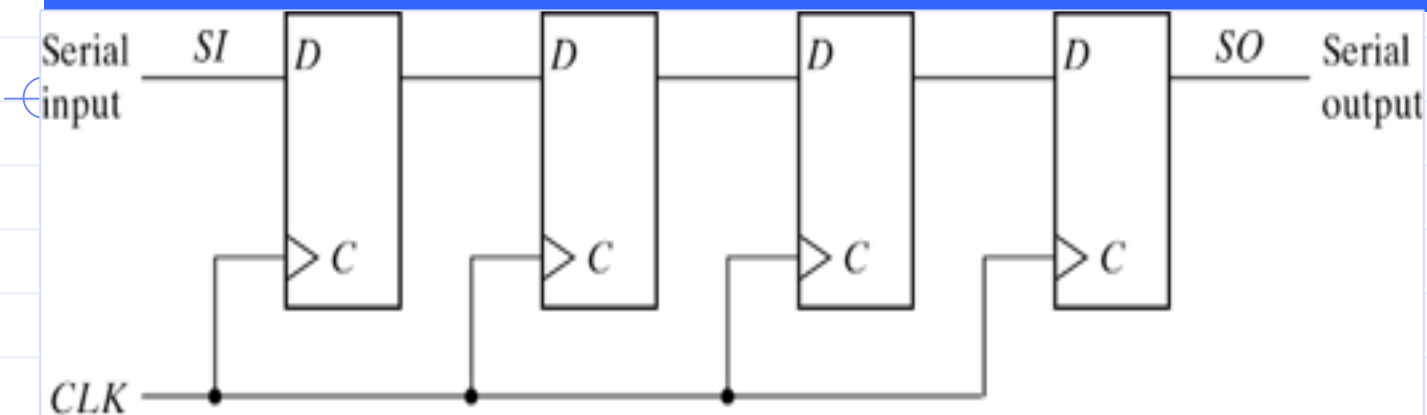


Fig. 6-3 4-Bit Shift Register

```
module shift_reg4_str (si, so, clock, r);  
    output    so;  
    output    [0:3] r;  
    input     si;  
    input     clock;  
  
    wire d1, d2, d3;  
  
    df_reset FF0 (.q(d1), .data(si), .reset(1'b1), .clk(clock));  
    df_reset FF1 (.q(d2), .data(d1), .reset(1'b1), .clk(clock));  
    df_reset FF2 (.q(d3), .data(d2), .reset(1'b1), .clk(clock));  
    df_reset FF3 (.q(so), .data(d3), .reset(1'b1), .clk(clock));  
  
    assign r = {d1, d2, d3, so};  
  
endmodule
```

6-2 SHIFT REGISTERS

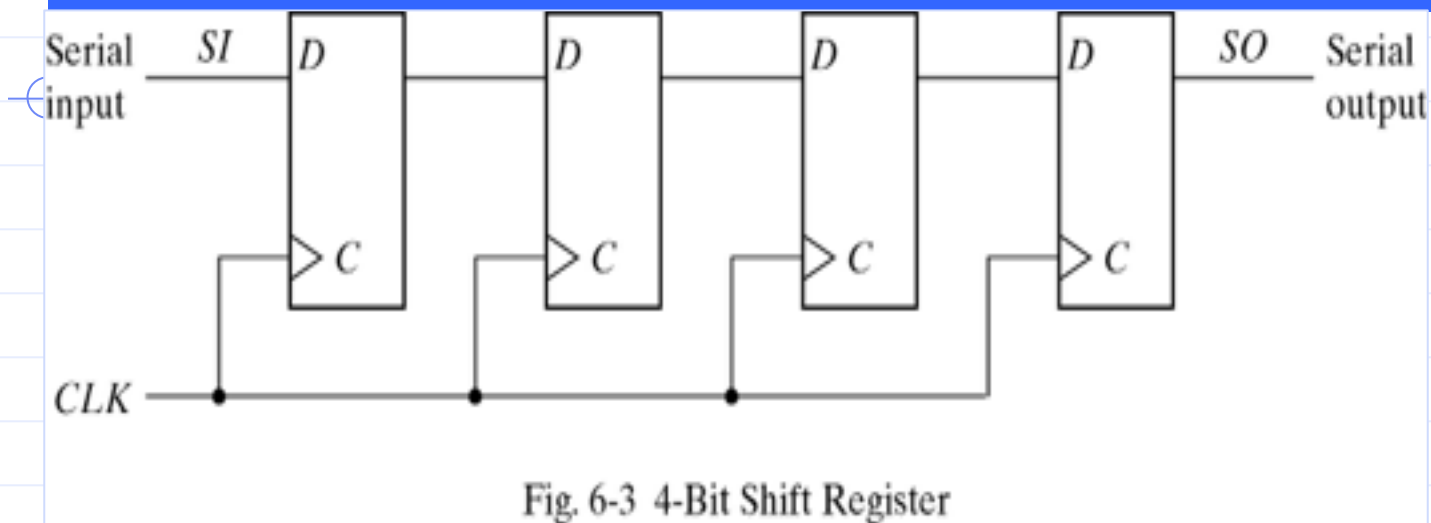


Fig. 6-3 4-Bit Shift Register

```
module shift_reg4_behav (si, so, clock, r);  
    output    so;  
    output    [0:3] r;  
    input     si;  
    input     clock;  
  
    reg [0:3] R;  
    wire      so;  
  
    always @(posedge clock) begin  
        R <= {si, R[0:2]} ;  
    end  
  
    assign so = R[3];  
    assign r = R;  
endmodule
```


6-2 SHIFT REGISTERS

```
module tb_shift_reg4;
  wire so_behav, so_str;
  wire [0:3] r_b, r_s;
  reg clk, si;

  shift_reg4_behav UDT0 (.si(si), .so(so_behav), .clock(clk), .r(r_b));
  shift_reg4_str UDT1 (.si(si), .so(so_str), .clock(clk), .r(r_s));
  initial begin
    clk = 0;
    si = 0;
  end
```


```
  always #50 clk = ~clk;
```

```
  initial begin
```

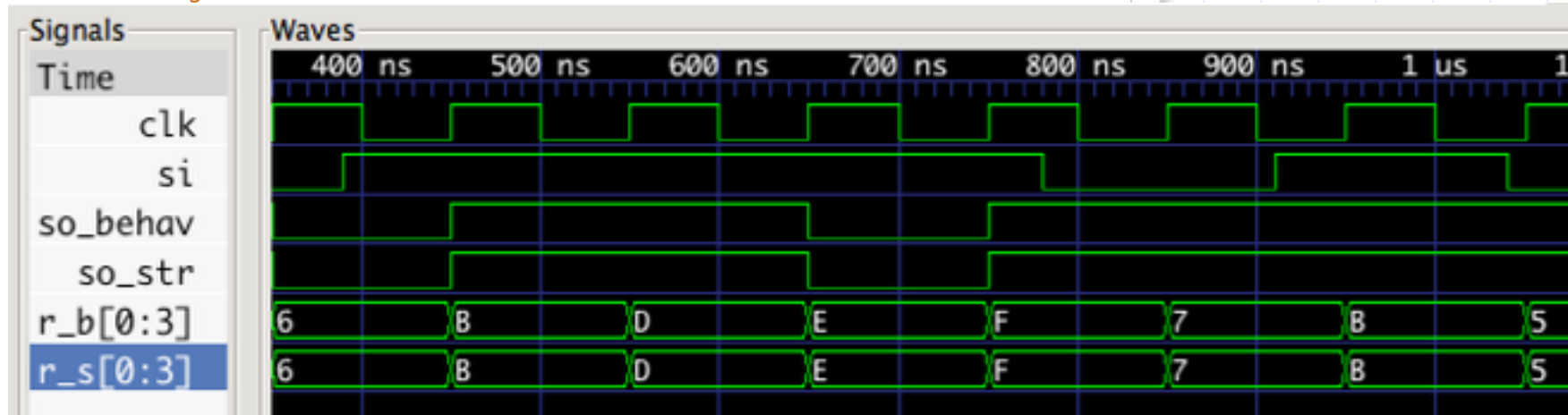

```
    #180 $TINISH;
  end
endmodule
```

Universal Shift Register

 

```

module mux4x1(out, d3, d2, d1, d0, s1, s0);
    output out;
    input d0, d1, d2, d3;
    input s1, s0;


    reg out;

    always @* begin
        case ({s1, s0})
            0: out <= d0;
            1: out <= d1;
            2: out <= d2;
            3: out <= d3;
            default: out <= 1'bx;
        endcase
    end
endmodule

```

Fig. 6-7 4-Bit Universal Shift Register

Universal Shift Register

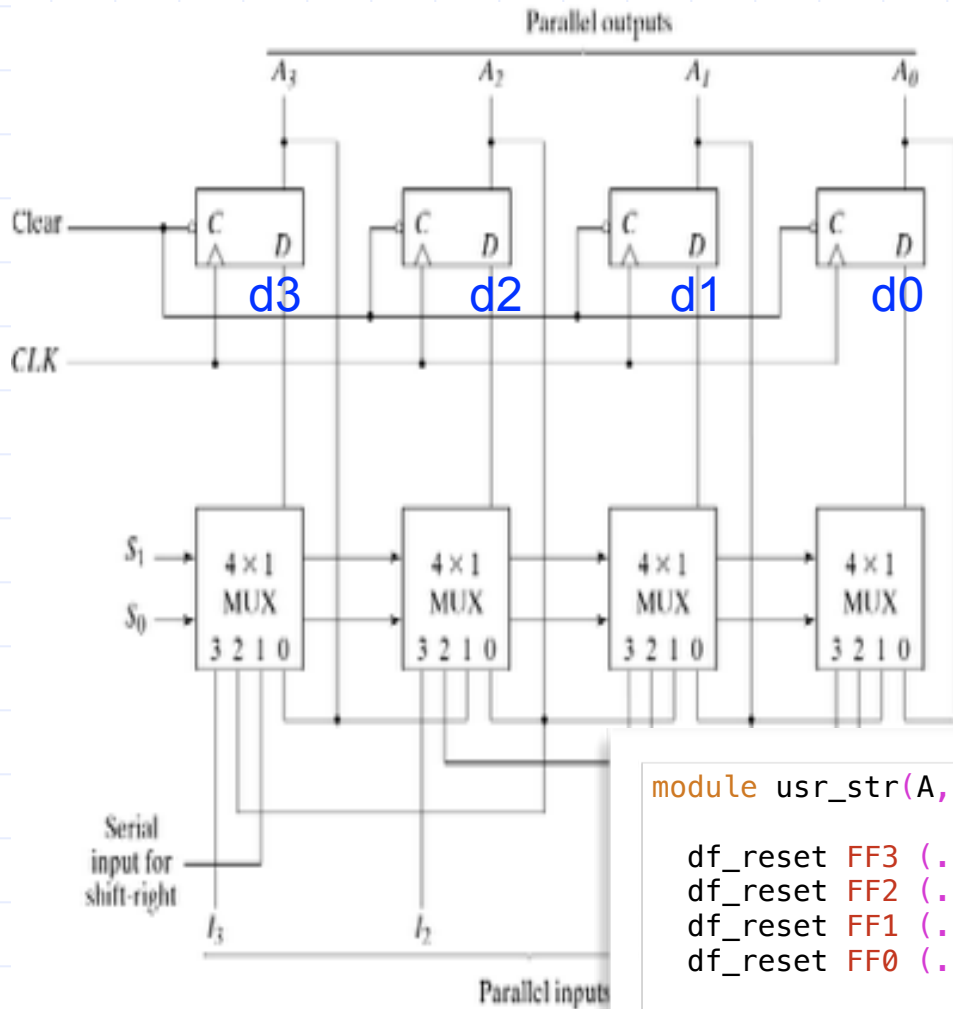


```
module usr_str(A, I, sir, sil, control, clear, clock);
```

```
    df_reset FF3 (.q(A[3]), .data(d3), .reset(clear), .clk(clock));
    df_reset FF2 (.q(A[2]), .data(d2), .reset(clear), .clk(clock));
    df_reset FF1 (.q(A[1]), .data(d1), .reset(clear), .clk(clock));
    df_reset FF0 (.q(A[0]), .data(d0), .reset(clear), .clk(clock));
```

```
endmodule
```

Fig. 6-7 4-Bit Universal Shift


Universal Shift Register

 

```

mux4x1 MUX3 (.out(d3), .d3(I[3]), .d2(A[2]), .d1(sir), .d0(A[3]), .s1(control[1]), .s0(control[0]));
mux4x1 MUX2 (.out(d2), .d3(I[2]), .d2(A[1]), .d1(A[3]), .d0(A[2]), .s1(control[1]), .s0(control[0]));
mux4x1 MUX1 (.out(d1), .d3(I[1]), .d2(A[0]), .d1(A[2]), .d0(A[1]), .s1(control[1]), .s0(control[0]));
mux4x1 MUX0 (.out(d0), .d3(I[0]), .d2(A[sil]), .d1(A[1]), .d0(A[0]), .s1(control[1]), .s0(control[0]));
    
```

Universal Shift Register

 

```

mux4x1 MUX3 (.out(d3), .d3(I[3]), .d2(A[2]), .d1(sir), .d0(A[3]), .s1(control[1]), .s0(control[0]));
mux4x1 MUX2 (.out(d2), .d3(I[2]), .d2(A[1]), .d1(A[3]), .d0(A[2]), .s1(control[1]), .s0(control[0]));
mux4x1 MUX1 (.out(d1), .d3(I[1]), .d2(A[0]), .d1(A[2]), .d0(A[1]), .s1(control[1]), .s0(control[0]));
mux4x1 MUX0 (.out(d0), .d3(I[0]), .d2(A[sil]), .d1(A[1]), .d0(A[0]), .s1(control[1]), .s0(control[0]));
    
```

Universal Shift Register

 


Fig. 6-7 4-Bit Universal Shift Register

```

module usr_behav(A, I, sir, sil, control, clear, clock);
    output [3:0] A;
    input [3:0] I;
    input [1:0] control;
    input sir, sil, clear, clock;

    wire d3, d2, d1, d0;
    reg [3:0] A;
    wire [3:0] I;

    always @(posedge clock or negedge clear) begin
        if (clear == 0) begin
            A <= 4'b0000;
        end begin
            case (control)
                0: A <= A;
                1: A <= {sir, A[3:1]};
                2: A <= {A[2:0], sil};
                3: A <= I;
            endcase
        end
    end

endmodule

```

Universal Shift Register

```
module tb_usr;
  reg  [3:0]  I;
  reg  sil, sir, clear, clock;
  reg  [1:0]  control;
  wire  [3:0] A_s, A_b;


  usr_str DUT0 (.A(A_s), .I(I), .sir(sir), .sil(sil), .control(control), .clear(clear), .clock(clock));
  usr_behav DUT1 (.A(A_b), .I(I), .sir(sir), .sil(sil), .control(control), .clear(clear), .clock(clock));

  initial begin
    I = 0; sil = 0; sir = 0; clear = 0; clock = 0; control = 0;


    #100 I = 4'b0011; control = 3; sil = 1; sir = 0; clear = 1;
    #100 control = 1;

    #100 I = 4'b0110; control = 3; sil = 0; sir = 1;
    #100 control = 2;

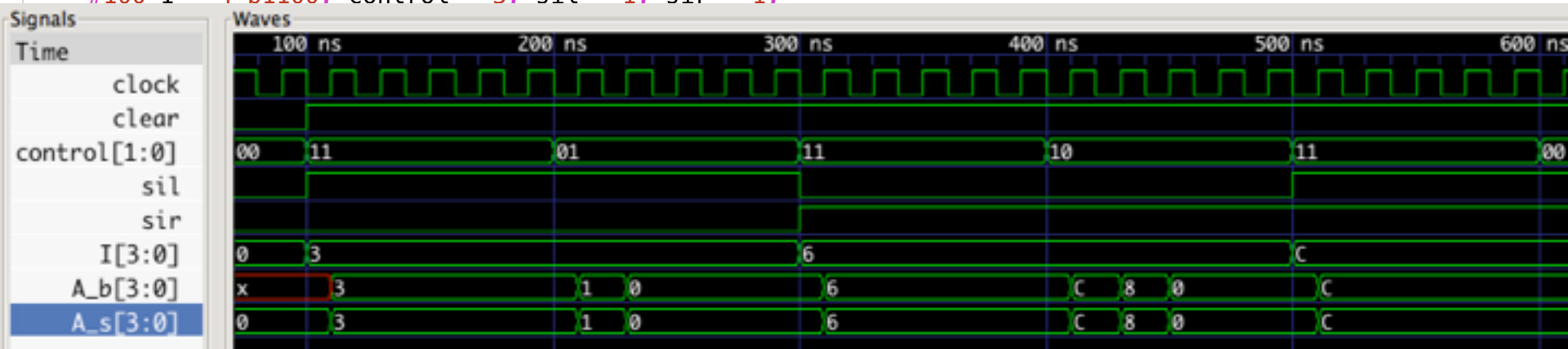    #100 I = 4'b1100; control = 3; sil = 1; sir = 1;
```



6-3 RIPPLE COUNTERS

 

(b) With D flip-flops

```
module df_reset (q, q_bar, data, reset, clk);
    output q, q_bar;
    input data, reset;
    input clk;
```

```
    reg q;
```

```
    assign q_bar = ~q;
```

```
    always @(negedge clk or negedge reset) begin
        if (reset == 0) q <= 0;
        else q <= data;
```

```
    end
```

```
endmodule
```

```
module ripple_counter_str (A, reset, count);
    output [3:0] A;
    input reset, count;
```

```
    wire d3, d2, d1, d0;
    wire [3:0] A;
```

```
    df_reset FF0 (.q(A[0]), .q_bar(d0), .data(d0), .reset(reset), .clk(count));
    df_reset FF1 (.q(A[1]), .q_bar(d1), .data(d1), .reset(reset), .clk(A[0]));
    df_reset FF2 (.q(A[2]), .q_bar(d2), .data(d2), .reset(reset), .clk(A[1]));
    df_reset FF3 (.q(A[3]), .q_bar(d3), .data(d3), .reset(reset), .clk(A[2]));
```


```
endmodule
```

6-3 RIPPLE COUNTERS

```
module tb_ripple;
  reg    count, reset;
  wire   [3:0] A_s, A_b;

  ripple_counter_str DUT_S (.A(A_s), .reset(reset), .count(count));
  ripple_counter_behav DUT_B (.A(A_b), .reset(reset), .count(count));

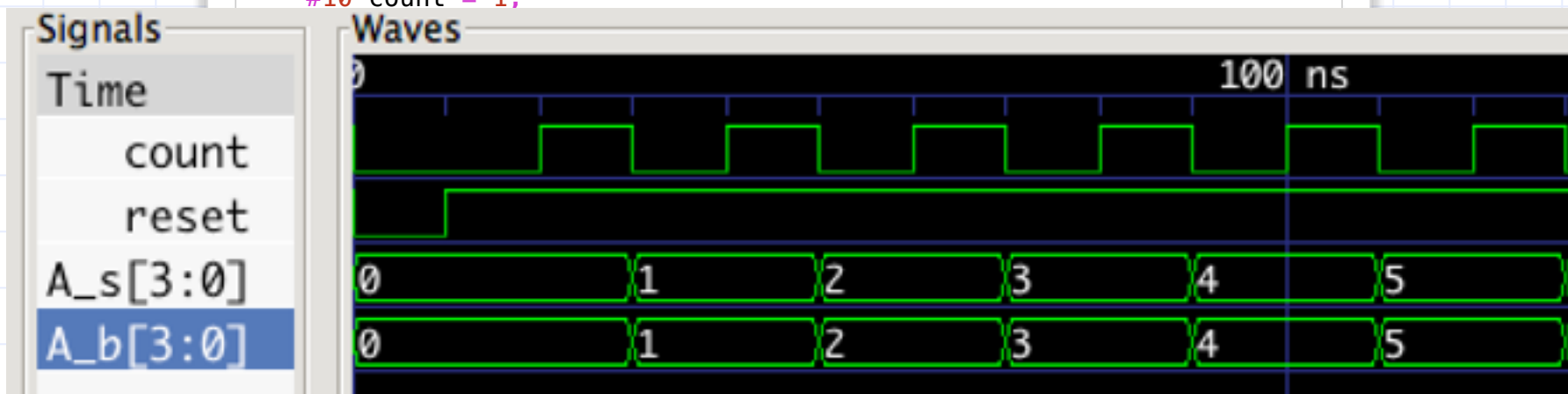  initial begin
    count = 0; reset = 0;
    #10 reset = 1;
    #10 count = 1;
    #10 count = 0;
    #10 count = 1;
    #10 count = 0;
    #10 count = 1;
    #10 count = 0;
    #10 count = 1;
  end
endmodule
```



6-3 RIPPLE COUNTERS

```
module tb_ripple;
  reg    count, reset;
  wire   [3:0] A_s, A_b;

  ripple_counter_str DUT_S (.A(A_s), .reset(reset), .count(count));
  ripple_counter_behav DUT_B (.A(A_b), .reset(reset), .count(count));

  initial begin
    count = 0; reset = 0;
    #10 reset = 1;
    #10 count = 1;
    #10 count = 0;
    #10 count = 1;
    #10 count = 0;
    #10 count = 1;
    #10 count = 0;
    #10 count = 1;
  end
endmodule
```

