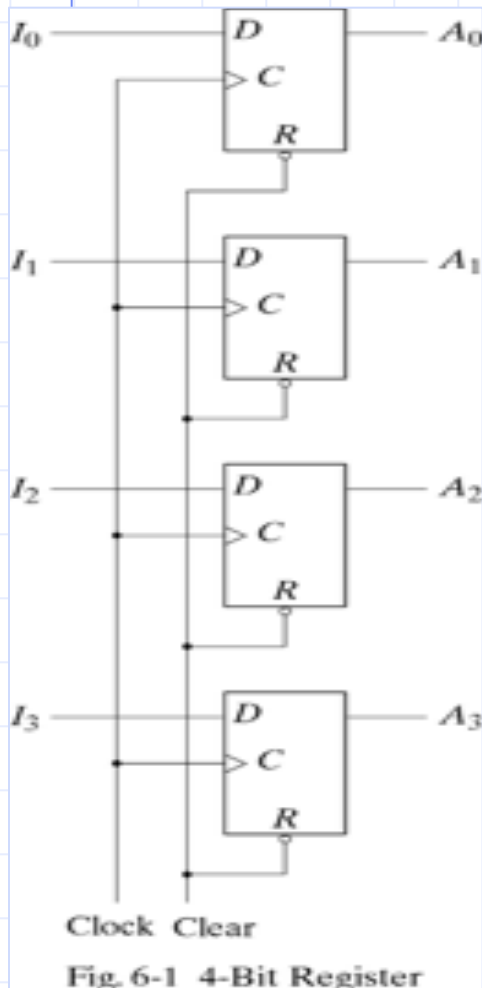


6 Registers and Counters

6-1 REGISTERS

⊕ **Register**- a group of binary cells suitable for holding binary information.



- ❑ Clock=0 -> 1 : input information transferred
- ❑ Clock=0 : unchanged
- ❑ Clear=0 : clearing the register to all 0's prior to its clocked operation.

Register with Parallel Load

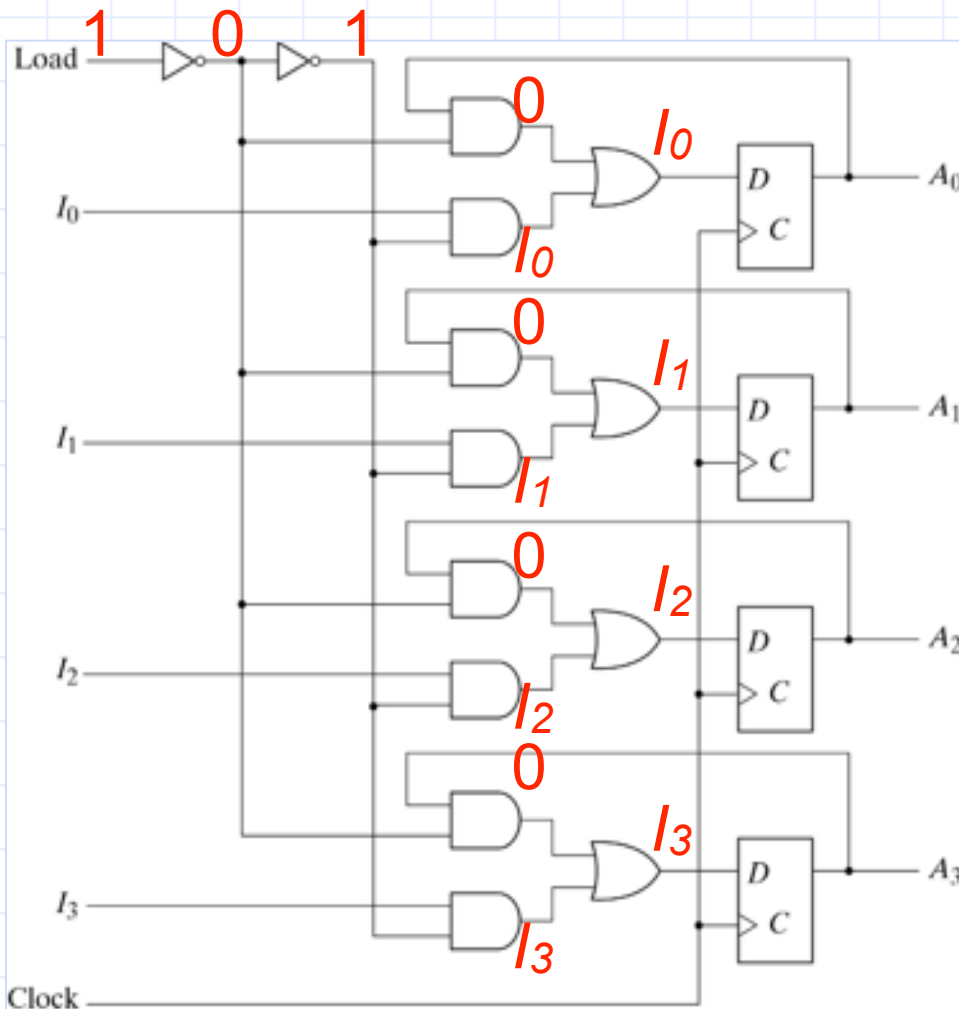


Fig. 6-2 4-Bit Register with Parallel Load

- ❑ Clock=0->1 : input information
-> loading
- ❑ Clock=0 or 0->1 or 1: the content of the register -> unchanged
- ❑ Load input=1 : the **I** inputs are transferred into the register

Register with Parallel Load


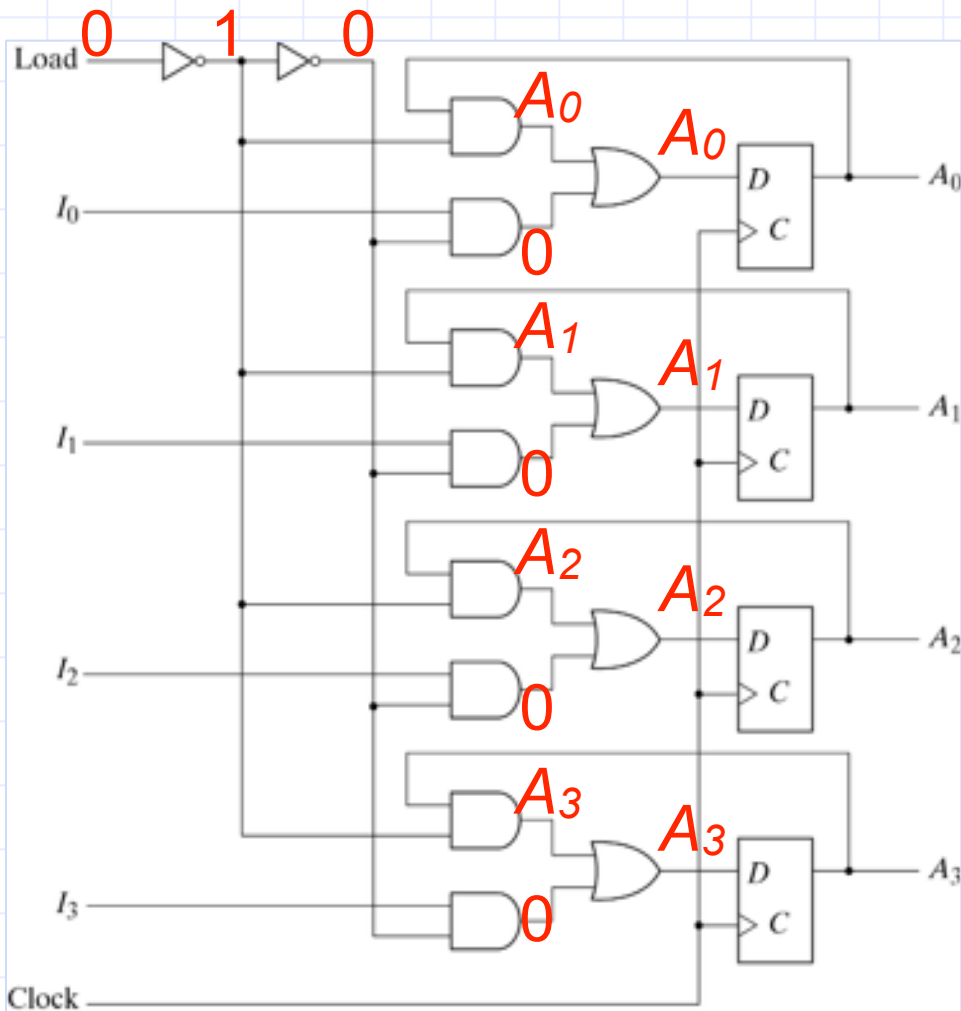


Fig. 6-2 4-Bit Register with Parallel Load

□ Load input=0 ; maintain the content of the register

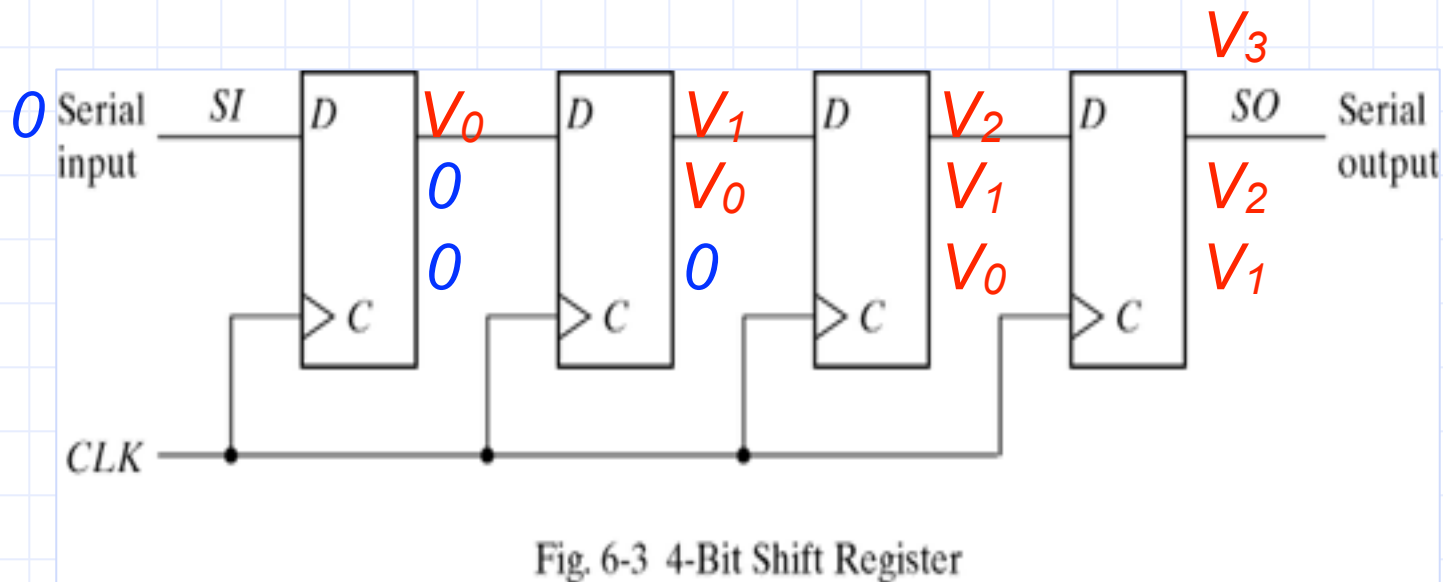6-2 SHIFT REGISTERS


Shift register-capable of shifting its binary information in one or both directions




The simplest shift register

Serial Transfer

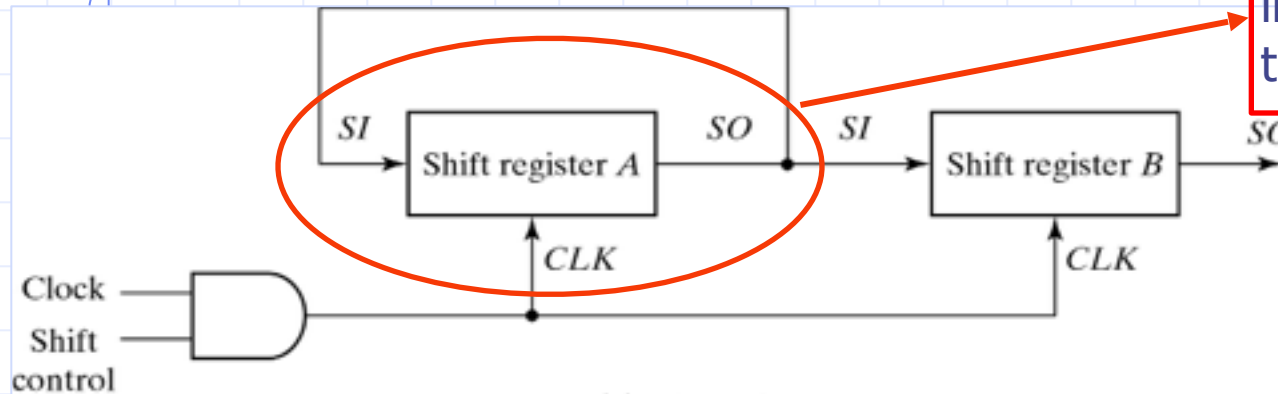To prevent the loss of information stored in the source register



(a) Block diagram

 


(b) Timing diagram

Fig. 6-4 Serial Transfer from Register A to register B


Serial-Transfer Example

Timing pulse	Shift register A	Shift register B	Serial output of B
Initial value	1 0 1 1	0 0 1 0	0
After T ₁	1 1 0 1	1 0 0 1	1
After T ₂	1 1 1 0	1 1 0 0	0
After T ₃	0 1 1 1	0 1 1 0	0
After T ₄	1 0 1 1	1 0 1 1	1


Serial Transfer

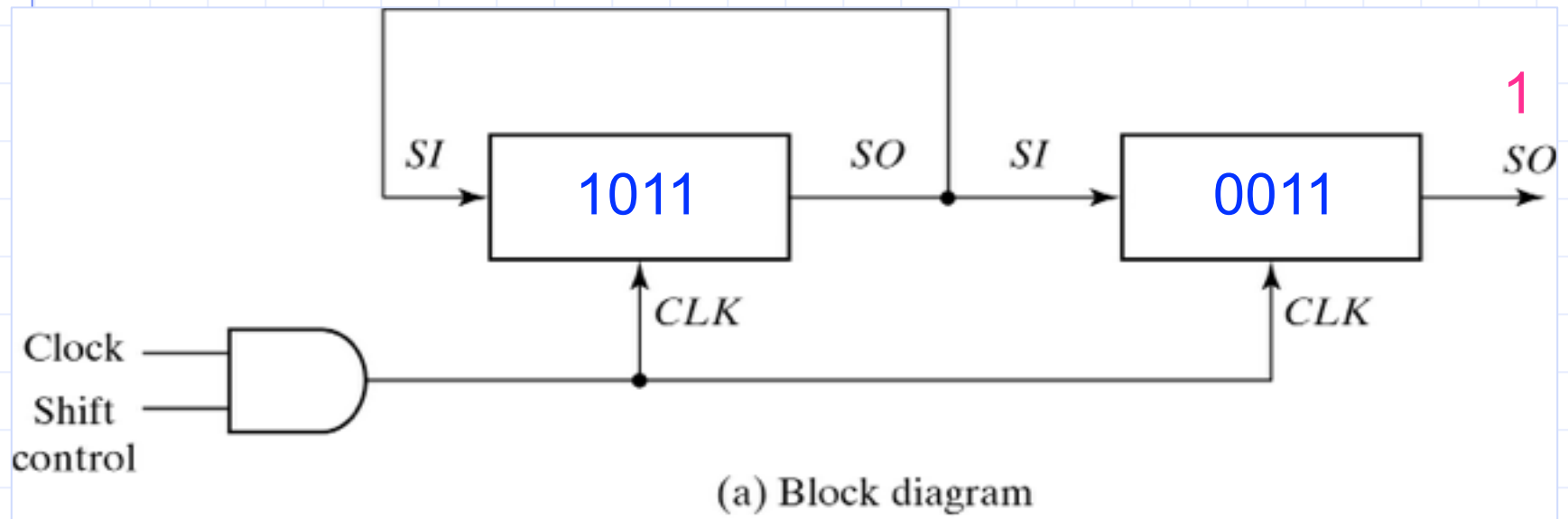


Serial Transfer

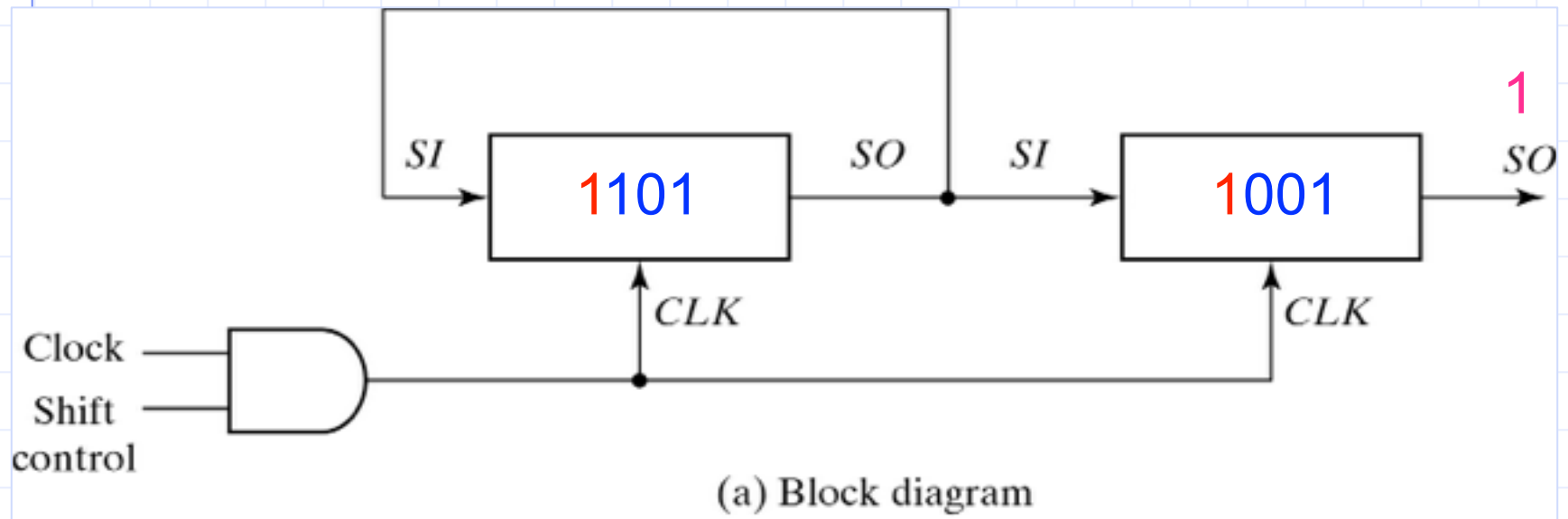


Serial Transfer

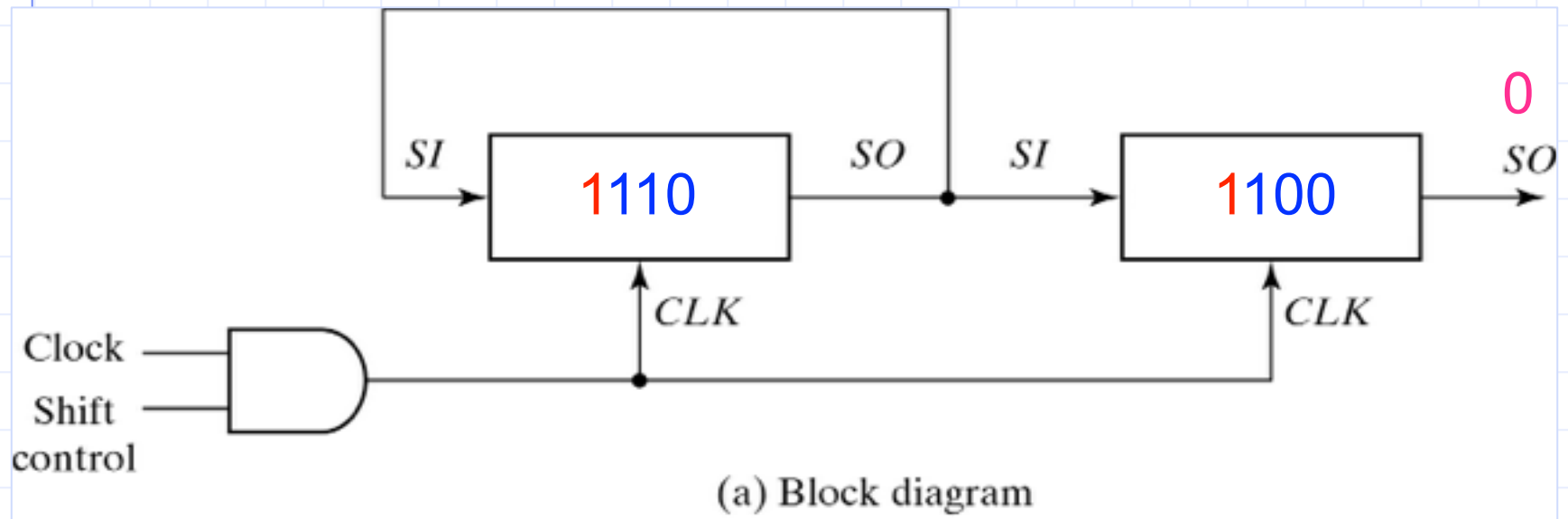

Serial Transfer

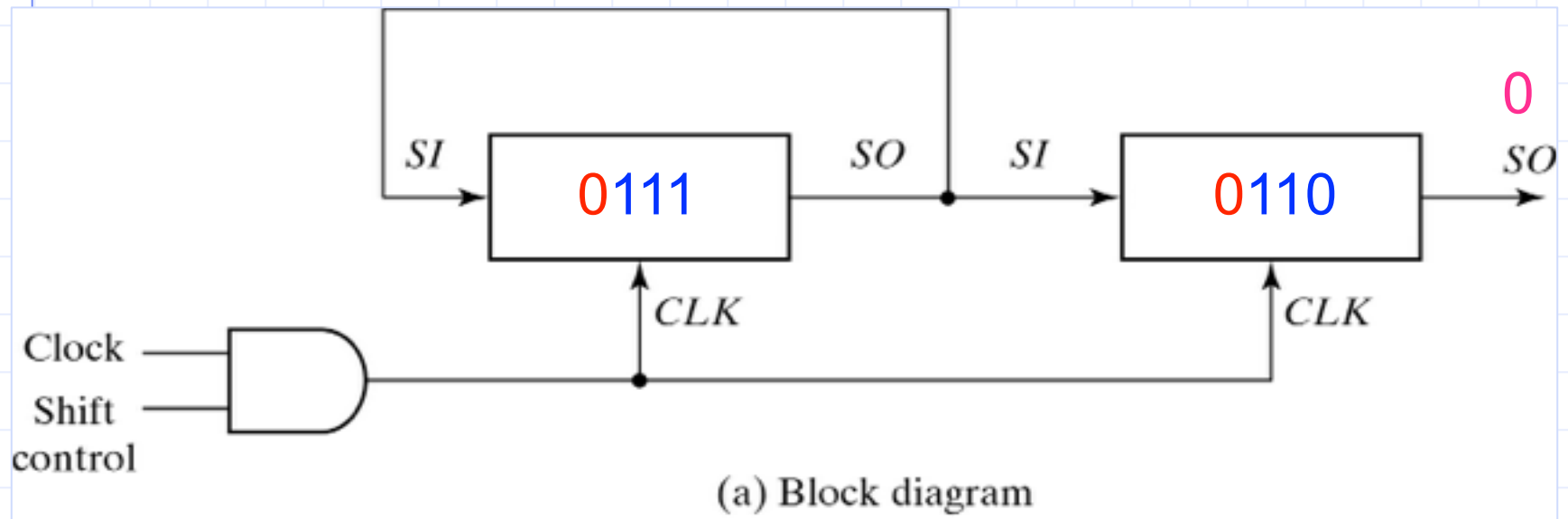

Serial Transfer

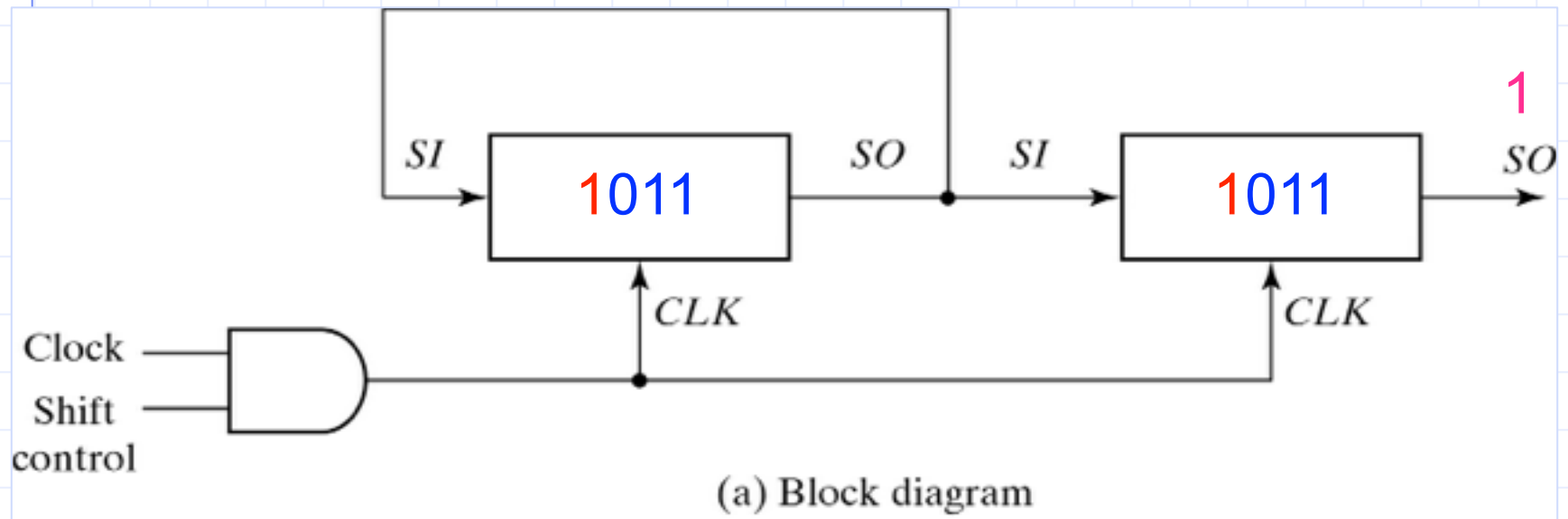

Serial Addition

 


Fig. 6-5 Serial Adder

Operation

- ❑ calculate **A+B**
- ❑ The **SO** of **A** and **B** provide a pair of significant bits for the **FA**
- ❑ Output **Q** gives the input carry at **z**
- ❑ The shift-right control enables both registers and the carry flip-flop.
- ❑ The sum bit from **S** enters the leftmost flip-flop of **A**

Serial Addition

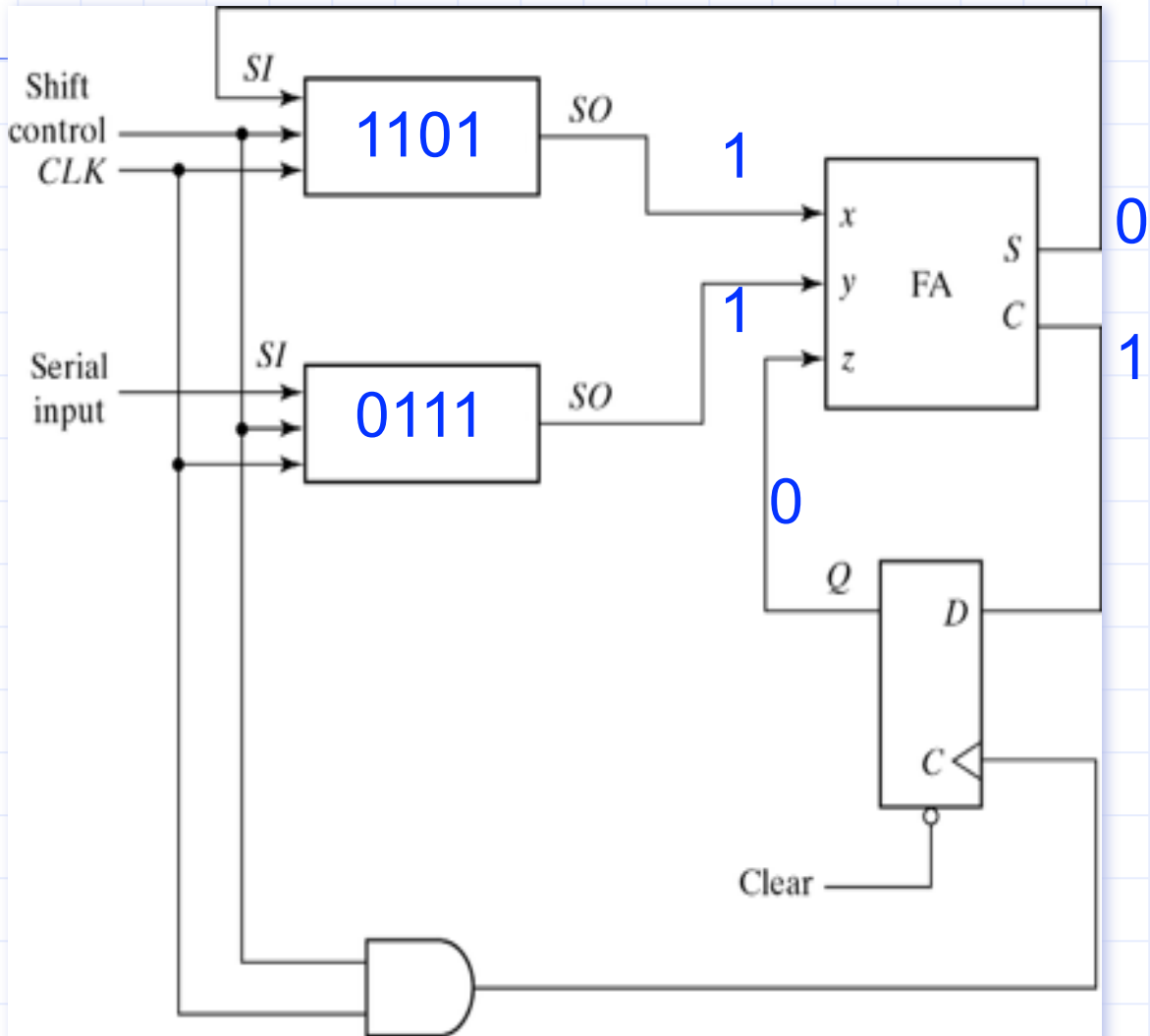


Fig. 6-5 Serial Adder

Serial Addition

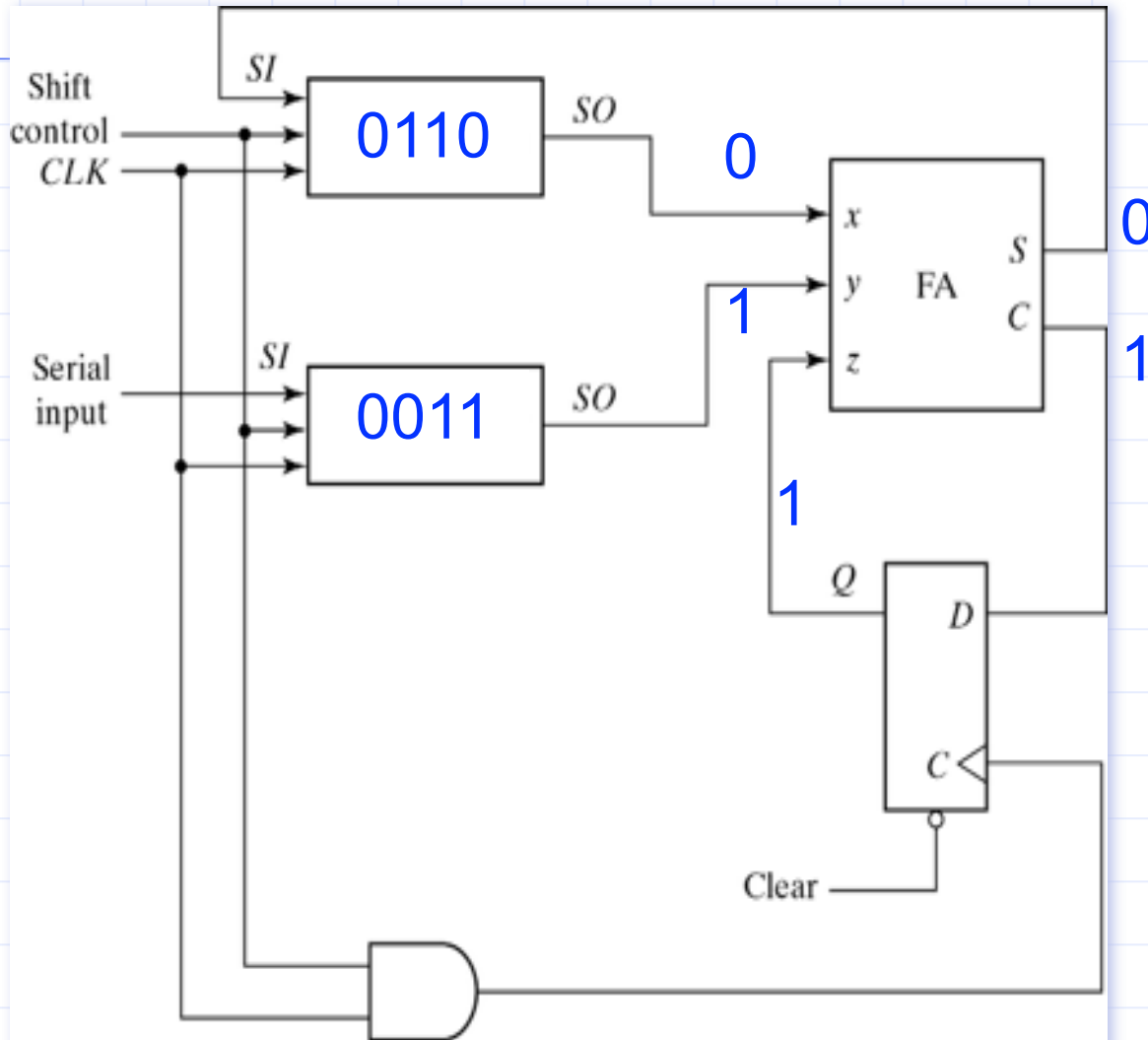


Fig. 6-5 Serial Adder

Serial Addition

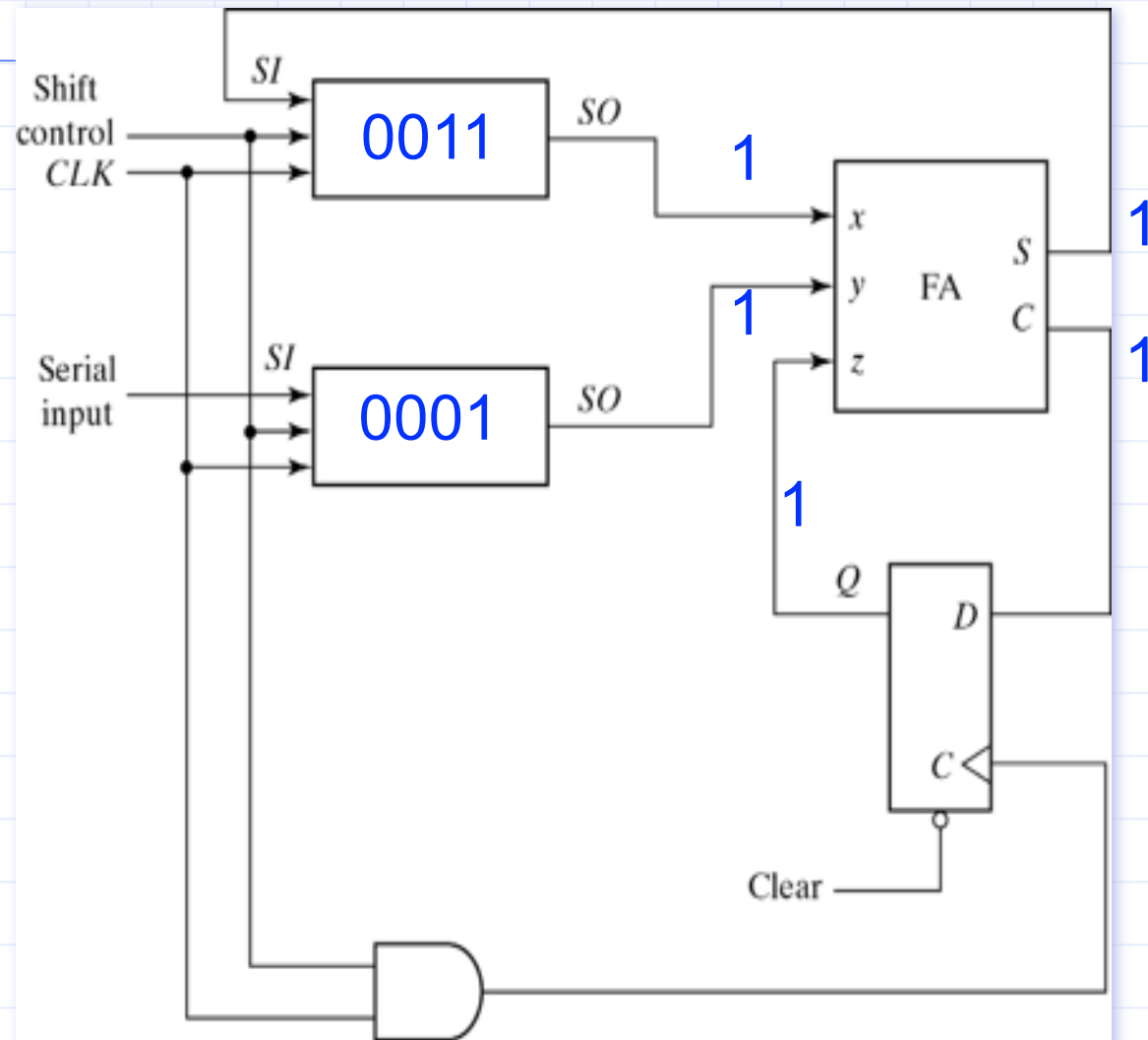


Fig. 6-5 Serial Adder

Serial Addition

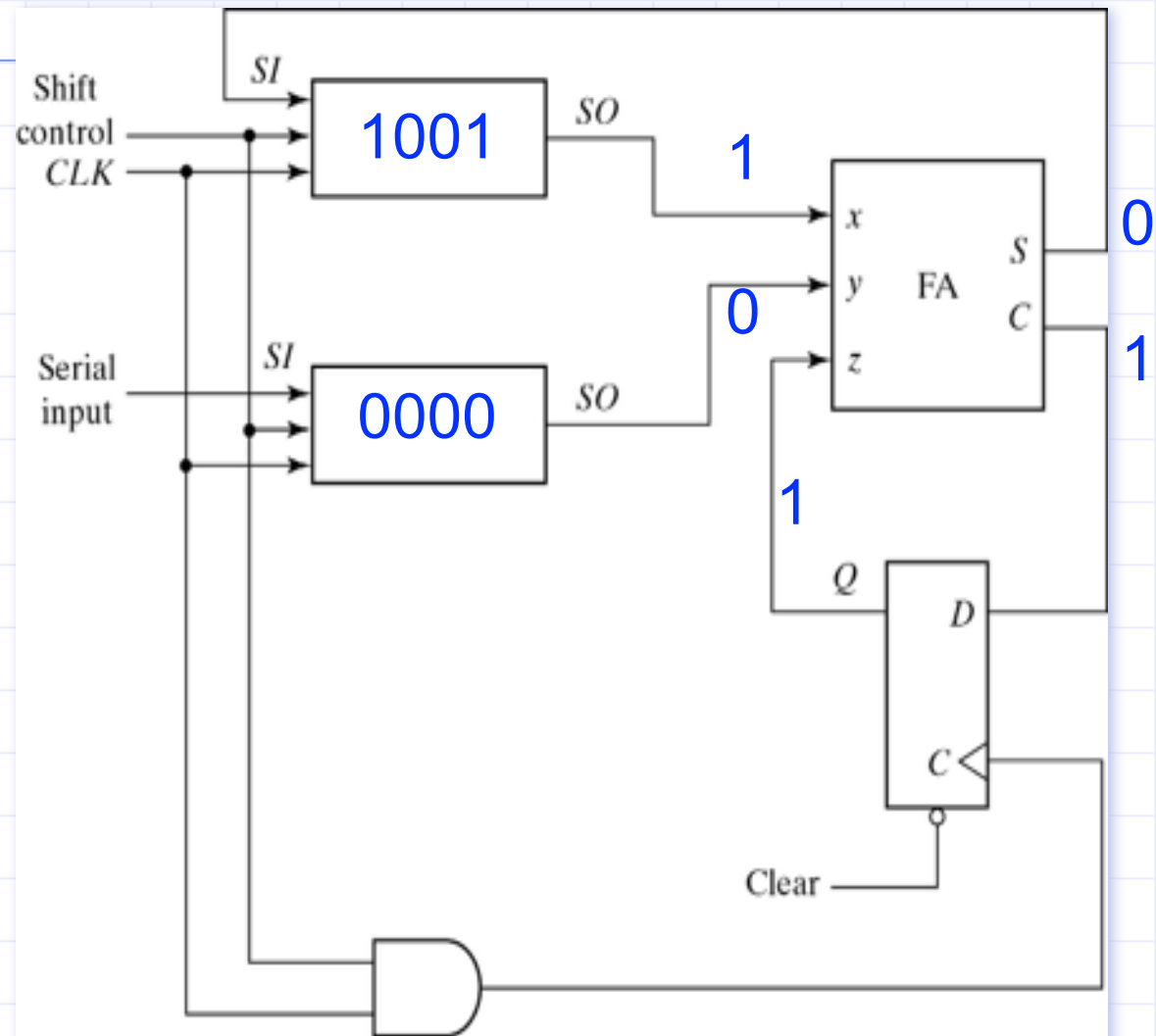


Fig. 6-5 Serial Adder

Serial Addition

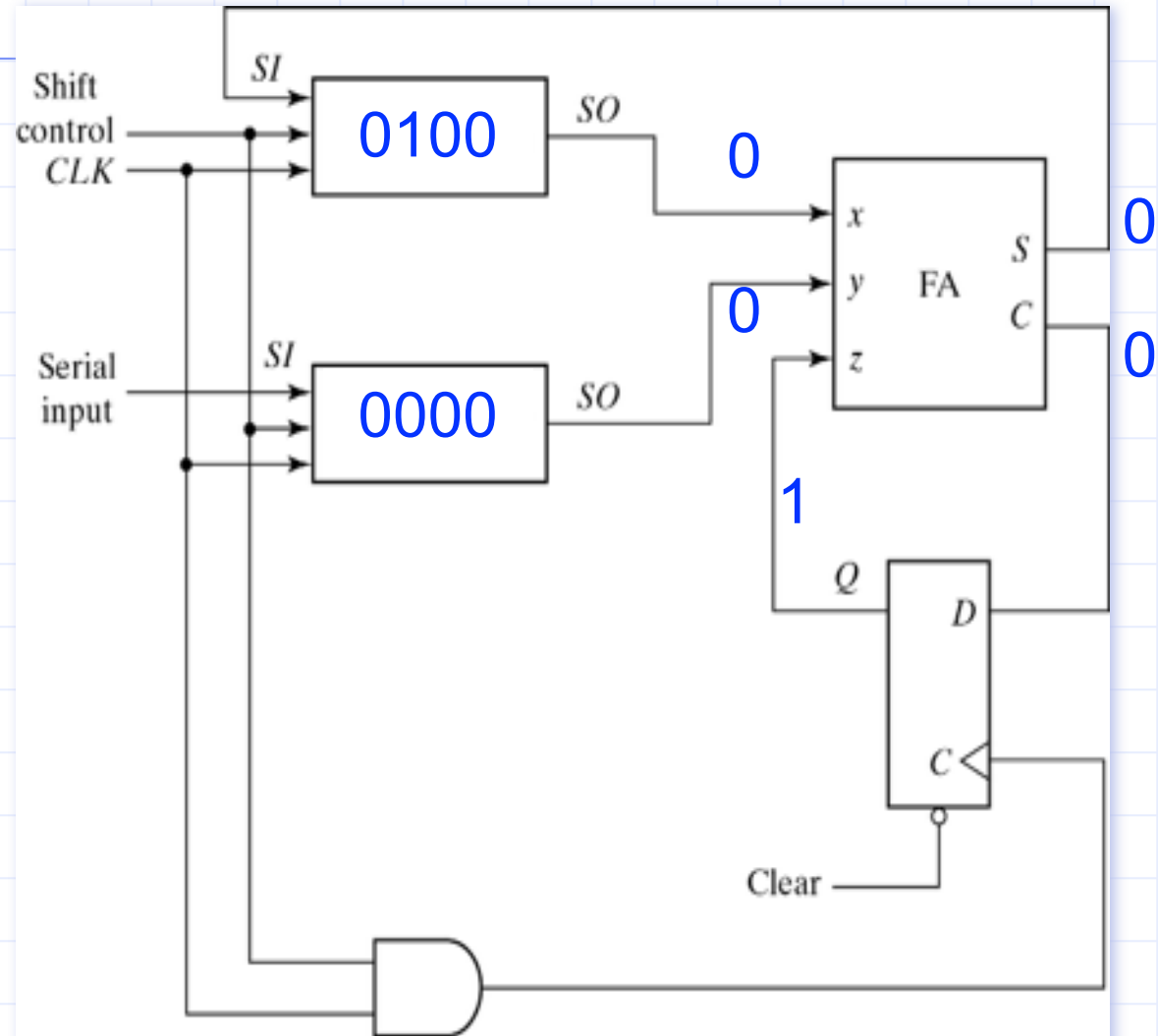


Fig. 6-5 Serial Adder

State Table for Serial Adder

Table 6-2
State Table for Serial Adder

Present State Q	Inputs $x \quad y$		Next State Q	Output S	Flip-Flop Inputs	
					J_Q	K_Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

By k-map

Second form of Serial Adder


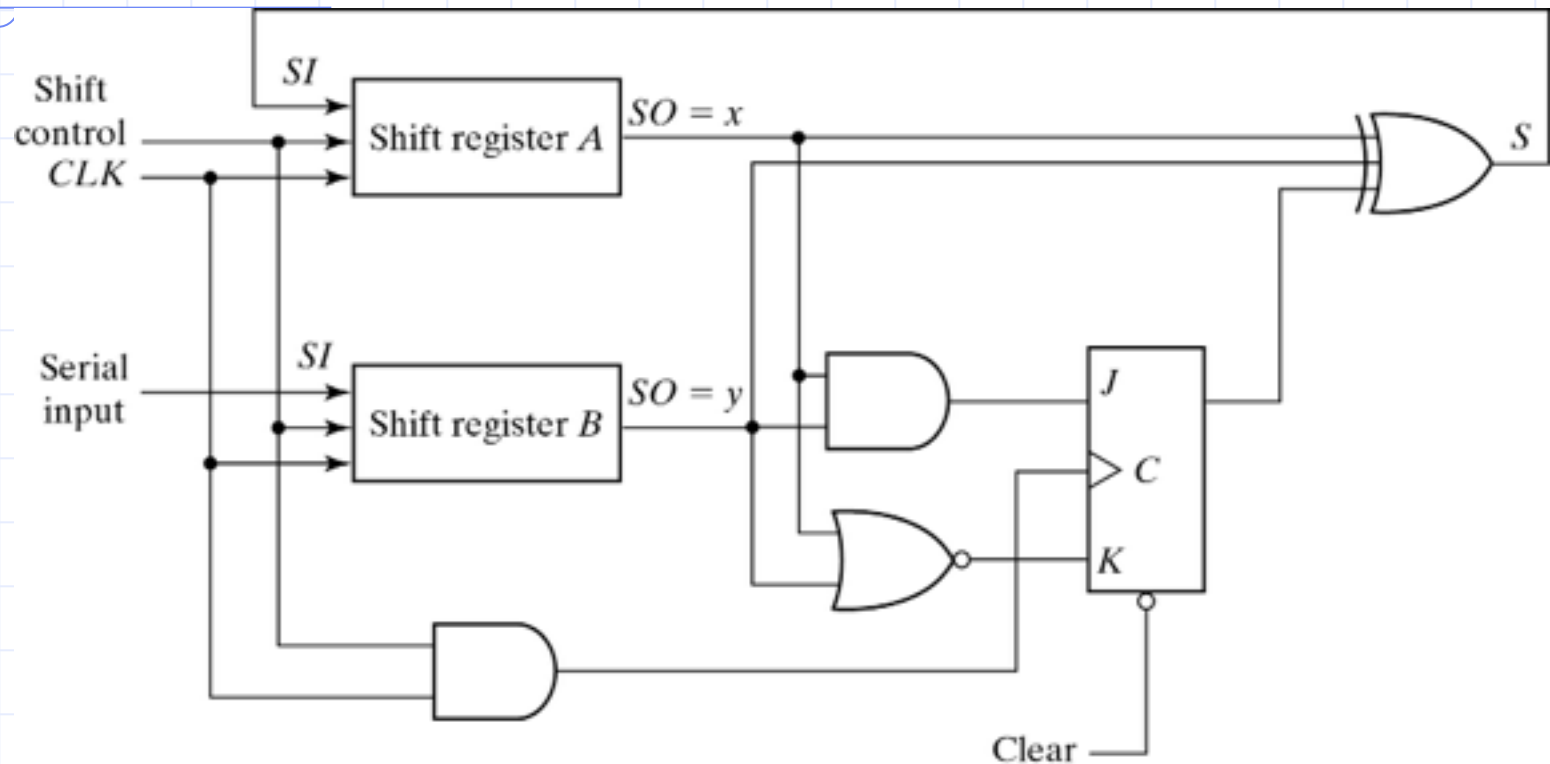


Fig. 6-6 Second form of Serial Adder


Universal Shift Register

 

□ $S_1, S_0 \rightarrow 0, 0$; No change

Fig. 6-7 4-Bit Universal Shift Register


Universal Shift Register

 

□ $S_1, S_0 \rightarrow 0, 1$; Shift right

Fig. 6-7 4-Bit Universal Shift Register


Universal Shift Register

 

□ $S_1, S_0 \rightarrow 1, 0$; Shift left

Fig. 6-7 4-Bit Universal Shift Register


Universal Shift Register

 


□ $S_1, S_0 \rightarrow 1, 1$; Parallel load

Fig. 6-7 4-Bit Universal Shift Register


6-3 RIPPLE COUNTERS

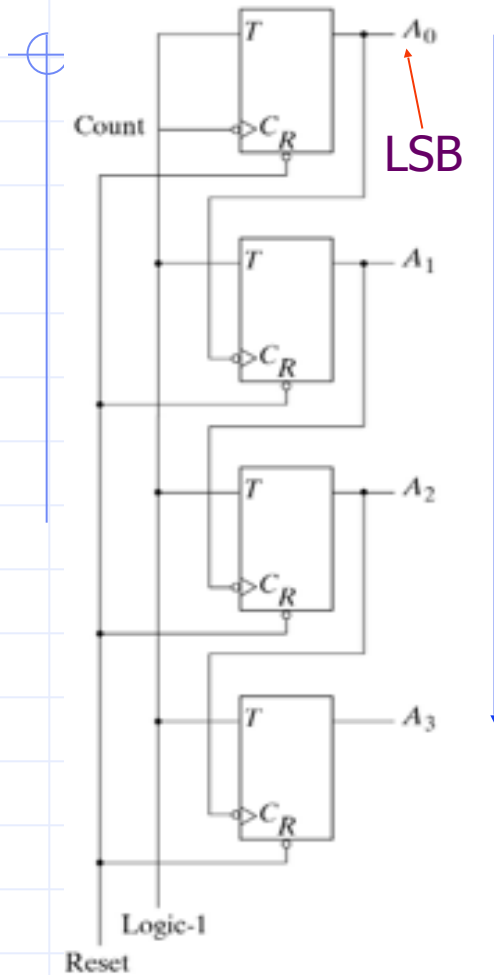


(a) With T flip-flops

 

6-3 RIPPLE COUNTERS

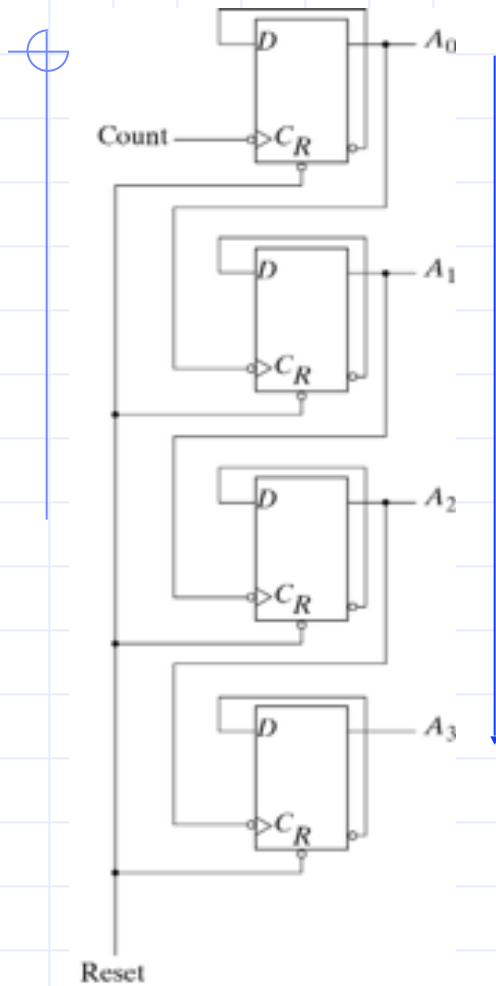

(b) With D flip-flops

 

Count sequence for a binary Counter

Count sequence A₃ A₂ A₁ A₀		Conditions for Complementing
0 0 0 0	Complement A ₀	
0 0 0 1	Complement A ₀	A ₀ will go from 1 to 0
0 0 1 0	Complement A ₀	and complement A ₁
0 0 1 1	Complement A ₀	A ₀ will go from 1 to 0
		and complement A ₁ ;
0 1 0 0	Complement A ₀	A ₁ will go from 1 to 0
0 1 0 1	Complement A ₀	and complement A ₂
0 1 1 0	Complement A ₀	A ₀ will go from 1 to 0
0 1 1 1	Complement A ₀	and complement A ₁
.....		
1 0 0 0	and so on...	

BCD Ripple Counter

Count: 1 -> 0

 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

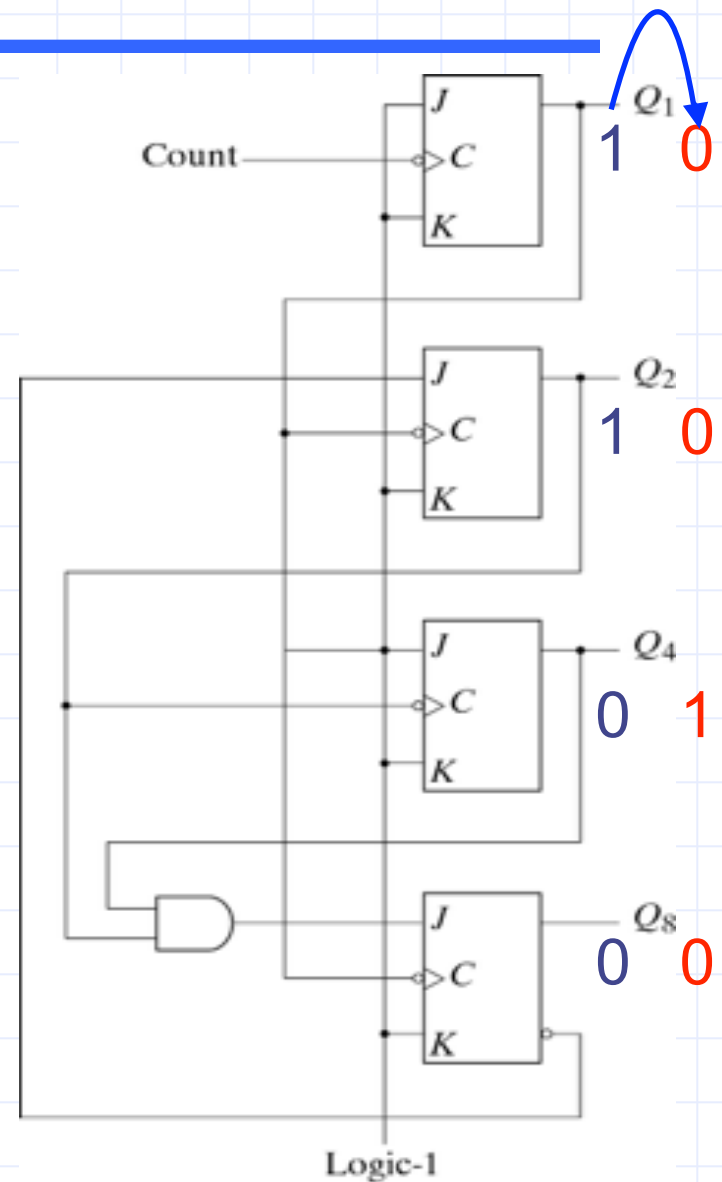


Fig. 6-10 BCD Ripple Counter

BCD Ripple Counter

Count: 1 -> 0

 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

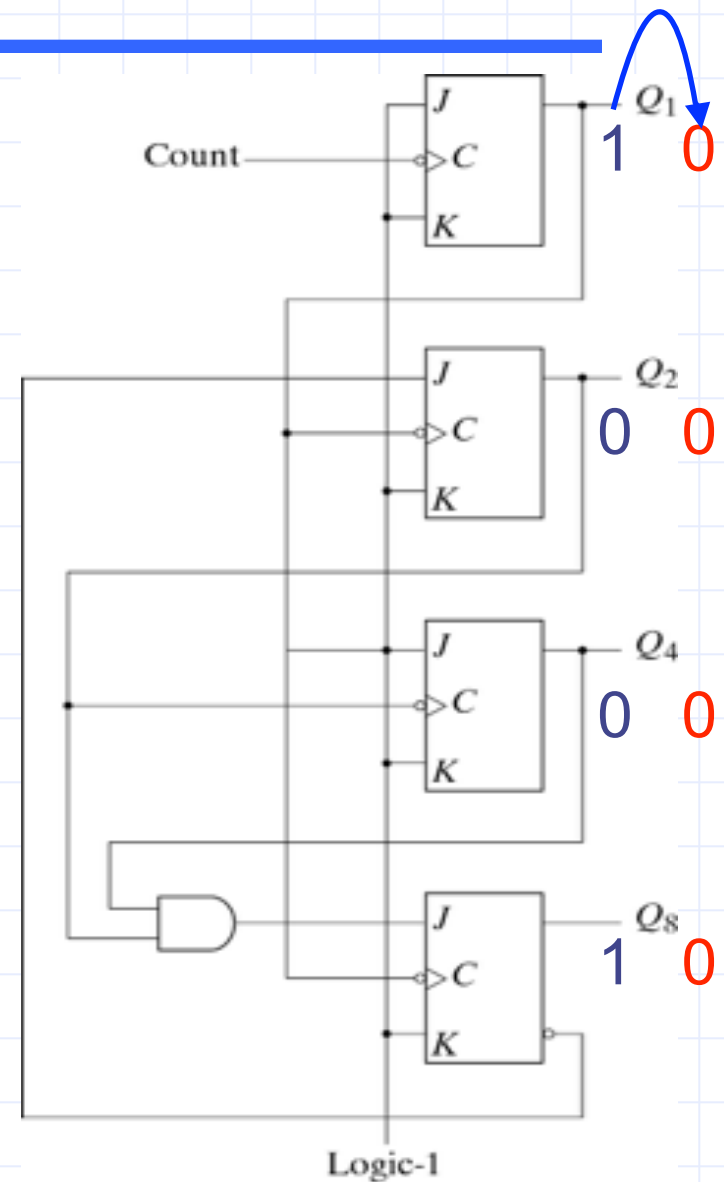


Fig. 6-10 BCD Ripple Counter

BCD Ripple Counter

operation

1. Q_1 is complemented on the negative edge of every count pulse.
2. Q_2 is complemented if $Q_8=0$ and Q_1 goes from 1 to 0. Q_2 is cleared if $Q_8=1$ and Q_1 goes from 1 to 0.
3. Q_4 is complemented when Q_2 goes from 1 to 0.
4. Q_8 is complemented when $Q_4Q_2=11$ and Q_1 goes from 1 to 0. Q_8 is cleared if either Q_4 or Q_2 is 0 and Q_1 goes from 1 to 0

Three-Decade Decimal BCD Counter

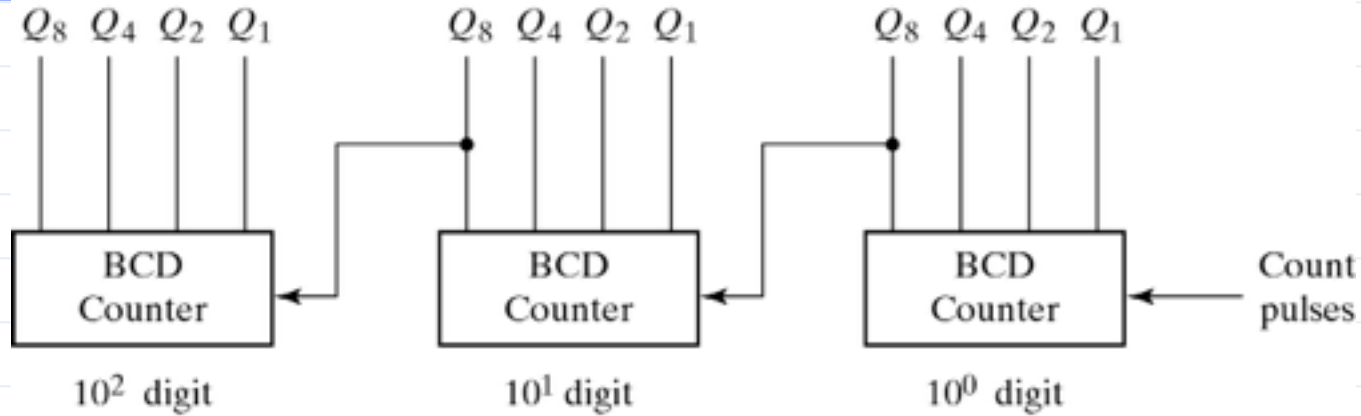


Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter

❑ To count from **0** to **999**, We need a three-decade counter.

6-4 SYNCHRONOUS COUNTERS


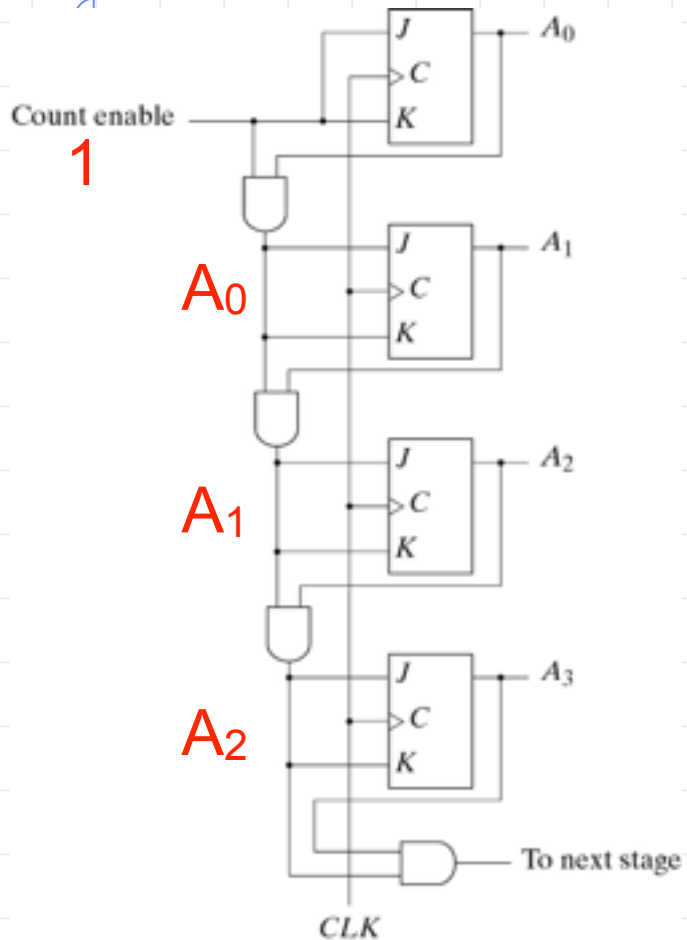


Fig. 6-12 4-Bit Synchronous Binary Counter

- ❑ The first stage A_0 has its **J** and **K** equal to **1** if the counter is enabled .
- ❑ The other **J** and **K** inputs are equal to **1** if all previous low-order bits are equal to **1** and the count is enabled.
- ❑ $A_0 = 1$ 이면, 클럭의 상승에지가 발생할 때 마다, A_1 의 값은 반전된다.

Up-Down Binary Counter

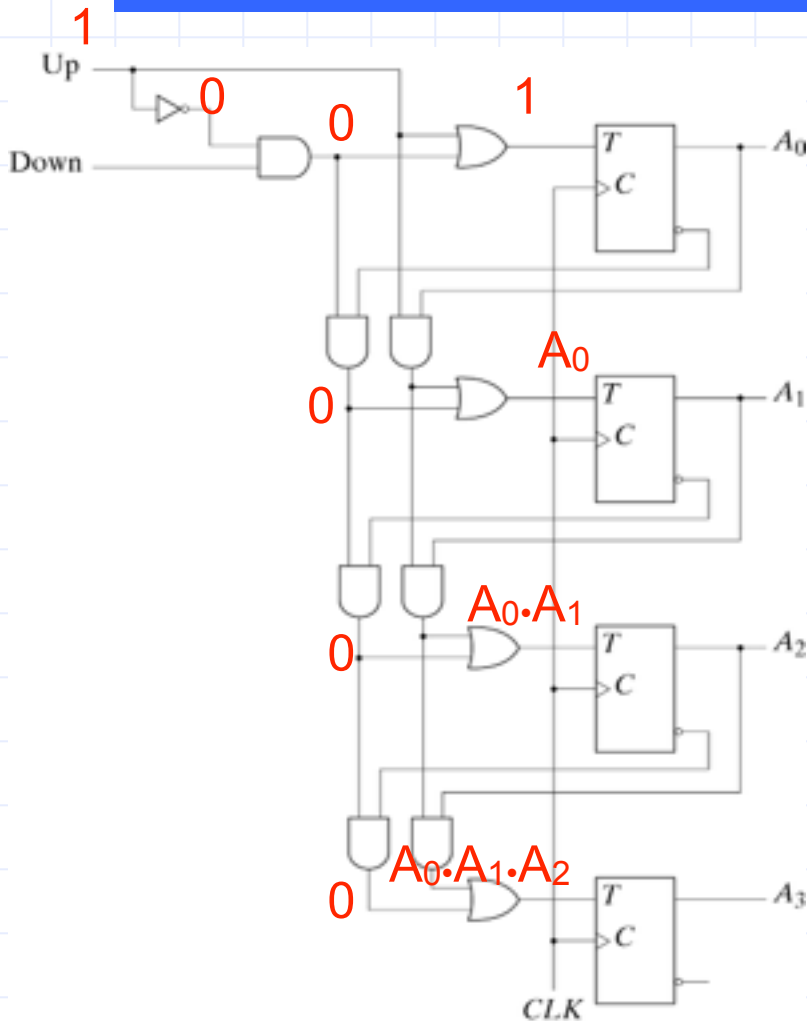


□ **Up** input control=**1** ;count up (the **T** inputs receive their signals from the values of the previous normal outputs of the flip-flops.)

0000
0001
0010
0011
0100

CLK: 0->1
CLK: 0->1
CLK: 0->1
CLK: 0->1

Fig. 6-13 4-Bit Up-Down Binary Counter

Up-Down Binary Counter

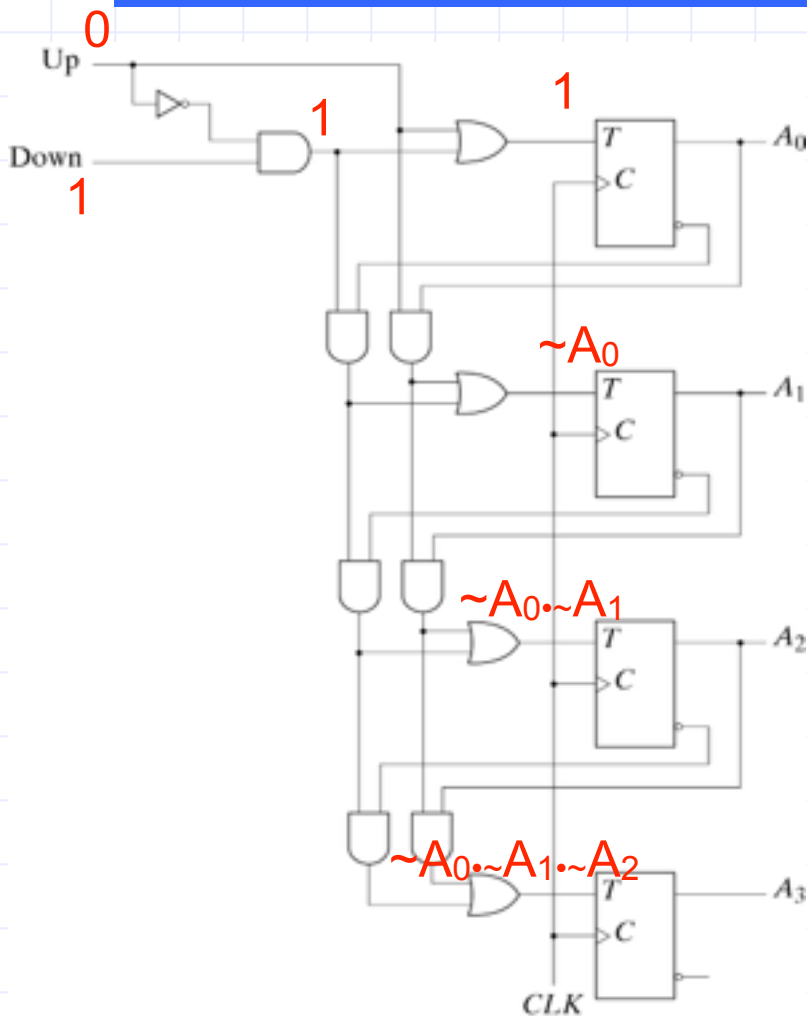

□ **Down** input control=**1**, **up** input control=**0** ;
count down


 


Fig. 6-13 4-Bit Up-Down Binary Counter


Up-Down Binary Counter

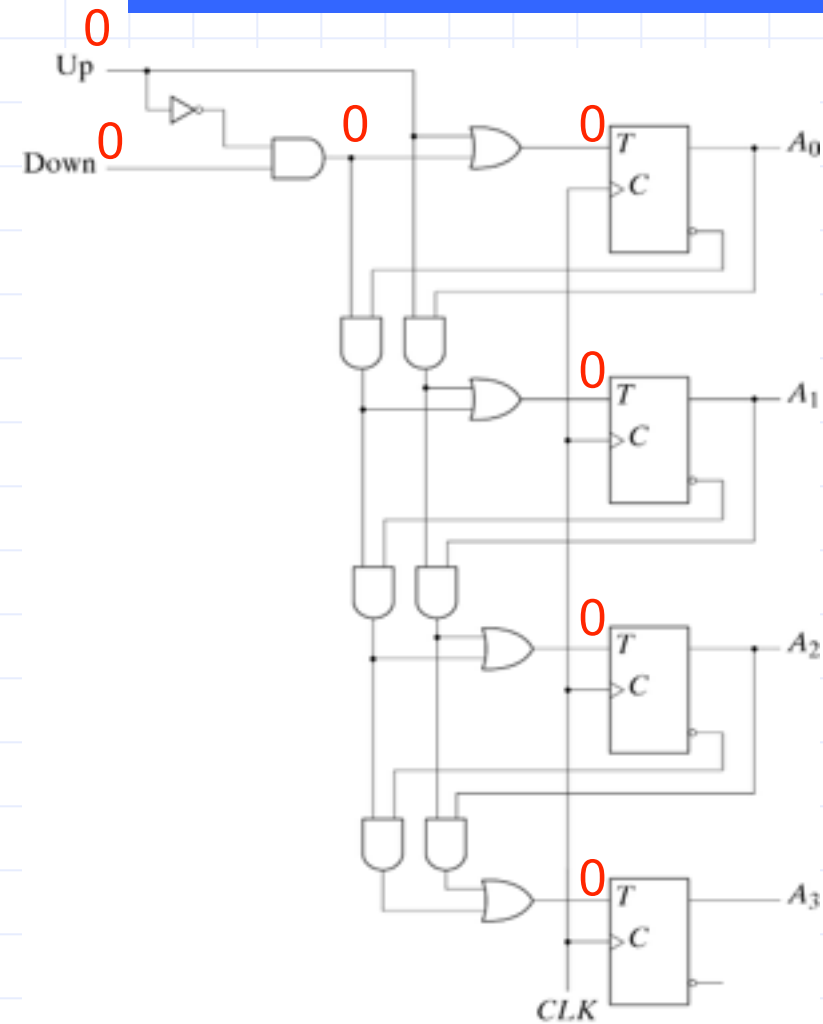

□ **Up=down=0** ;unchanged state

Fig. 6-13 4-Bit Up-Down Binary Counter

Up-Down Binary Counter

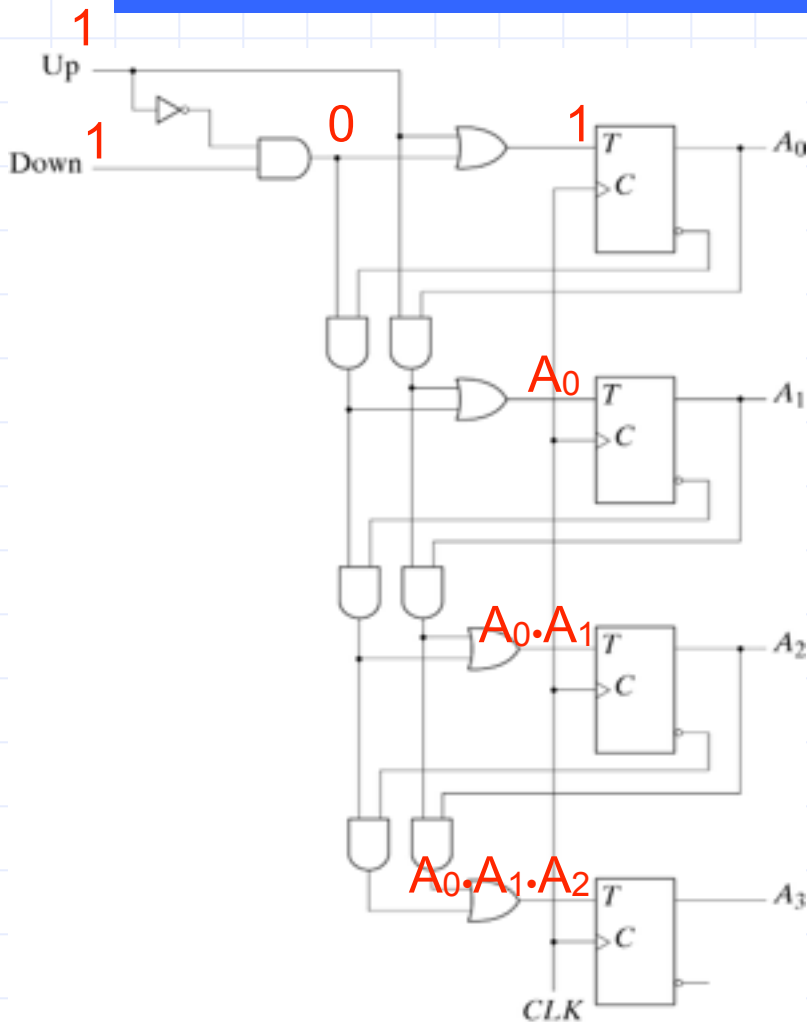

□ Up=down=1 ;count up

Fig. 6-13 4-Bit Up-Down Binary Counter

BCD Counter

Table 6-5
State Table for BCD Counter

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

$$T_{Q1} = 1$$


$$T_{Q2} = Q'_8 Q_1$$

$$T_{Q4} = Q_2 Q_1$$

$$T_{Q8} = Q_8 Q_1 + Q_4 Q_2 Q_1$$

$$y = Q_8 Q_1$$

Binary Counter with Parallel Load

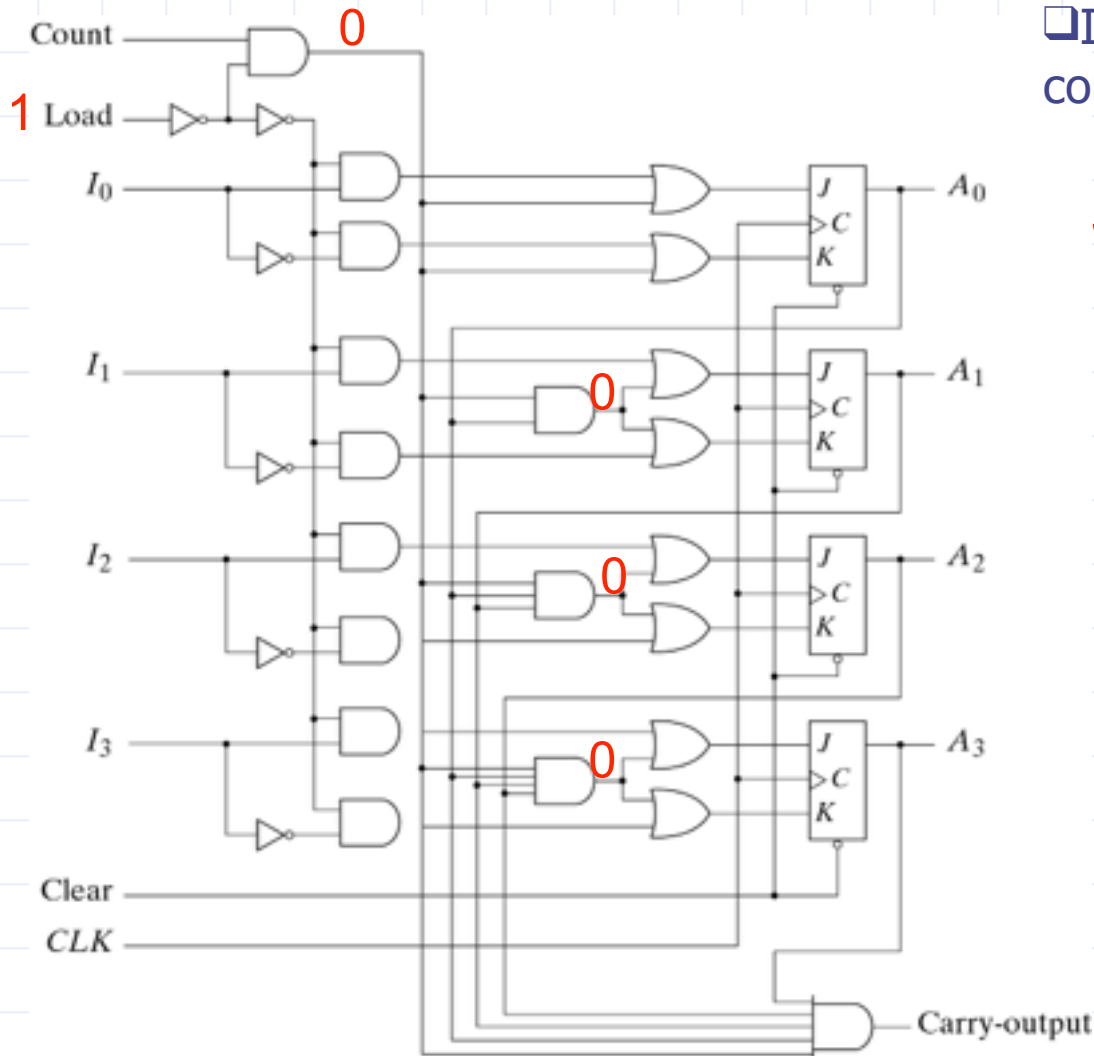

□ Input **load** control=1 ; disables the count sequence ,data transfer

$$J_i = I_i$$

$$K_i = \sim I_i$$

$$A_i = I_i$$

Fig. 6-14 4-Bit Binary Counter with Parallel Load

Binary Counter with Parallel Load

 


Fig. 6-14 4-Bit Binary Counter with Parallel Load

□ **Load** = 0 and **count** = 1 ; count

$$J_0 = 1$$

$$K_0 = 1$$

$$J_1 = A_0$$

$$K_1 = A_0$$

$$J_2 = A_0 \cdot A_1$$


$$K_2 = A_0 \cdot A_1$$

$$J_3 = A_0 \cdot A_1 \cdot A_2$$

$$K_3 = A_0 \cdot A_1 \cdot A_2$$



Binary Counter with Parallel Load

 


□ **Load=0** and **count=0** ; unchanged

$$J_i = 0$$

$$K_i = 0$$

Fig. 6-14 4-Bit Binary Counter with Parallel Load

Binary Counter with Parallel Load

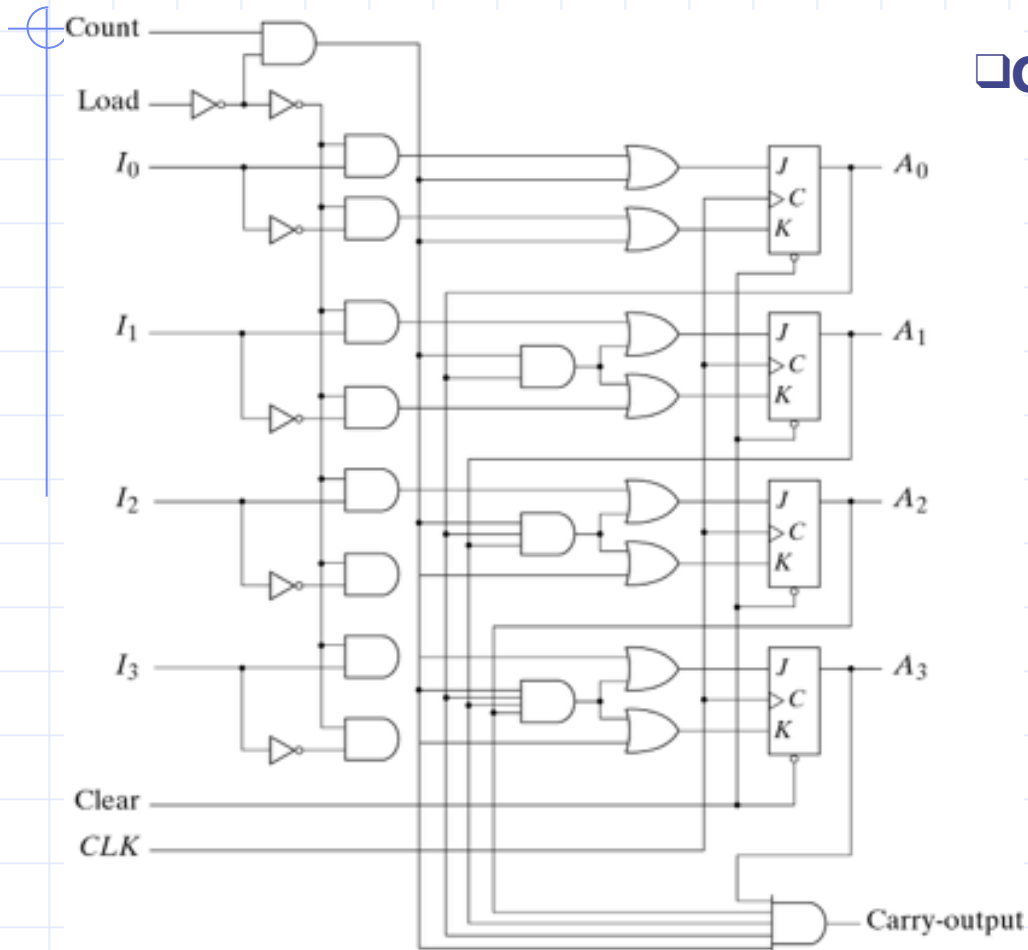

□ **Carry out=1**(all flip-flop=1)

Fig. 6-14 4-Bit Binary Counter with Parallel Load

BCD COUNTER using Binary Counter with Parallel Load

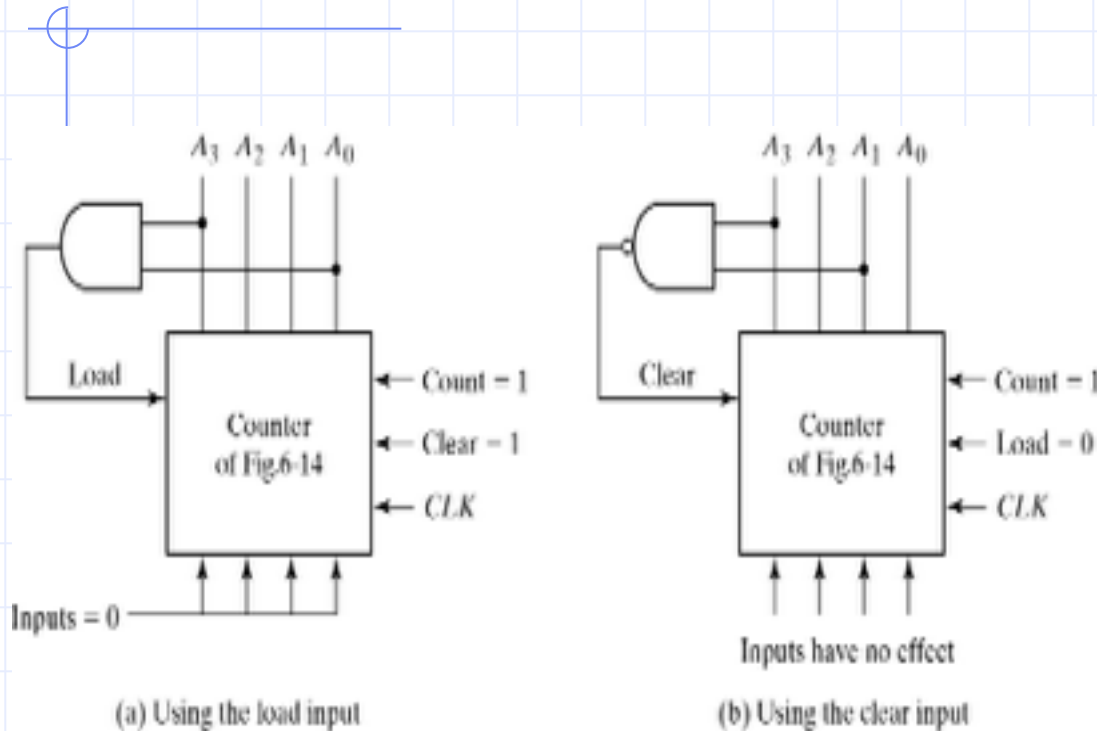



Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load

❑ The **AND** gate detects the occurrence of state **1001(9)** in the output. In this state, the load input is enabled and all-**0**'s input is loaded into register.

❑ The **NAND** gate detects the count of **1010(10)**, as soon as this count occurs the register is **cleared**.

❑ A momentary **spike** occurs in output A_2 as the count goes from **1001** to **1010** and immediately to **0000**

6-5 OTHER COUNTERS

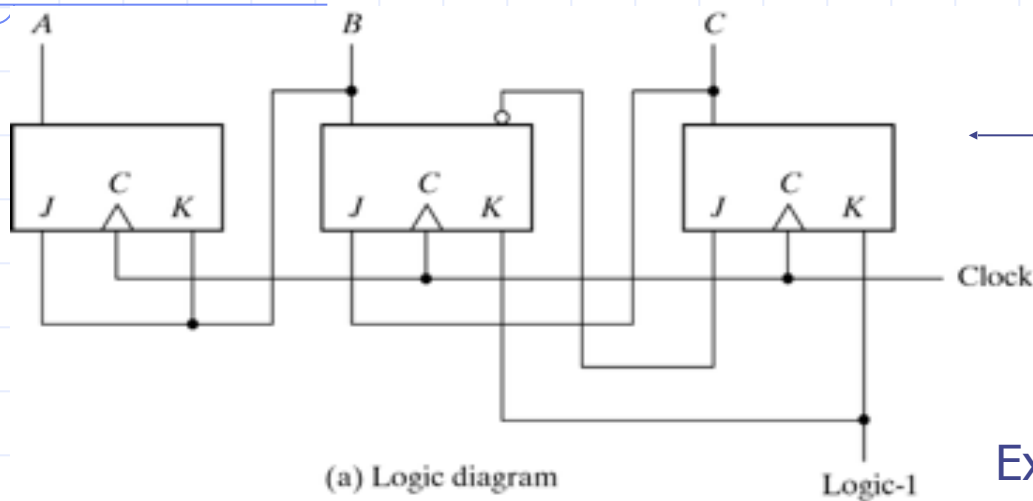

$$\begin{aligned} J_A &= B & K_A &= B \\ J_B &= C & K_B &= 1 \\ J_C &= B' & K_C &= 1 \end{aligned}$$

Except **011, 111**

 


Fig. 6-16 Counter with Unused States

Table 6-7
State Table for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

Ring Counter


 
 


Fig. 6-17 Generation of Timing Signals

- ❑ A circular shift register with only one flip-flop being set at any **particular time**. ; all others are cleared.
- ❑ **The single bit** is shifted from one flip-flop to the other.

Johnson Counter

 

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

Fig. 6-18 Construction of a Johnson Counter

□ A circular shift register with **the complement output of the last flip-flop** connected to the input of the first flip-flop.